



# Civinnovate

Discover, Learn, and Innovate in Civil Engineering

## U:1: Electric Component and Circuits

Basic passive component.

(a) active components: if power is generated. eg. battery, voltage source, current source.

(b) Passive components: if power is consumed,  
Inductance and capacitor - store energy  
Resistor  $\rightarrow$  absorbed

### (a) Resistor:

Resistance :- Resistance is defined as a property of a material to oppose the flow of electric current through it. It depends on intrinsic character of material and geometry, it is denoted by  $R$  and unit is  $\Omega$ , and given by

$$R = \frac{\rho l}{A} \Omega$$

where,

$\rho$   $\rightarrow$  resistivity of material

$l$   $\rightarrow$  length of "

$A$   $\rightarrow$  cross sectional area ..

Now,


$$\rho = R \frac{A}{l} \text{ if } A = 1\text{m}^2 \text{ and } l = 1\text{m.}$$

Specific resistance is defined as the resistance offered by the body to the flow of current.

Resistor = It is an electronic device built to have specific value of resistance. It is used in circuit to limit or control the flow of current and divide the voltage to produce heat.

Types of resistors: (A)  $\Rightarrow$  Fix value

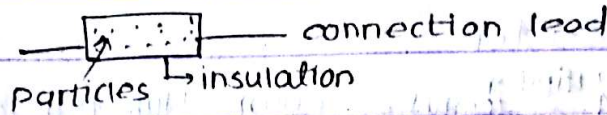(a) Carbon resistor: They are made of finely ground particles of carbon and ceramic and enclosed in a insulation.




They are compact, robust and easy to manufacture, Temperature sensitive and high tolerance.

(b) Wirewound :- It consists of uniform wire wound around a insulating material. They have high accuracy so used in the circuit where the value of resistance is very critical.




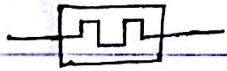
(c) Film resistor: Thin or thick layer of resistive material is deposited in an insulating base to make film resistor.



They are very compact and accurate and used in integrated circuits.

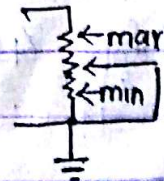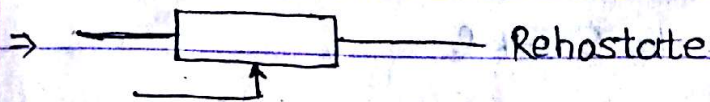(B) Adjustable or variable resistor:


$\rightarrow$  value of resistance can be changed from min to max in given range. It is basically cylindrical wire wound resistor with a moveable arm that in contact with a resistance element.



$\Rightarrow$  Potentiometer (Pot)

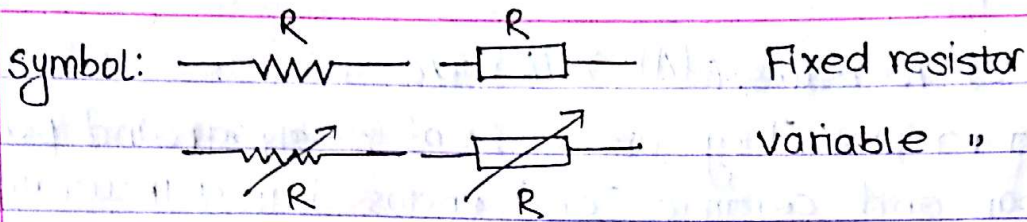$\Rightarrow$  Trimmer if tool is needed to adjust resistance





\* Color code in Resistor

(Small gap) left	Multiplier (Right)	Color	Numerical value	Multiplying factor	tolerance
A	B	C	D		
digit	tolerance.				
$R = AB \times C \pm D$					
		Black	0	$10^0$	$\pm 0\%$
		brown	1	$10^1$	$\pm 1\%$
		red	2	$10^2$	<del><math>\pm 1\%</math></del> $\pm 2\%$
		orange	3	$10^3$	<del><math>\pm 1\%</math></del>
		yellow	4	$10^4$	
		Green	5	$10^5$	
		Blue	6	$10^6$	
		violet	7	$10^7$	
		Grey	8	$10^8$	
		white	9	$10^9$	
		Gold	-	$10^{-1}$	$\pm 5\%$
		Silver	-	$10^{-2}$	$\pm 10\%$
		no color	-		$\pm 20\%$

eg: find nominal resistance and possible range of actual resistor of band having color band yellow, violet, Orange, silver

$$R = AB \times C \pm D$$

$$= 47 \times 10^3 \pm 10\% \text{ of } R$$

$$= 47 \text{ k}\Omega$$

Range 42.3 k $\Omega$  to 51.7 k $\Omega$

(ii)  $\overbrace{\text{brown, black}}^{\text{small gap}}, \overbrace{\text{red, gold}}^{\text{large gap}}$

$$R = ABXC \pm D$$
$$= 10 \times 10^2 \pm 5\%$$
$$= 1000 \pm 5\%$$
$$= 1 \text{ k}\Omega \pm 5\%$$

$$R = 1 \text{ k}\Omega$$

$$\text{Range} = \left(1000 - 1000 \times \frac{5}{100}\right) \text{ to } \left(1000 + 1000 \times \frac{5}{100}\right)$$
$$= 950 \text{ to } 1050$$

Black Boy Ride On Your  
Green Bike in Very Good  
weather.

## (B) Capacitor

① capacitance = capacitance is a property of element to store charge in it and oppose to any change in voltage. It is measured in Farad, most common unit  $\mu\text{F}$ ,  $\text{nF}$ ,  $\text{pF}$  ( $10^{-12}$ )

A capacitor is a physical device that store energy by virtue of voltage exist in it.

When, voltage  $v$  is applied on a capacitor of capacitance  $C$ , then charge stored in it is given by,

$$Q = VC$$

current voltage relationship, on capacitor,

$$I = \frac{dq}{dt}$$
$$= \frac{d(VC)}{dt}$$
$$I = C \frac{dv}{dt}$$


Reactance or Impedance of capacitor :

$Z_c = \frac{1}{\omega C}$  where,  $\omega \Rightarrow$  angular velocity

$Z_c = \frac{1}{2\pi fC}$

Application:

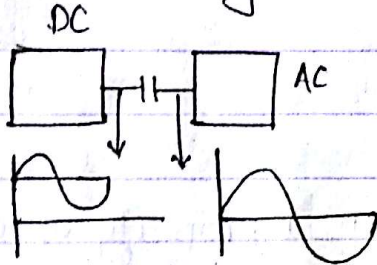- Ⓐ It is used to store electrical energy
- Ⓑ Oppose any change in voltage across it
- Ⓒ To couple AC voltage between circuit and oppose DC



Types of capacitor:

Ⓐ fixed value capacitor: Based on dielectric used

- mica capacitor
  - ceramic capacitor
  - film capacitor
- } non polar / capacitor


⊗ Electrolytic capacitor  $\rightarrow$  polar capacitor



Ⓑ variable capacitor : variable capacitor is usually made of air dielectric.

for parallel plate capacitor  $C = \frac{\epsilon_0 A}{d}$


Symbol:

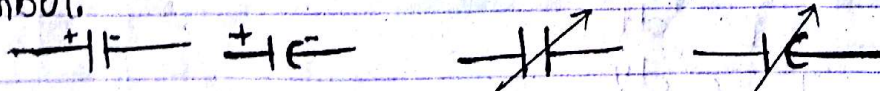


fixed value

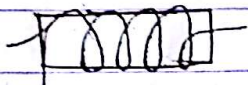
## Inductor:

It is a property of circuit to oppose the change in current through it. Its unit is Henry. Most common unit  $\mu\text{H}$ ,  $\text{mH}$ . Inductor is a circuit element that stores energy by virtue of a current flowing through it and stores energy in the form of magnetic field.



Based on core used,

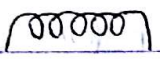air core  core is non ferrous material

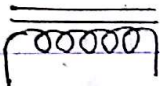iron core  core is ferrous

in inductor,  $V \propto \frac{di}{dt}$

$$V = L \frac{di}{dt}$$

$$\therefore L = \frac{V}{\left(\frac{di}{dt}\right)}$$

impedance:  $Z_L = j\omega L = 2\pi fL$  (complex no.)

## Application of Inductor

- (a) store electrical energy
- (b) To oppose any change in current through it
- (c) To block AC signal

## Types of inductor

- (a) fixed value inductor

→ filter chokes → power supply

→ Audio frequency chokes (AFC) to block audio signal

RF chokes: to block radio freq signals

(b) variable inductor:-

used in tuning circuit, phase shifting and switching of bands in amplifiers

\* movable core-type ~~700007~~

\* Tap switching type

Ohm's law:-

Physical condition remaining constant, at constant temperature, the current flowing in any conductor is directly proportional to the potential difference between two ends, i.e.,

$$I \propto V$$

$$I = \frac{V}{R}$$

where  $\frac{1}{R}$  is a proportionality constant.


$\therefore V = IR \rightarrow R$  is defined as the opposition to the flow of electric current through the conductor.

Kirchhoff's law:-

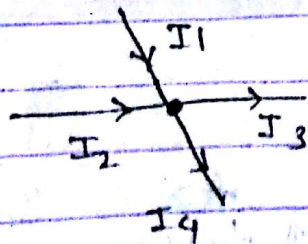(a) Kirchhoff's current law: (KCL):- The algebraic sum of current at any point is zero, i.e.,  $\sum I = 0$


$$I_1 + I_2 = I_3 + I_4$$

$$\sum (I_{\text{incoming}}) = \sum (I_{\text{outgoing}})$$



⑥ Kirchhoff's voltage law (KVL): The algebraic sum of voltage in any closed loop is zero. or The algebraic sum of the product of current and resistance in a loop is zero. i.e.,  $\sum V = 0$

or  $\sum I \times R = 0$

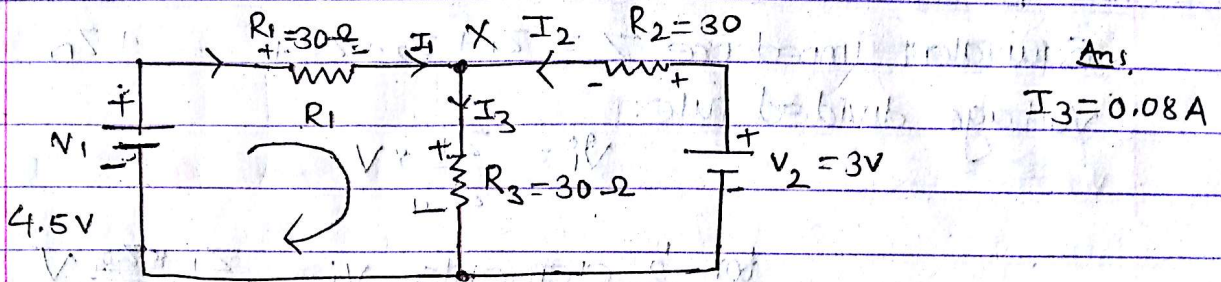

Sign convention:- voltage drop is taken as negative  
voltage rise is taken as +ve

loop A  $\Rightarrow V_1 - I_1 R_1 - I_3 R_3 = 0$

$\therefore V_1 = I_1 R_1 + I_3 R_3$  ——— ①

loop B  $\Rightarrow V_2 - I_2 R_2 - I_3 R_3 = 0$

$\therefore V_2 = I_2 R_2 + I_3 R_3$  ——— ②

at point X, KCL

$I_3 = I_1 + I_2$

using eq ①

$V_1 = I_1 R_1 + I_3 R_3$

$V_1 = I_1 R_1 + (I_1 + I_2) R_3$

$4.5 = 30 I_1 + 30 I_1 + 30 I_2$

$4.5 = 60 I_1 + 30 I_2$

$I_1 = \left( \frac{4.5 - 30 I_2}{60} \right)$

eq ②

$V_2 = I_2 R_2 + I_3 R_3$

$3 = 30 I_2 + 30 I_1$

$3 = 30 I_2 + 30 \times \left( \frac{4.5 - 30 I_2}{60} \right)$


or,  $6 = 120 I_2 + 4.5 - 30 I_2$

or,  $1.5 = 90 I_2$

$\therefore I_2 = \frac{1.5}{90} =$

## Series and parallel combination of base components

(a) Series combination:

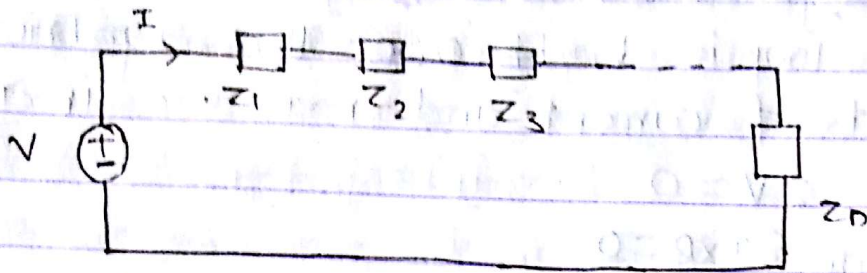


Equivalent impedance  $Z = Z_1 + Z_2 + Z_3 + \dots + Z_n$

voltage divided rule:

$$V_i = \frac{Z_i}{Z_{eq}} \times V$$

for 2 elements  $V_i = \frac{Z_1}{(Z_1 + Z_2)} V$

(b) Parallel combination:

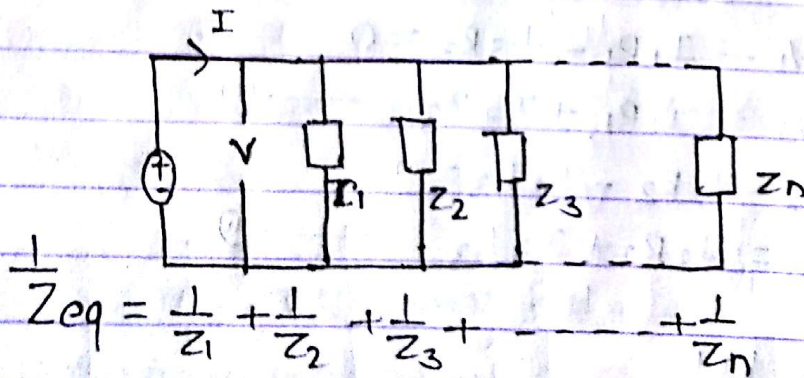


$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_n}$$

current divide rule:  $I_j = \frac{Z_{eq}}{Z_j} \times I$


for 2 elements,  $I_j = \frac{Z_2}{Z_1 + Z_2} \times I$

$$I_j = \frac{Z_2}{Z_1 + Z_2} \times I$$

Element	impedence	Series	Parallel
General	$Z$	$Z_{eq} = \sum Z_i$	$\frac{1}{Z_{eq}} = \sum \frac{1}{Z_i}$
Resistor	$R$	$R_{eq} = \sum R_i$	$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$
Capacitor	$C = \frac{1}{j\omega C}$	$\frac{1}{C_{eq}} = \sum \frac{1}{C_i}$	$C_{eq} = \sum C_i$
Inductor	$L = j\omega L$	$L_{eq} = \sum L_i$	$\frac{1}{L_{eq}} = \sum \frac{1}{L_i}$

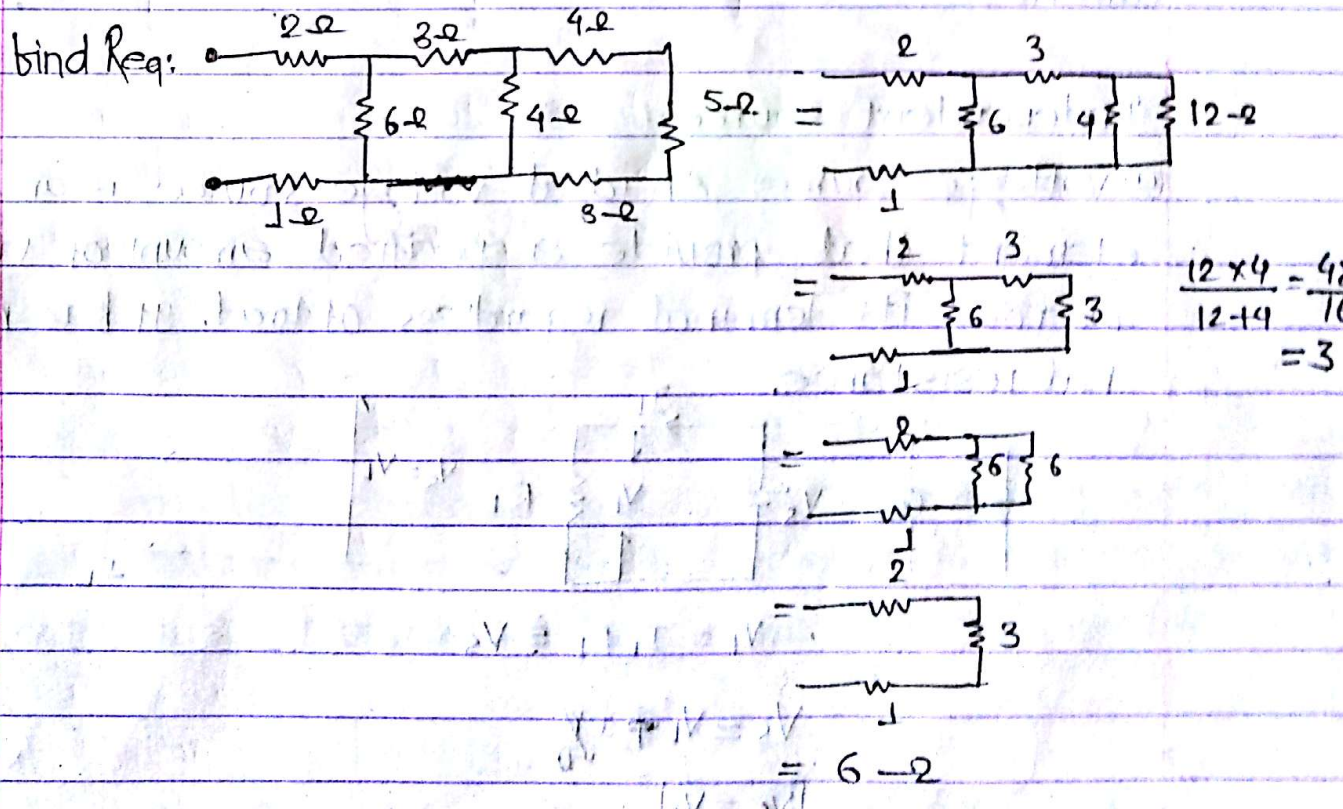

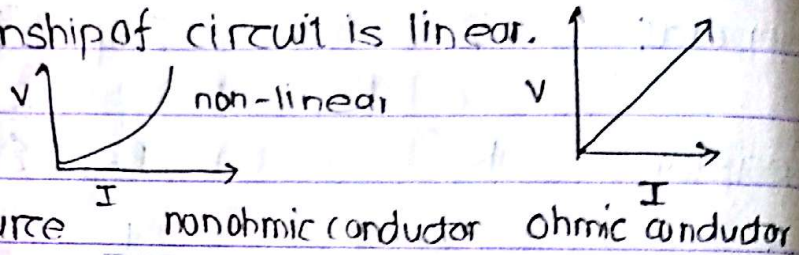① Linearity :- It is a behaviour of circuit in which the input and output relationship of circuit is linear.



② Signal source.

Ⓐ dependent signal source

Ⓑ independent signal


Also it can be classified as

→ voltage source

→ current "

Independent source:-

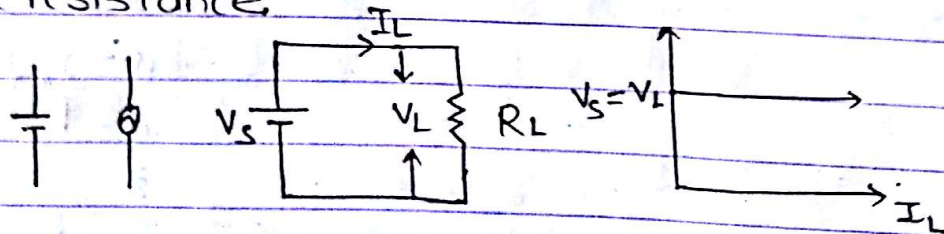Ⓐ voltage source: An ideal voltage source is an active element that provide a specified amount of voltage across its terminal regardless of load, it has no internal resistance.




$$V_L = I_L R_L = V_S$$

$$V_S = V_L + I \cdot 0$$

$$V_S = V_L$$

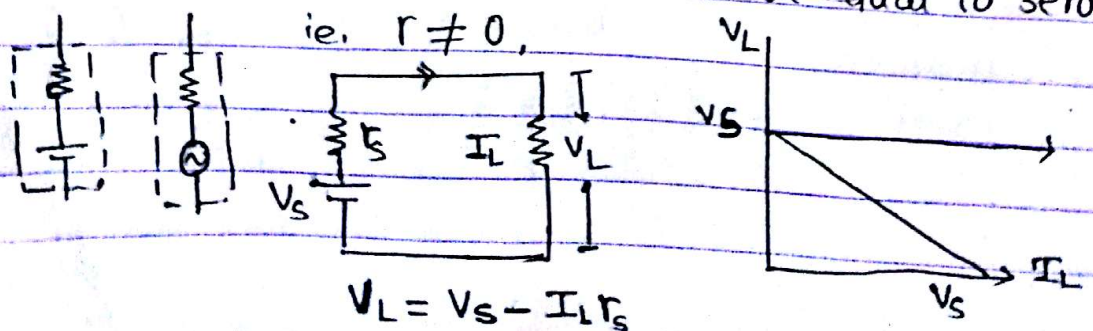in practical case, internal resistance not equal to zero




$$V_L = V_S - I_L r$$


### Independent source
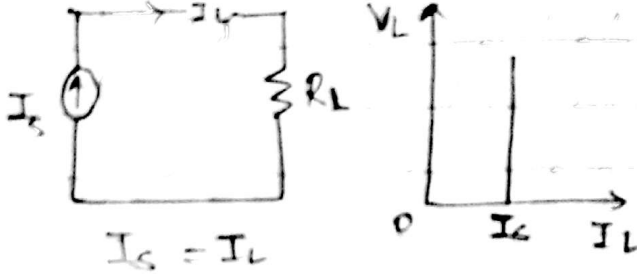
#### ① current source

An ideal current source has infinite internal resistance




In real practise,  $R_{in} \neq \infty$

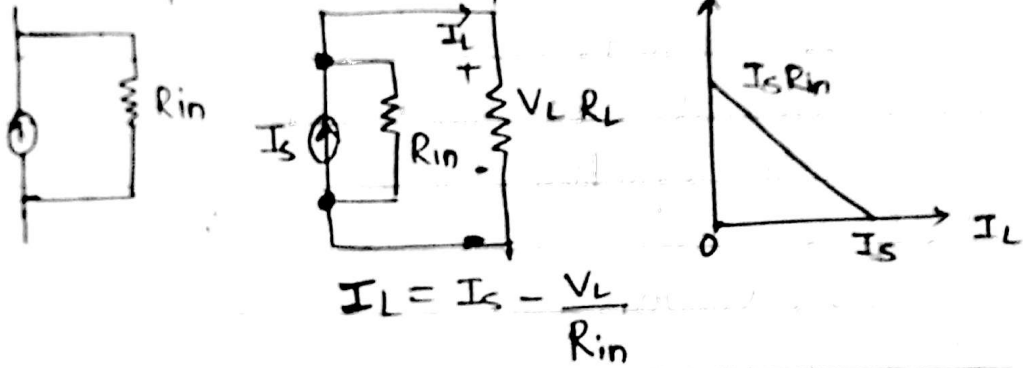
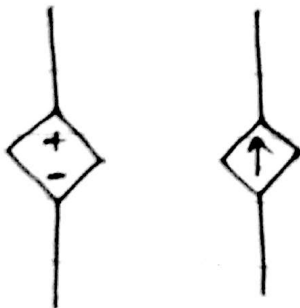
#### 1.2.2 Controlled source or dependent source

An ideal, dependent or controlled source is <sup>to</sup> four terminal device which output depends on input. dependent sources are usually represented by diamond shape symbol.



- ① voltage dependent voltage source : (VDVS)
- ② voltage dependent current source (VDCS)
- ③ current dependent voltage source (CDVS)
- ④ current dependent current source (CDCS)

① VDVS


$V_2 \propto V_1$        $V_2 \rightarrow$  output,  $V_1 =$  input

or,  $V_2 = \mu V_1$

or,  $\mu = \frac{V_2}{V_1}$  (voltage gain)

$\mu$  is unit less and expressed in dB

$\mu_{dB} = 20 \log(\mu)$

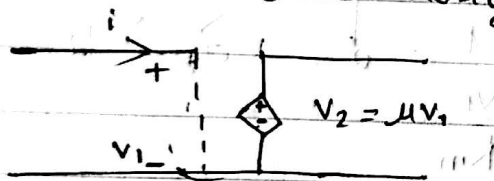


② VDCS

①  $i_2 \propto V_1$

$I_2 = g_m V_1$

$\therefore g_m = \frac{I_2}{V_1}$  mutual conductance / transconductance

Its unit is Siemens

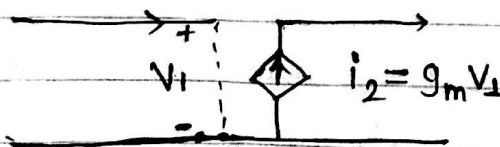


③ CDVS:

$$V_2 \propto I_1$$

$$V_2 = r_m I_1$$

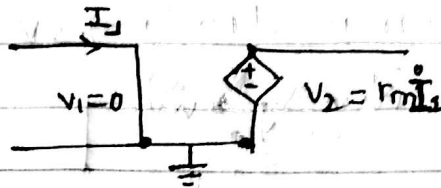$r_m \rightarrow$  mutual resistance or transresistance  
unit  $\Omega$




④ CDCS :-

$$I_2 \propto I_1$$

$$\therefore \frac{I_2}{I_1} = \beta$$

Where  $\beta$  is current gain.

$$\beta_{dB} = 20 \log(\beta)$$

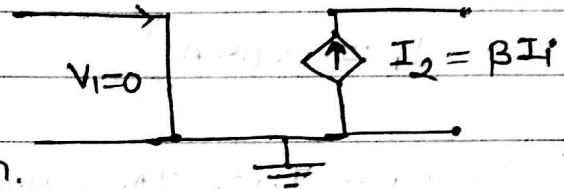


(1.3) Network Theorem:

① Superposition theorem:- In a linear network with multiple source, the current in any branch is the sum of current which would flow in that branch due to its source acting alone with all other voltage source replaced by short circuit and current source by open circuit.


eg: find the current flowing through  $30\text{-}\Omega$  resistor by using superposition theorem.

Voltage source short circuit

open circuit current

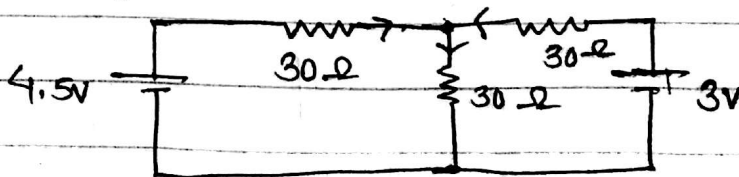

① Case I: Current due to 4.5V

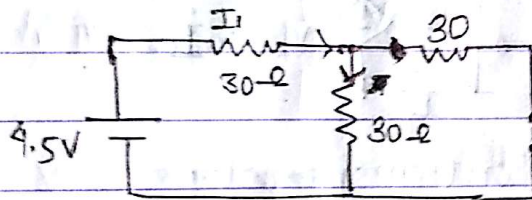


$$R_{eq} = 45 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{4.5}{45} = 0.1 \text{ A}$$

in branch

$$I_1 = 0.05 \text{ A}$$

Case 2: Current due to 3V

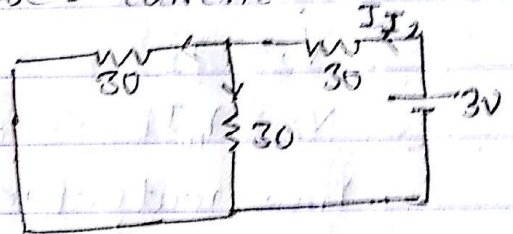

$$R_{eq} = 45 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{3}{45} = 0.067 \text{ A}$$

branch.

$$I_2 = 0.03 \text{ A}$$

$$\therefore I_T = I_1 + I_2 = 0.05 + 0.03 = 0.08 \text{ A}$$


through  
30- $\Omega$

### Introduction to filter:

Filter is a network that transmit signal within a given frequency range, attenuates <sup>(bypass)</sup> all the remaining signal.

A filter posses one pass band (a band of frequencies in which the attenuation is theoretically zero.

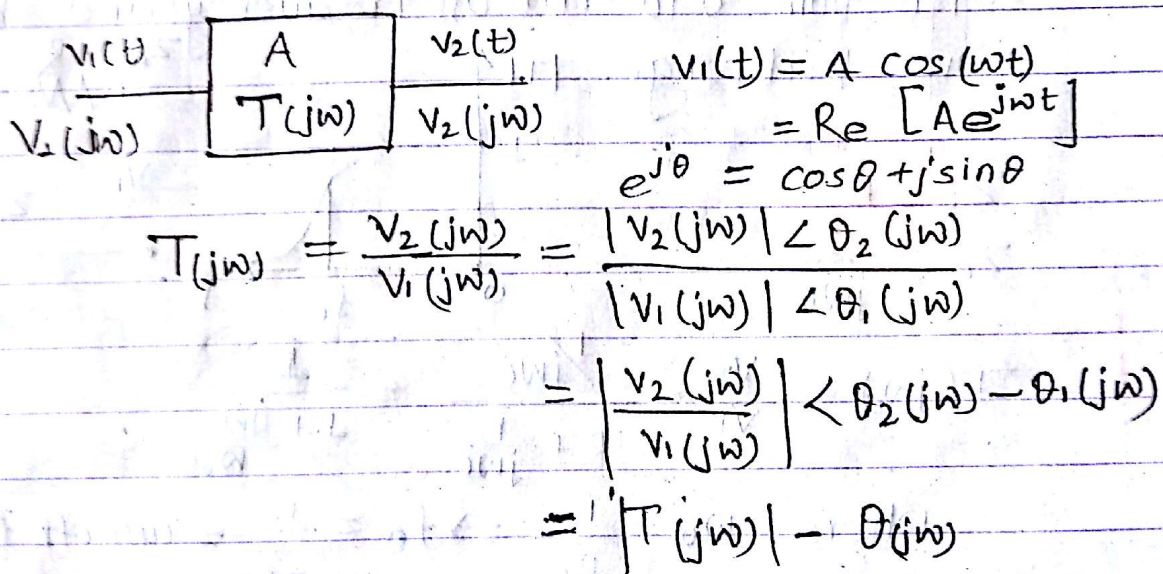- \* Stopband: The band of frequency in which attenuation is theoretically infinite.
- \* The frequency that separate various pass band and stop band is called cut off frequency
- \* Transfer function and frequency response  
Basically, filter circuits are analyzed in frequency domain. freq. response is a steady state response of any circuit while subjected to a sinusoidal input.



- \* Plot of Transfer function vs  $f \Rightarrow$  freq<sup>n</sup> response.
- \* Plot of magnitude of  $T(j\omega)$  vs  $f \rightarrow$  magnitude response.
- \* Plot of angle of  $T(j\omega)$  vs  $f \rightarrow$  phase response.




$$Z_c = \frac{1}{j\omega C} \propto \frac{1}{f}$$

$$V_2 \approx V_1, \quad f=0, \quad X_c \rightarrow \infty \Rightarrow V_2 = V_1$$

$$\textcircled{ii} \quad f = f_c \Rightarrow X_c = R, \Rightarrow V_2 = 0.707 V_1$$

$$\textcircled{iii} \quad f = \infty \Rightarrow X_c = 0 \Rightarrow V_2 = 0$$

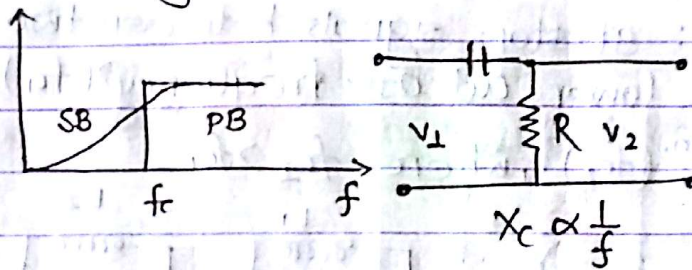\* High Pass filter : A high pass filter passes signals above a cut off frequency and block the lower frequency.



$$X_c = R$$

$$\frac{1}{2\pi f_c C} = R$$

$$\therefore f_c = \frac{1}{2\pi RC}$$

$$f=0, \quad X_c \rightarrow \infty, \quad V_2 = 0$$

$$f = f_c, \quad X_c = R, \Rightarrow V_2 = 0.707 V_1$$


$$f \Rightarrow \infty, \quad X_c = 0, \quad V_2 = V_1$$

$$T(j\omega) = \frac{V_2}{V_1} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 - j/\omega RC} = \frac{1}{1 - j \frac{\omega_0}{\omega}}$$

$$\text{Where, } \omega_0 = \frac{1}{RC} \Rightarrow f_c = \frac{1}{2\pi RC} = \text{cut off freq.}$$



$$|T(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_0}{\omega}\right)^2}} \quad \text{ie, } \angle \theta = \theta + \tan^{-1}(\omega_0/\omega)$$

$\omega$	$ T(j\omega) $
0	0
$\omega_0$	0.707
$\infty$	1

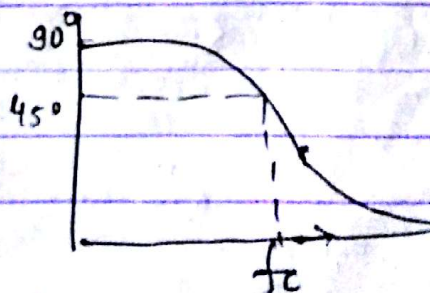



\* Band pass filter:

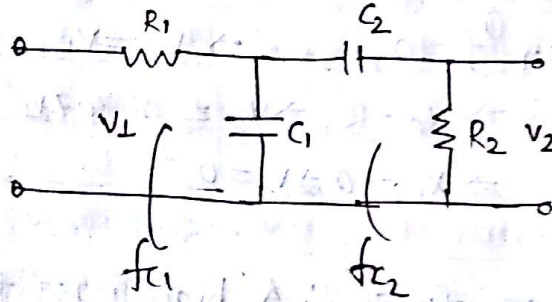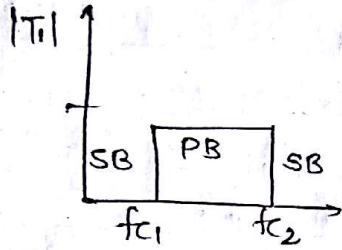It passes signals bet<sup>n</sup> two cutoff frequency known as lower cut off freq<sup>n</sup> ( $f_{c1}$ ) and higher cut off freq. ( $f_{c2}$ ), where  $f_{c2} > f_{c1}$ .



$$f_{c1} = \frac{1}{2\pi R_1 C} \quad f_{c2} = \frac{1}{2\pi R_2 C}$$

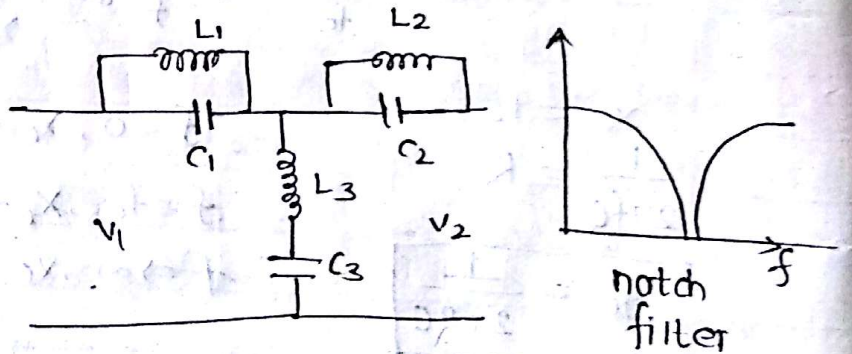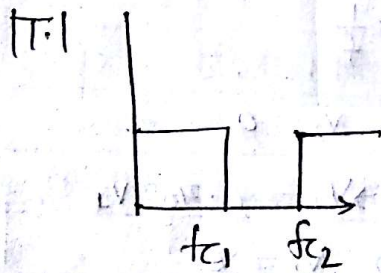\* Band ~~pass~~ <sup>stop</sup> filter: It stops signals between two cutoff frequency known as lower cut off frequency ( $f_{c1}$ ) and higher cut off freq<sup>n</sup> ( $f_{c2}$ ), where  $f_{c2} > f_{c1}$ .




Remaining part:
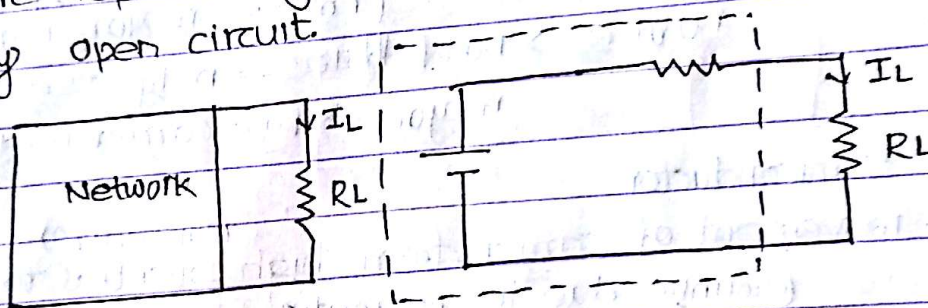
### Thevenin's Theorem.

Any circuit can be replaced by a series combination of ideal voltage source  $V_{th}$  and a resistance  $R_{th}$ .  
 Where,  $V_{th}$  is known as Thevenin's voltage.  
 It is a open circuit voltage across load terminal equivalent.


$R_{th}$ : Thevenin resistance: It is the total resistance at the open circuited terminal when all voltage source are replaced by short circuit and all current source by open circuit.



Current flowing through  $R_L \Rightarrow I_L = \frac{V_{th}}{R_L + R_{th}}$


Eg:

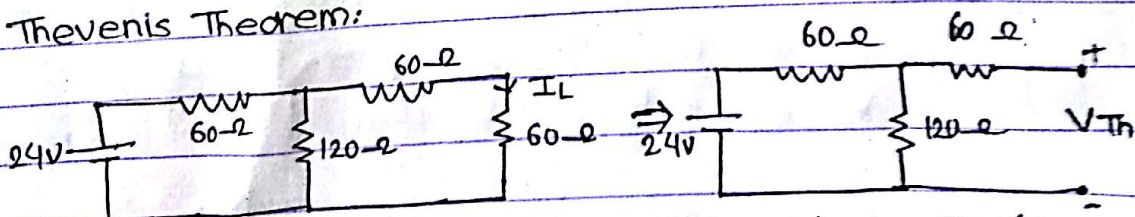find current through  $60\Omega$  by Thevenin's Theorem:



$$\therefore V_{th} = \frac{24 \times 60}{60 + 120} = 16V$$

for Resistance ( $R_{th}$ )

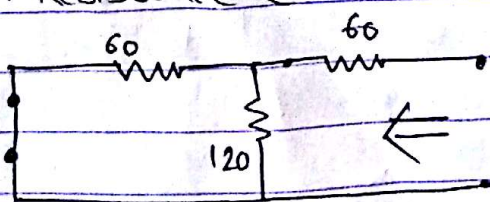

$$R_{th} = 60 \parallel 120 + 60 = \frac{60 \times 120}{60 + 120} + 60$$

$$\therefore R_{th} = 100\Omega$$


$$\therefore I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{16}{100 + 60} = 0.1 A$$

(b) Norton's Theorem:


Any circuit can be replaced by parallel combination of current source,  $I_n$  and resistance,  $R_n$ .

$I_n$  → current passing through selected pair of terminal with short circuited.

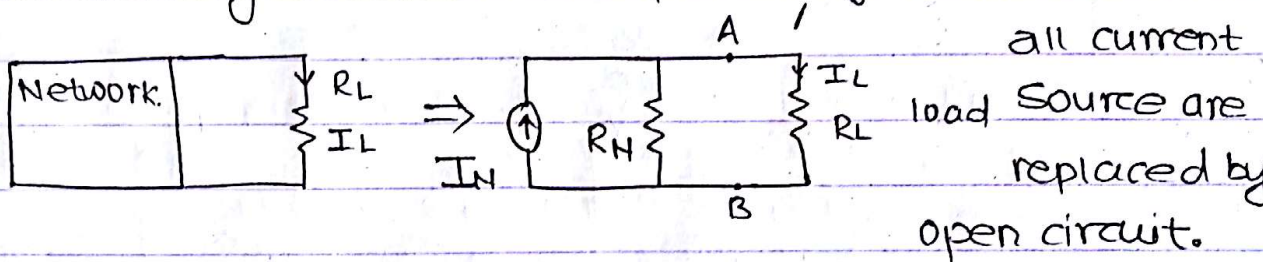$R_n$  → It is a total resistance at the terminal AB, when all voltage source are replaced by short circuit and



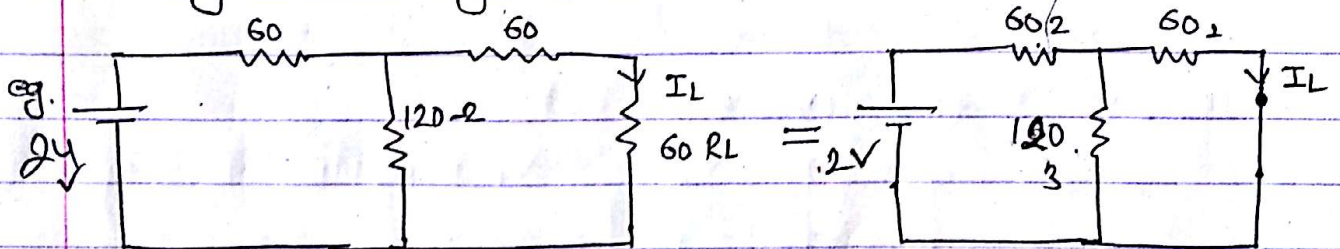current source is a component whose task is to provide a constant amount of current outputting as much or as little voltage necessary to maintain constant current.



$I_L$  can be calculated as

$$I_L = \frac{I_n \cdot R_n}{(R_n + R_L)}$$

$$= \frac{R_n}{(R_n + R_L)} \times I_n$$


① remove load Resistor from Original circuit and short circuit.

$$R_{eq} = (60 \parallel 120 + 60)$$

$$= \frac{60 \times 120}{60 + 120} + 60$$

$$\therefore R_n = 100 \Omega$$

for  $I_n$

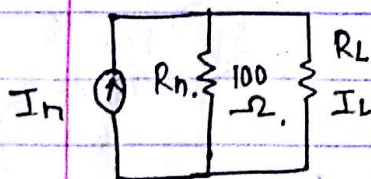

$$I_n = \frac{120 \times 0.24}{120 + 60} = 0.16 \text{ V}$$

$$I_L = \frac{0.16 \times 100}{100 + 60}$$


$$= 0.1 \text{ A}$$

$$I_t = \frac{V}{R} = \frac{24}{100} = 0.24 \text{ A}$$
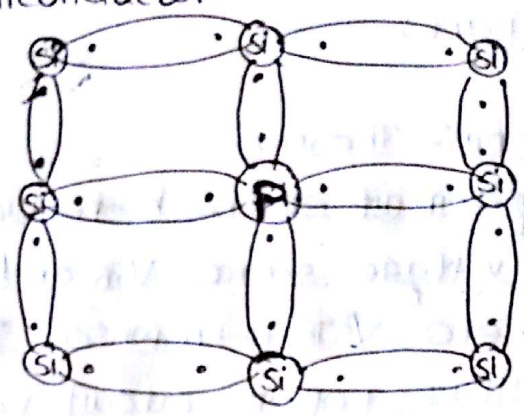
# C:2 Basic concept of semiconductor

Si } valence electron 4  
Ge }

at 0 K, pure semiconductor act as insulator.



Pure semiconductor or Intrinsic  
Impure or Extrinsic

majority charge carriers  
minority " "

adding impurities - doping

- ① Tri-valent (B) no of hole > no of electron. P type semiconductor (hole is major charge carrier)
- ② Penta valent (P) no of e<sup>-</sup> > no of hole → n type semiconductor major charge carrier is electron.



## ① Conduction in semiconductor

- Ⓐ Diffusion: - movement of carriers from high potential to low potential (concentr<sup>n</sup>)  
(mainly due to majority charge carriers)
- Ⓑ Drift: - in presence of electric field; for same material minority charge carriers moves,

Semiconductor:

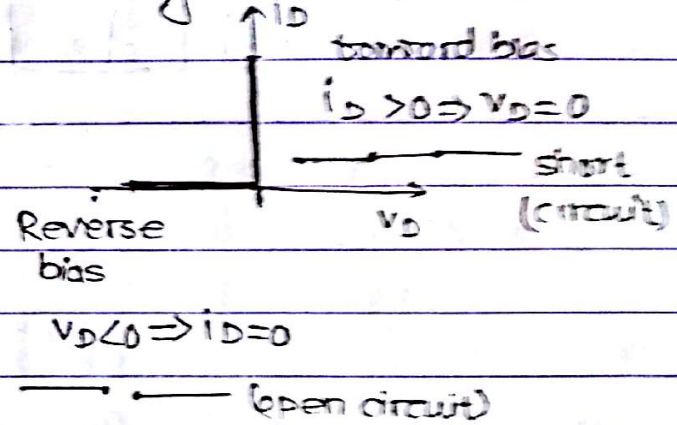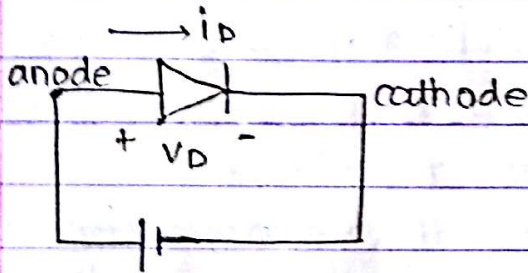
Q.2 Diode :-

Ideal diode :- Ideal diode a fictitious two terminal element that conducts current only in one direction




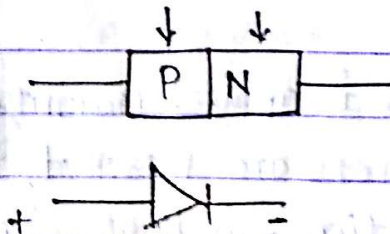Q.3: Semiconductor diode:


(PN) Junction diode are real diode that can be built. A PN Junction is formed by introducing donor impurities in one side and acceptor impurities into other side of the single crystal of diode.



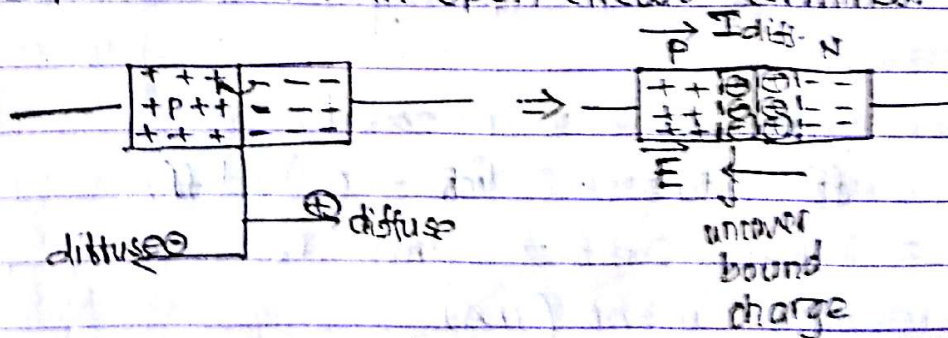
Q.3.1: The PN Junction with open circuit terminal:



(a) Forward bias :-

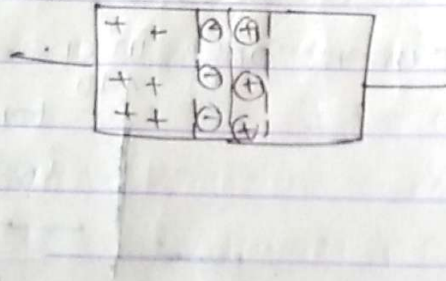

Reversed bias: ( $V$  applied  $< 0$ )

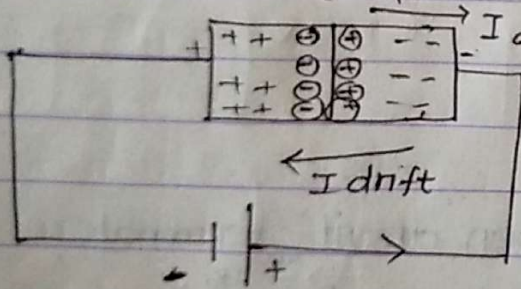

$V_r$  as applied - Majority charge carriers are repelled from Junction - width of depletion region increases and

barrier potential also increased.

$I_{diff}$  reduces, ( $I_{diff} \rightarrow 0$ ) (diff)


$$\therefore I = I_{drift} - I_{diff} = I_{drift} = I_s$$

$I =$  reverse current ( $\mu A$ )

When reverse bias voltage is increased <sup>but</sup> net electric field increase, but drift current doesn't change <sup>because</sup> ~~but~~ no of carriers drifting across the junction is small. So the current that exists under reversed biased condition is called reversed saturation current ( $I_s$ ).

$I_s$  is doubled its value for every  $5^\circ$  centigrade rise in temperature. The typical value range from  $10^{-8}$  to  $10^{-15}$  A.

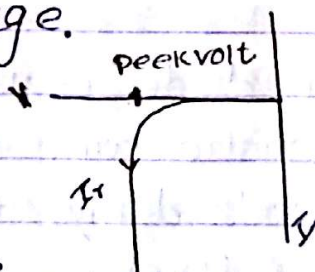When the magnitude of reverse voltage <sup>( $V_r$ )</sup> exceed the threshold value called breakdown voltage, the reverse current increase rapidly. ~~Then~~ <sup>with small voltage</sup> ~~th~~ <sup>increases</sup> then diode is said to be breakdown. The max. reverse bias voltage that can be applied before entering the breakdown voltage is known as peak reverse voltage or peak inverse voltage.



### Break Down Method:

<p>① Avalanche Breakdown:          Occurs in lightly doped PN Junction</p>	<p>Zener Breakdown          occurs in heavily doped PN-Junction.</p>
<p>② Breakdown voltage is greater than 5V</p>	<p>Zener voltage is less than 5V</p>
<p>③ Minority carriers are generated by collision.</p>	<p>Minority charge <sup>carriers</sup> are generated by Electric field in depletion region.</p>

Voltage current relationship of diode:

diode current:

$$i_D = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

Where,  $I_D$  = current through diode

$V_D$  → voltage across diode

$I_s$  → saturation current

$V_T$  → Thermal voltage =  $\frac{KT}{q}$

Where,  $K$  → Boltzmann constant)  $1.38 \times 10^{-23}$

$T$  - absolute temperature.

$q$  → electron charge

$n$  → Identity factor or material scale factor, it has value bet<sup>n</sup> 1, and 2, assume  $n=1$ , unless otherwise specified.

$V_T \approx 25$  mV (at room temp)

### # Semiconductor diode characteristic:


The characteristic curve shows the voltage . ampere behaviour of diode during toward and reversed bias condition,  $i_D = f(V_D)$

#### (A) Forward Bias

In forward bias region significant current flow, i.e., ( $V_D > 0$ ) ( $I_D \gg I_s$ )

So,  $i_D = I_s \left[ e^{\frac{V_D}{nV_T}} \right]$

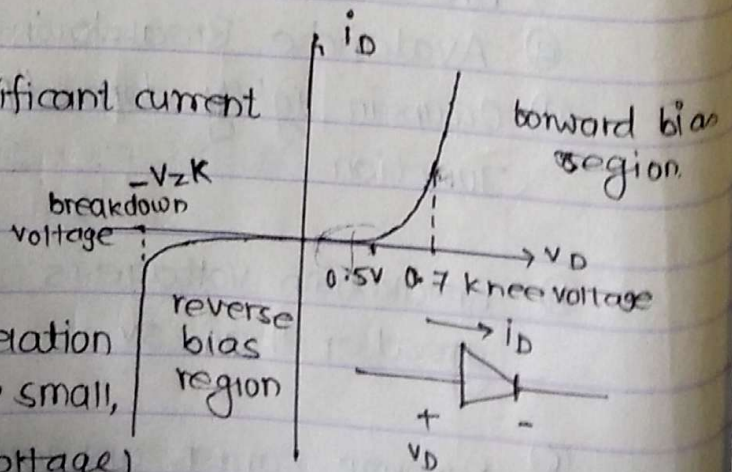
due to exponential I-v relationship current is negligibly small, for,  $V_D < 0.5$  V (cutting voltage)



after the diode voltage reaches the Threshold voltage, the diode current rises sharply for small increment of diode voltage.

for fully conducting diode,  
 $0.6 < V_D < 0.8V$

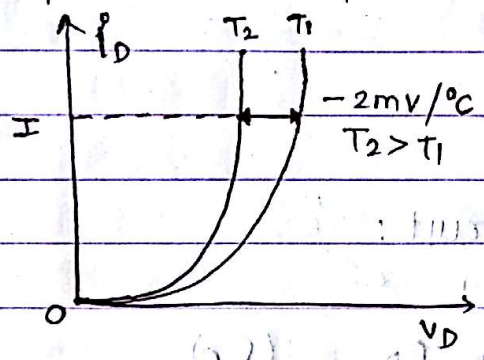
\* Temperature Dependence: at given constant diode current



The diode voltage decreases approximate  $-2mV/^\circ C$  where as current approximate with increase temperature.

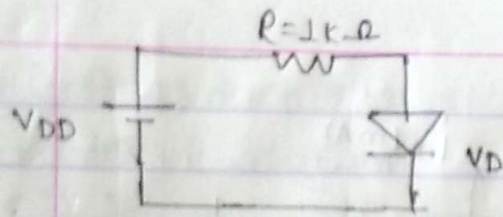(B) Reverse bias Region: ( $V_D < 0$ ) / ( $i_D \approx -I_S$ ), Ideally, the reverse current is constant and independent of reverse bias voltage so it is called saturation current. However, practically reverse current is much larger than  $I_S$  due to leakage effect and also increases somewhat increase in reverse bias voltage.

Temperature dependence: Reverse current double for every  $10^\circ C$  rise in temperature



decay volt = 0.1V

Now,  $I_1 = 1mA$

$V_1 = 0.7V$

$$V_{D2} - V_{D1} = 2.3nV_T \log\left(\frac{I_{D2}}{I_{D1}}\right)$$

or,  $0.1 = 2.3nV_T \log(10)$

or,  $0.1 = 2.3nV_T \times 1$

$\therefore 2.3nV_T = 0.1$

For,

ite. 1:  $I_1 = \frac{5 - 0.7}{1 \times 10^3} = 4.3 mA$

$$V_2 = V_1 + 0.1 \log\left(\frac{I_2}{I_1}\right)$$

$= 0.763V$

ite. 2:  $I_3 = \frac{5 - 0.763}{1 \times 10^3} (= 4.237 mA)$

$$V_3 = V_2 + 0.1 \log\left(\frac{I_{D2}}{I_{D1}}\right)$$
$$= 0.763 + 0.1 \times \log\left(\frac{0.4237}{4.3}\right)$$

$V_3 = 0.762V$

$V_3 - V_2 = 0.762 - 0.763 = -0.001V$

$V_D = 0.762V$

$I_D = 4.237 mA$

2.5 Modeling The diode:

Modeling is a representation of device with equivalent equipment element such as inductor, capacitor, voltage and current source. The equivalent circuit that doesn't lose functional behaviour is called modeling of diode. The model of diode for DC and AC is different.

DC Model: Large signal model:


(a) ideal diode model:

most simplified model

used when supply voltage is much higher than diode voltage

Mathematically. Diode on :  $I_D > 0, V_D = 0$  [short circuit]  
 diode off :  $V_D < 0, I_D = 0$  [open circuit]

forward bias - short circuit.

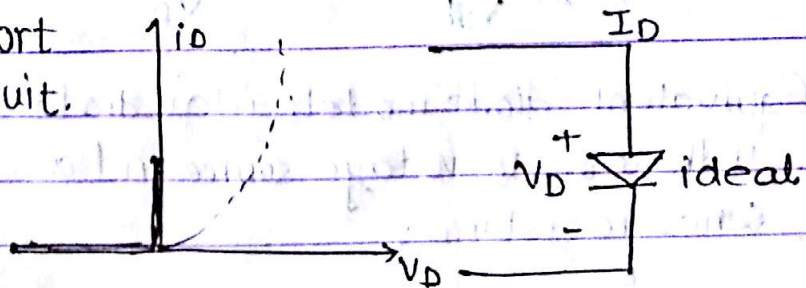



(b) Constant voltage drop model:


Mostly used in the initial design and analysis phase. It is assumed that the forward conducting diode exhibit a constant voltage drop  $V_D$  (usually 0.7V)

Mathematically:


Diode on  $I_D > 0, V_D = 0.7V$

diode off  $V_D < 0.7V, I_D = 0$

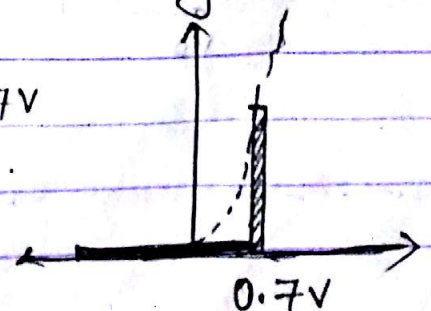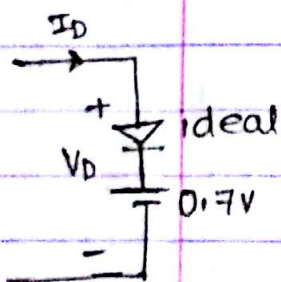

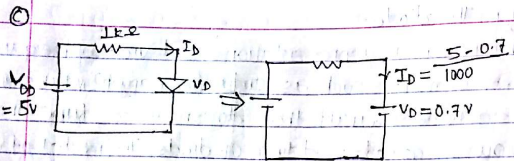


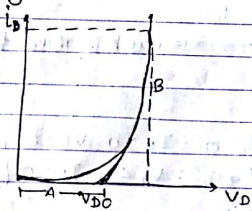\* Piecewise linear model:  
battery plus resistance model.




mathematically,  
diode on:  $I_D = \frac{V_{DD} - V_{D0}}{r_D}$   
 $V_D \geq V_{D0}$   
diode off:  $V_D \leq V_{D0}, I_D = 0$   
Where,  $r_D = \frac{\Delta V_D}{\Delta I_D}$  = inverse slope of line B  
= average or resistance or forward bias resistance

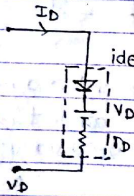\* Equivalent diode model: ideal diode with a 0.7V voltage source and a series resistance.




- @ let,  $V_{DD} = 5V, R = 1k\Omega$ , calculate  $I_D$  and  $V_D$  by
- ① ideal diode voltage model
  - ② constant voltage "
  - ③ Piecewise linear model


ideal model concept

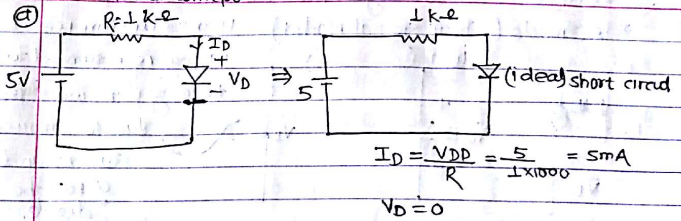

② constant voltage drop:


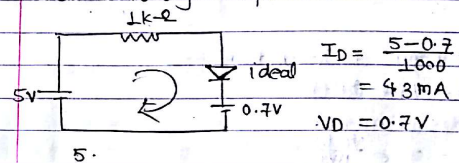


③ Piecewise linear model:

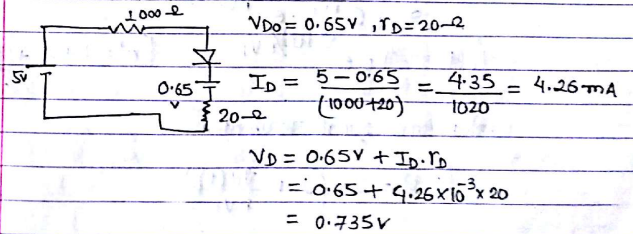

Small signal  $v_d(t)$  is superimposed on  $V_D$  due to this dc voltage the operating point of diode is  $(V_D, I_D)$ . Now, if we consider the effect of superimposed small signal  $v_d(t)$  on diode, voltage and current variation are shown.

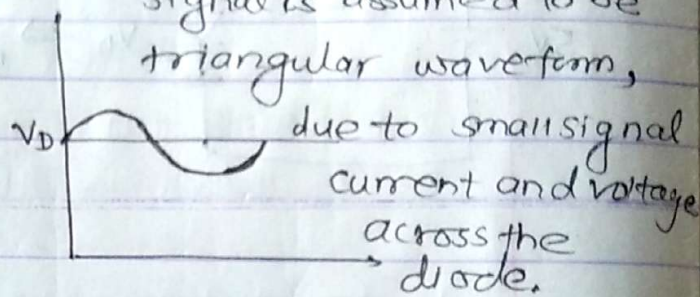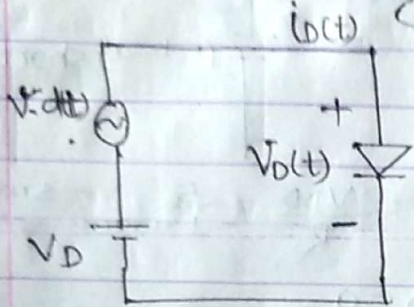\* AC mode (Small Signal Model) Here superimposed small signal is assumed to be triangular waveform,



Assumption: signal amplitude is sufficiently small ( $v_d \leq 10mV$ )

Total instantaneous diode voltage

$$v_D(t) = V_D + v_d(t)$$

instantaneous current:

$$i_D(t) = I_S e^{\frac{v_D(t)}{nV_T}}$$

$$= I_S e^{\frac{V_D + v_d(t)}{nV_T}}$$

$$= I_S e^{\frac{V_D}{nV_T}} \cdot e^{\frac{v_d(t)}{nV_T}}$$

$$i_D(t) = I_D e^{v_d(t)/nV_T}$$

$$\left[ e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots \right]$$

neglect

under small signal assumption,

$$i_D(t) = I_D \left( 1 + \frac{v_d(t)}{nV_T} \right)$$

$$= I_D + \frac{I_D v_d(t)}{nV_T}$$


$$\therefore i_D(t) = I_D + i_d$$

$$\therefore i_d = \frac{I_D v_d(t)}{nV_T} = \frac{v_d(t)}{r_d}$$

~~$r_d = \frac{V_d}{I_d}$~~   
 ~~$r_d = \frac{V_d}{I_s}$~~

$\therefore r_d = \frac{nV_T}{I_D}$  known as diode small signal resistance or dynamic resistance

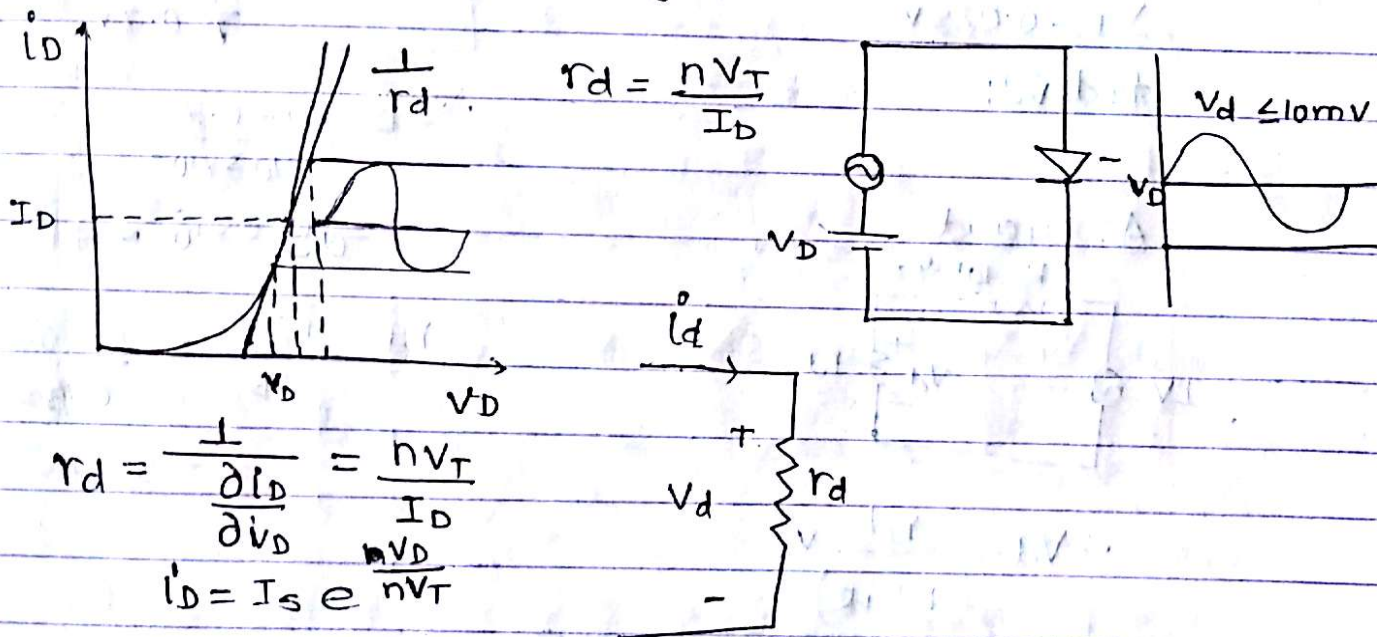
Equivalent circuit model: dynamic resistance



$$r_d = \frac{1}{\frac{\partial I_D}{\partial V_D}} = \frac{nV_T}{I_D}$$

$$I_D = I_s e^{\frac{qV_D}{nV_T}}$$



Small signal high frequency model

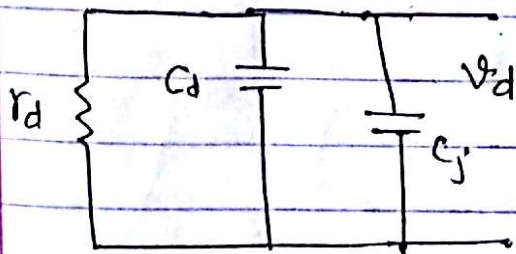

$C_d$  → diffusion capacitance


$C_j$  = depletion capacitance

Junction capacitance

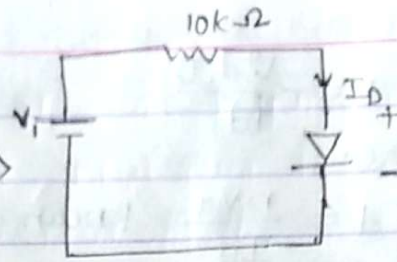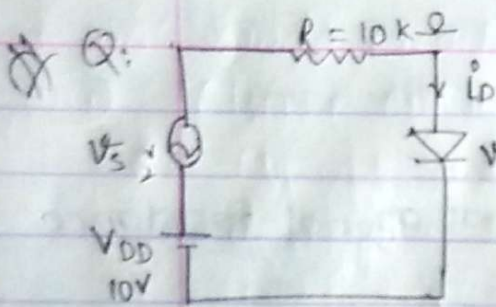

Equivalent DC circuit:

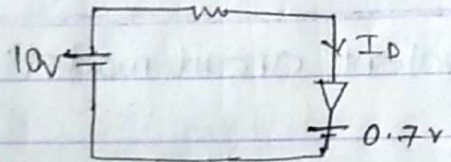
$V_D = 0.7V$  at  $1mA$   
 diode  $n = 2$   
 $V_T = 0.025V$   
 find  $v_D$ ;



$$I_D = \frac{10 - 0.7}{10^3 \times 10}$$

$$= 0.93 \times 10^{-3} \text{ mA}$$

AC circuit

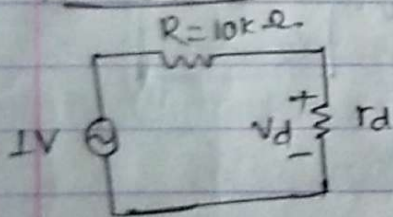


$$r_d = \frac{nV_T}{I_D} = \frac{2 \times 0.025}{0.93 \times 10^{-3}}$$

$$= 53.8 \Omega$$

$$\therefore V_d = \frac{r_d}{r_d + R} v_s$$

$$= \frac{53.8}{(53.8 + 10 \times 10^3)}$$


$$= 5.3 \text{ mV}$$

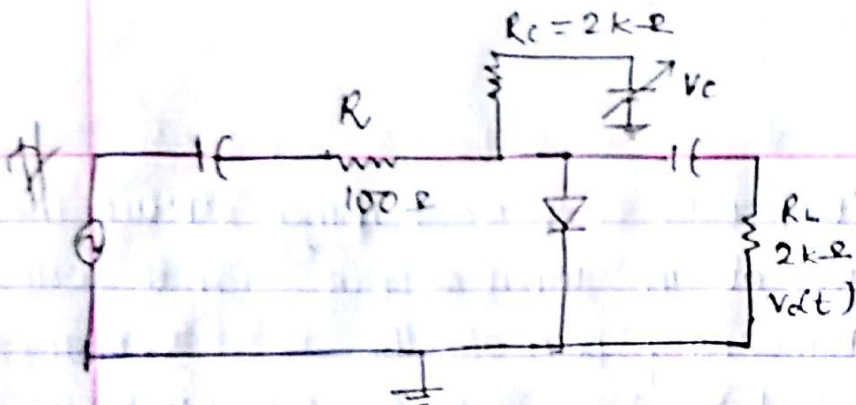

$n = 1$  at  $300K$   
 $V_T = 0.026V$   
 $V_D = 0.6V$   
 $V_C = 1.6V$   
 $V_C = 10.6V$

$A_V = \frac{V_o}{V_{in}}$

DC circuit


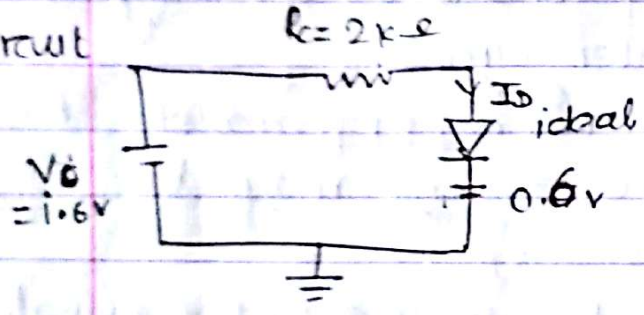


$$I_D = \frac{1.6 - 0.6}{2 \times 1000}$$

$$= 0.5 mA$$

$$r_d = \frac{n V_T}{I_D} = 52 \Omega$$

AC circuit

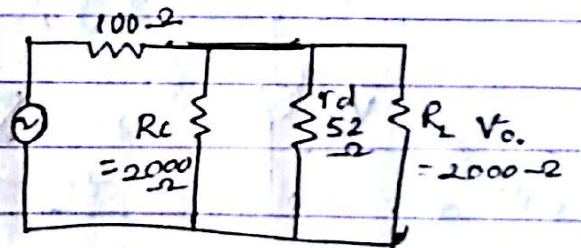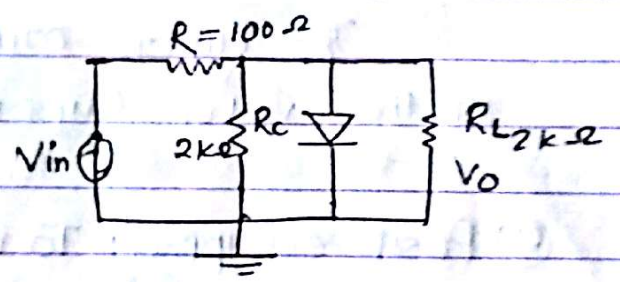

$$R_{eq} = (2000 // 2000) // 52$$

$$= 1000 + 52$$

$$= 1052 \Omega$$

$$R_p = 49.43 \Omega$$

$$V_o = \frac{R_p}{R_p + R}$$


$$\therefore A_V = \frac{V_o}{V_{in}}$$

2.6 Diode circuit

**(Imp)** Clipper circuit: Clipper is a waveshaping circuit that clip off a portion of an input output signal without destroying the remaining part of the waveform. It is used for signal shaping and to the following circuit. It is also known as limiter circuit.

The clipper could be ~~reverse~~<sup>series</sup> or parallel based on the level of clipping, the clipping may be:

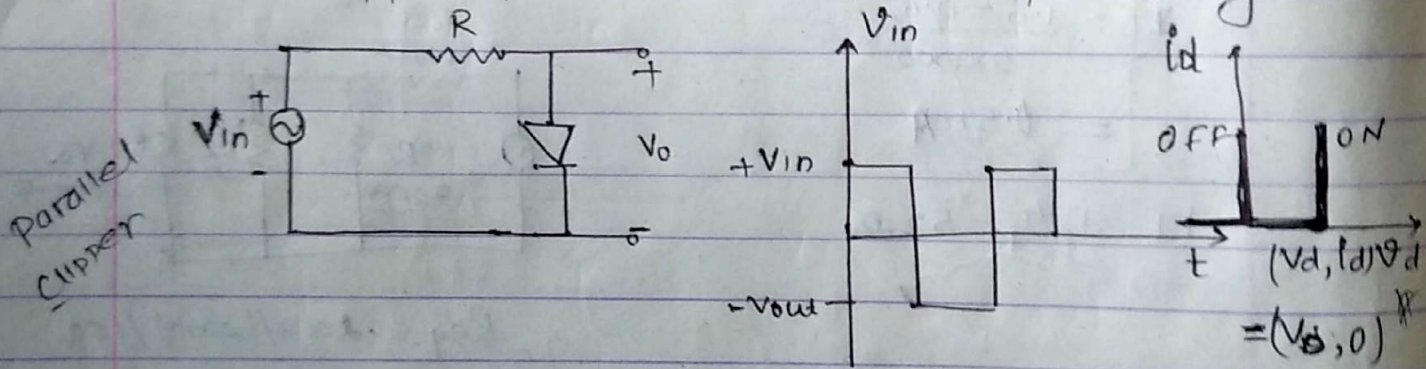① Positive Clipper: To remove the positive part of signal



\* Input output voltage required to turn on diode:  $(0.7, 0)$   
 apply  $i_D = 0, V_D = V_D$  practical (case)


KVL  
 $V_{in} = V_D$

$\therefore V_{in} > V_D$  to turn on the diode.

\* output in both states

when diode is on,  $V_o = V_D$   
 off,  $V_o = V_{in}$

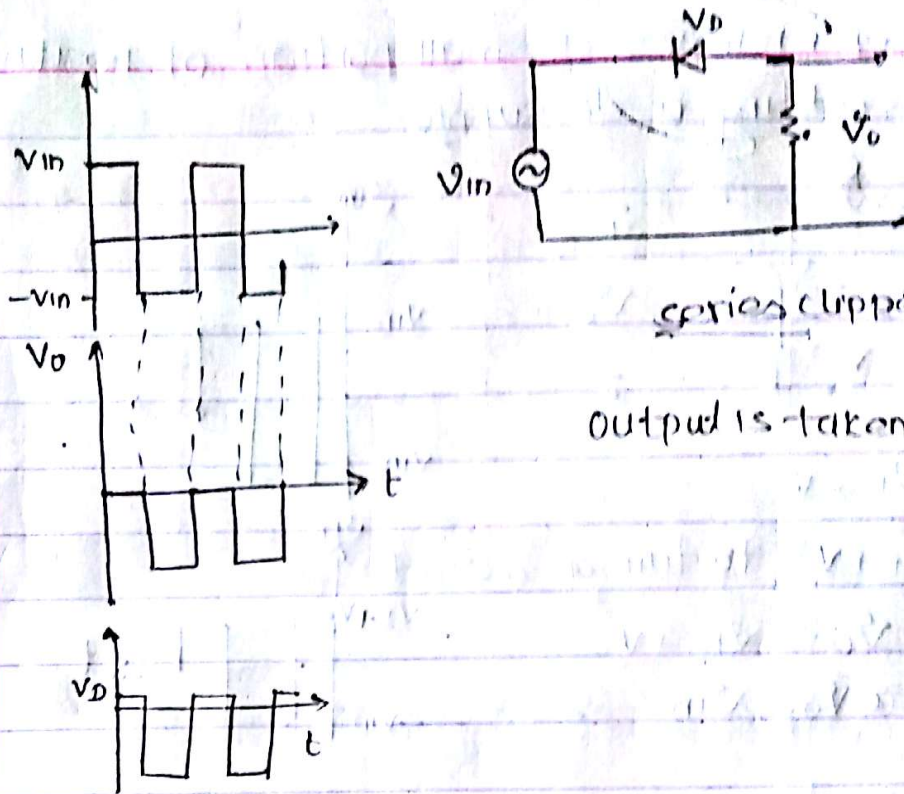
for ideal,  $V_D = 0$ , so,  
 $V_{in} = 0$



series clipper,

output is taken across resistor

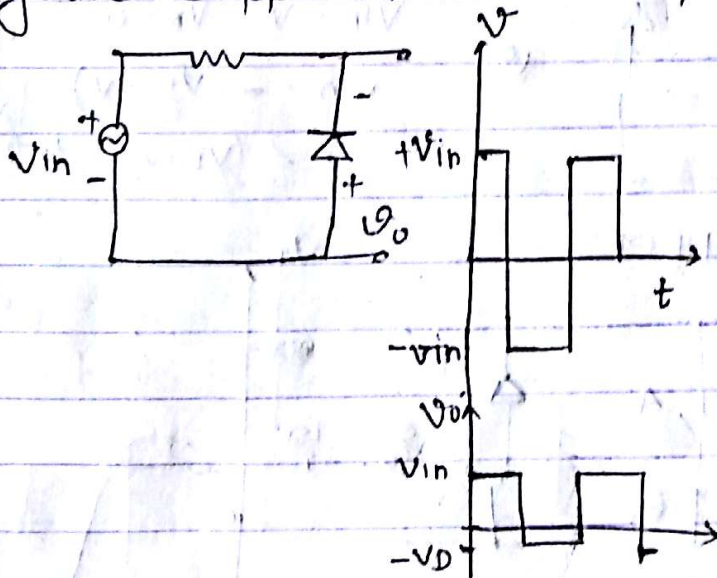ⓑ Negative Clipper: removes -ve part of signal.



applying KVL:



$$V_{in} = -V_D$$

$V_{in} < -V_D$  : to turn on diode

Diode is ON  $\Rightarrow V_o = -V_D$

Off,  $V_o = V_{in}$

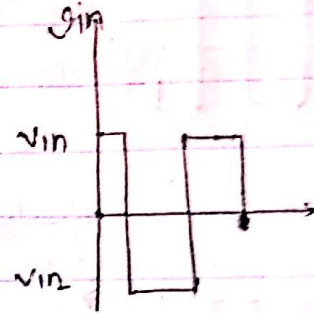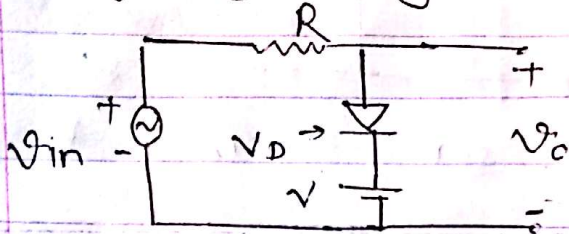(+ve) Biased Clipper: removes a small portion of positive or -ve cycle by adding a dc supply:




$$v_{in} = V_D + V$$


$v_{in} > (V_D + V)$  to turn on a diode

ON  $\Rightarrow v_o = V_D + V$

OFF  $\Rightarrow v_o = v_{in}$

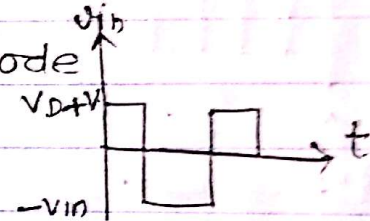

-ve Bias Clipper:

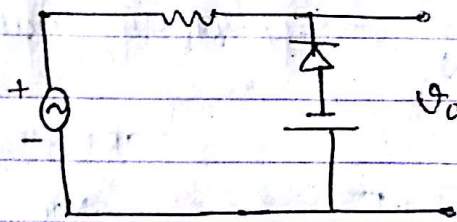



$$v_{in} + V_D + V = 0$$

$$v_{in} = -(V_D + V)$$

$v_{in} < (V_D + V)$  to turn on.

ON  $v_o = -(V_D + V)$   
OFF  $v_o = v_{in}$


(d) Combination Clipper:-

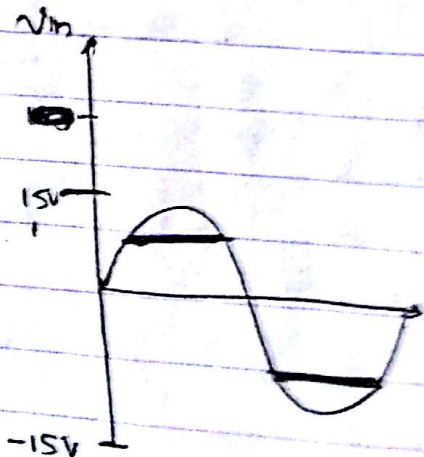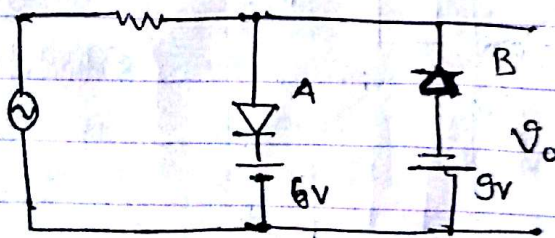

69
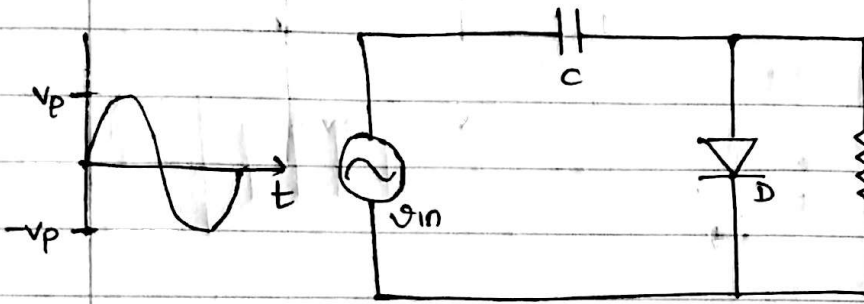
### Clamper circuit:

Clamper circuit is used to add a DC voltage to AC signal so that +ve and -ve peaks are clamped to a specific dc level. It must have a capacitor, diode and resistor.




Following two assumptions are used in clamper circuit

- (i) Capacitor charges quickly
- (ii) discharge is very slow


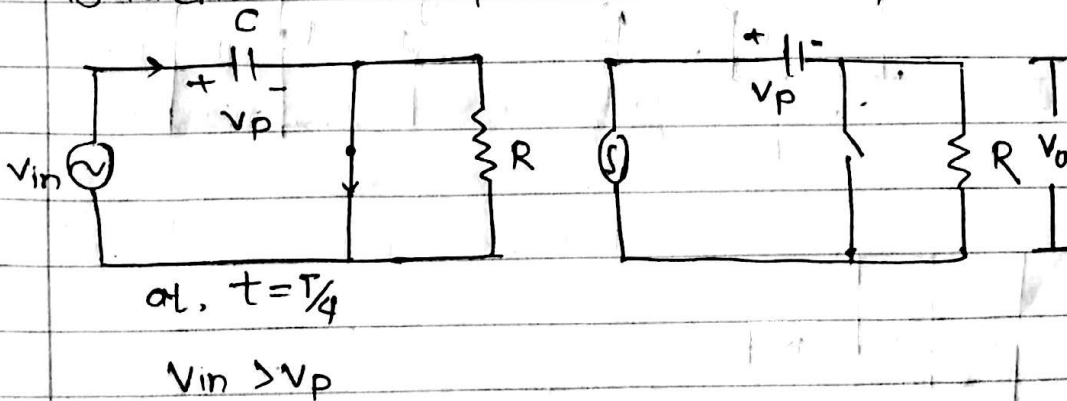
### negative clamper circuit:

On the positive half cycle, the diode turns on, shorting the resistor. The capacitor will charge upto a voltage quickly with the polarity shown. Slightly beyond the +ve peak, the diode turns off. Since the time constant ( $t = RC$ ) is made very large, the capacitor retains the voltage identically.


Since the output as  $V_o = V_{in} - V_p$ , the o/p signal is identical to input and is clamped to  $-V_p$  volts.





Q:

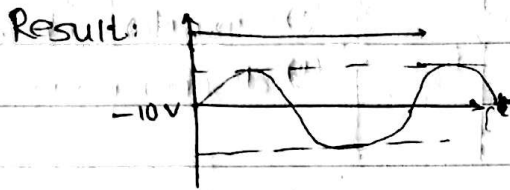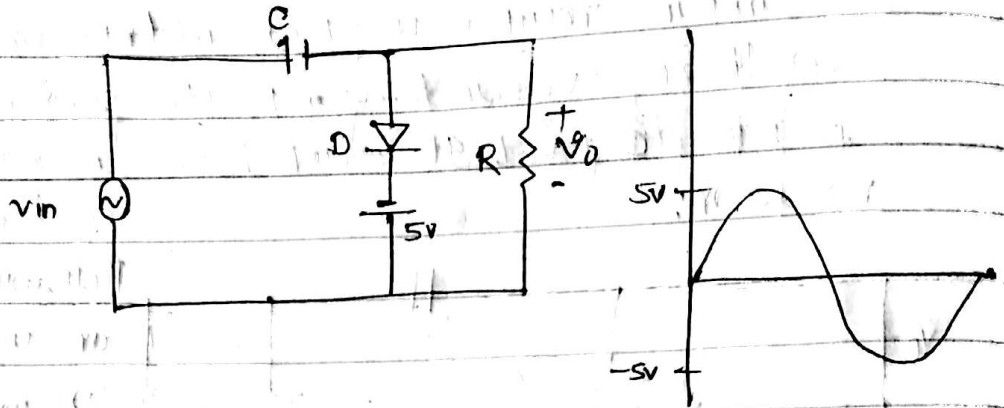

Soln:

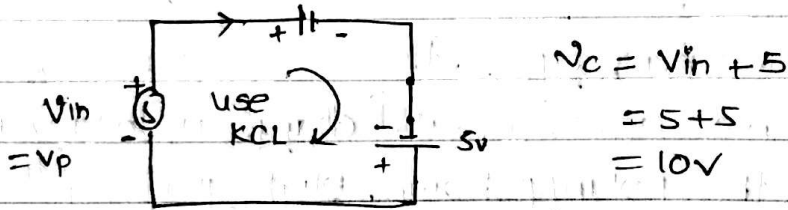



Positive Clamper:

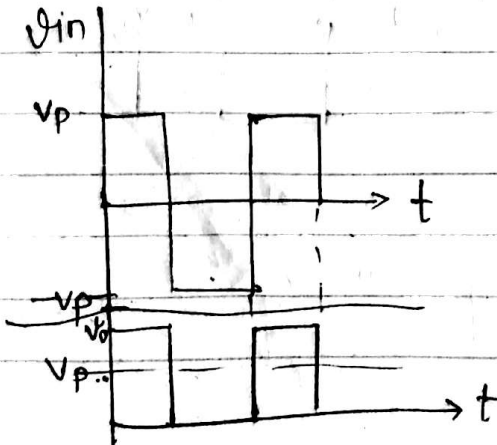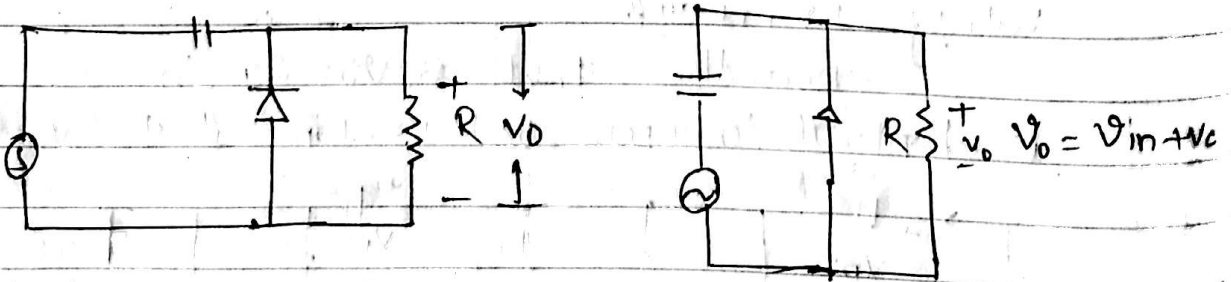

### Special diode:
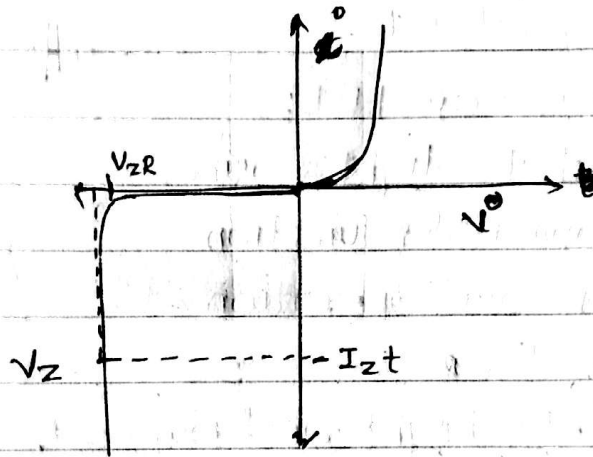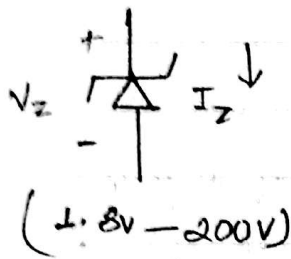
#### ① Zener diode:


Zener diode is designed to operate specially in breakdown region. It is a heavily doped semiconductor diode with smaller reverse break down voltage.



When the diode current is greater than knee current  $I_{zk}$ , the characteristic curve is almost vertical i.e. voltage across diode remains constant independent of reverse current. The property is used to regulate voltage so Zener diode is used as a voltage regulator.
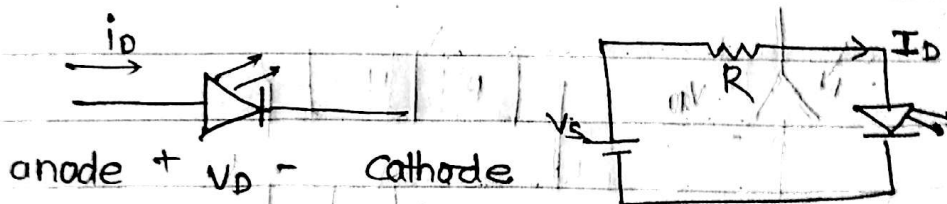
#### 2.7.2 LED: Light Emitting Diode:

LED converts a forward current into light in variety of ~~cross load~~ color: red, green, yellow, orange, infra-red. LED is fabricated by using compound semi-conductor, such as gallium arsenide phosphide (GaAsP) or gallium phosphide (GaP). LED have a typical voltage drop from 1.5 to 2.5V for currents between 10 to 50 mA.



### Operation of LED:

In forward bias LED, when majority carriers recombine they radiate energy in the form of light. The light emitted by LED is proportional to the forward current.

### Advantage of LED:


- \* Solid state light source
- \* low power consumption
- \* fast on off operation
- \* longer life
- \* Extremely bright and low cost.

### Application of LED

- \* Power indicator
- \* Displays [ 7 segment display ]
- \* Engineering light.
- \* Alarm system.


### 2.7.3 Photo Diode:

Photo diode is used to convert light signal into electrical signal. It is made by using compound semiconductor such as Gallium Arsenide. It is constructed such that its PN junction can be exposed to light through the clear window or lens.

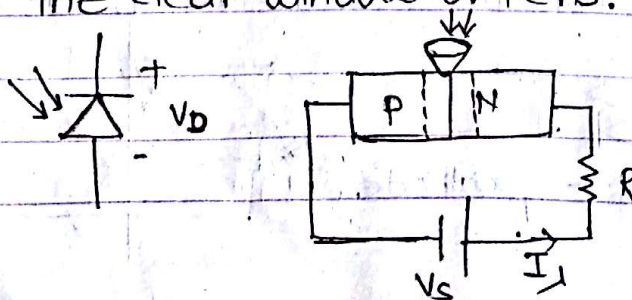
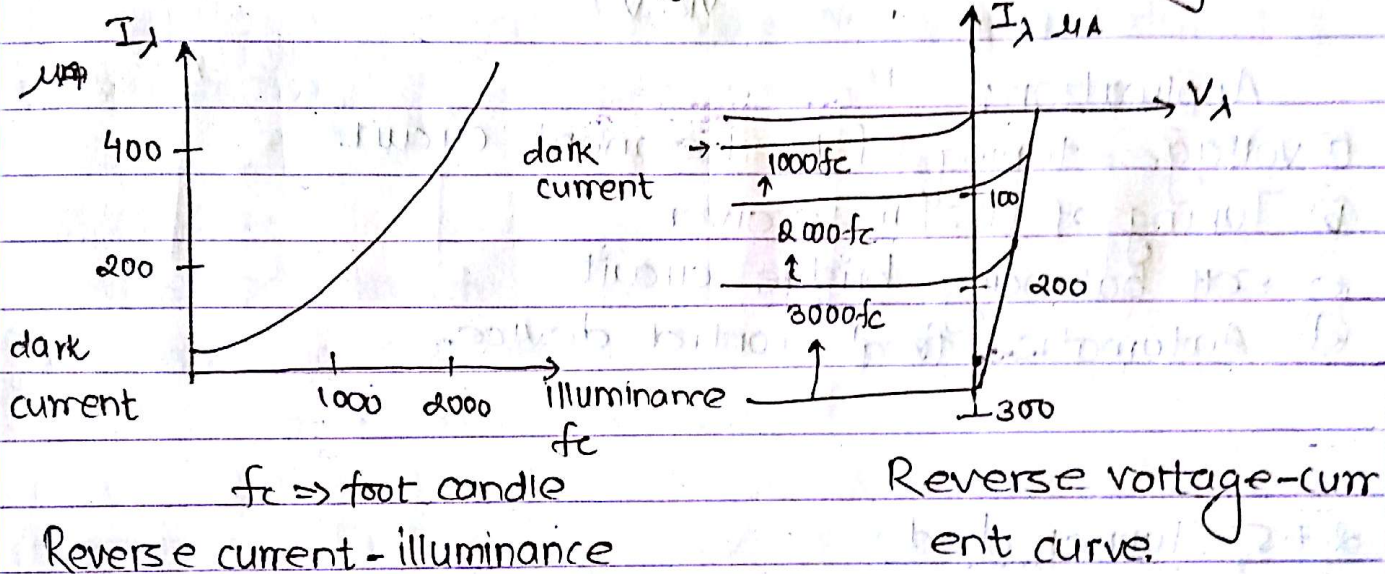
### Operation:

If a reversed biased PN Junction is exposed to incident light the photon striking the junction break the covalent bonds generating electrons holes pair. These minority carriers are swept across the junction giving rise to a reverse current that current known as photo current, is proportional to intensity of the incident light.



Reverse current - illuminance

Reverse voltage-current curve.

### Application:

- Ⓐ Optical transmission
- Ⓑ Photo detector in alarm and counting system.
- Ⓒ Solar cell.

### 2.7.4: Varactor diode or varicap:


varactor diode ( voltage variable capacitor, varicap or tuning diode) is a semiconductor voltage dependent capacitor. It utilize the property of voltage dependent junction capacitance of the diode that exists in the.

reversed biased junction.

The capacitance can vary from 2 to 100 pF depending on v<sub>r</sub> cap.


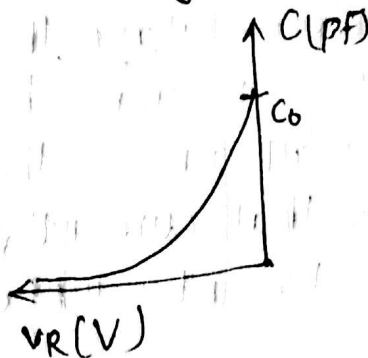
$$C_j = \frac{C_j(0)}{\left(1 + \frac{V_R}{V_0}\right)^n}$$




Application:

- (a) voltage tuning of LC Resonant circuit.
- (b) Tuning of TV, fm. receiver
- (c) self balancing bridge circuit
- (d) Automatic freq<sup>n</sup> control device.
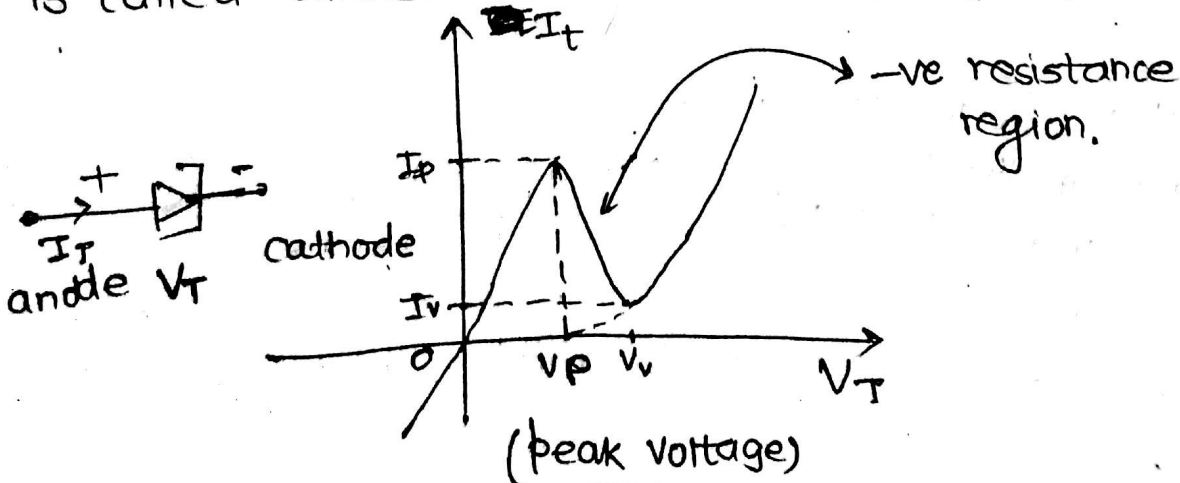
### 2.7.5 Tunnel diode

Tunnel diode is highly doped s/c diode with breakdown voltage at 0V. Due to high doping the depletion region is too thin that many carriers can penetrate through the junction even when they do not possess enough energy. This phenomenon is known as tunneling and the diode is called tunnel diode or Esaki diode.



In reverse bias condition, the diode acts as an excellent conductor. Forward biased also produce immediate conduction. The current reaches a max. value (peak current) for small diode voltage  $V_p$ . If forward voltage is further increased beyond  $V_p$ , the current decreases to min. value ( $I_v$ ) (valley current) at  $V_v$ . The region bet<sup>n</sup> peak and valley point is called '-ve resistance'.

for voltage greater than  $V_v$ , the current start to increase exactly as a normal diode.

### Application:-


- ① High speed switch
- ② As microwave oscillator
- ③ Relaxation oscillator circuit.

### Advantages


- \* low noise
- \* low power consumption
- \* high speed

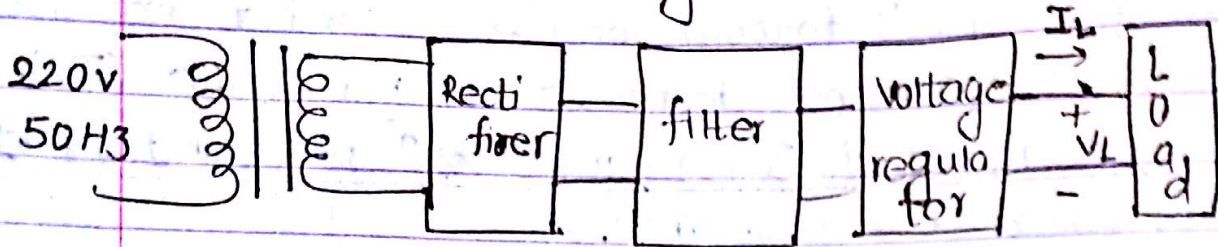2.8. DC Power supply:

DC power supply converts high voltage AC into one or more low DC voltage.



step down Transformer.

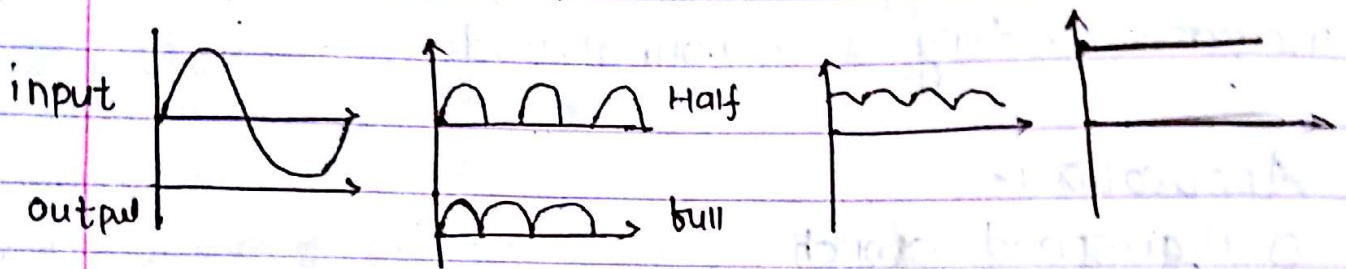

2.8.1 Review of AC signal:

Power AC signal:

① average value: 
$$V_{DC} = \frac{1}{T} \int_0^T v_s(t) dt$$

$= \frac{V_p}{\pi/2}$  for sine wave

$= 0.632 V_p$

② Rms value = 
$$\sqrt{\frac{1}{T} \int_0^T v_s^2(t) dt}$$

$= \frac{V_p}{\sqrt{2}}$

③ for ac + dc

$$v_s(t) = V_s + v_s(t)$$

DC component 
$$V_s = \frac{1}{T} \int_0^T v_s(t) dt$$

\* AC component:  $V_r(t) = V_s(t) - V_s$

rms value of (ripple) AC is,

$$V_{r \text{ rms}} = \sqrt{\frac{1}{T} \int_0^T V_r^2(t) dt}$$

$$V_{r(\text{rms})} = \sqrt{V_{\text{rms}}^2 - V_{\text{DC}}^2}$$

(ac)      (ac+dc)

\* ripple factor,  $r = \frac{V_{r(\text{rms})}}{V_{\text{DC}}} \times 100\%$

$$= \frac{\sqrt{V_{\text{rms}}^2 - V_{\text{DC}}^2}}{V_{\text{DC}}} \times 100\%$$

$$= \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{DC}}}\right)^2 - 1} \times 100\%$$

$$= \sqrt{K_f^2 - 1} \times 100\%$$

$$\frac{V_{\text{rms}}}{V_{\text{DC}}} = K_f \rightarrow \text{form factor}$$

\* Rectification efficiency

$$\eta = \frac{\text{DC power deliver to load}}{\text{AC input power}}$$

$$= \frac{P_{\text{DC}}}{P_{\text{AC}}} = \frac{I_{\text{DC}}^2 \cdot R_L}{I_{\text{rms}}^2 \cdot R_L} = \left(\frac{I_{\text{DC}}}{I_{\text{rms}}}\right)^2$$

$$= \frac{1}{K_f^2}$$

where,  $\frac{I_{\text{rms}}}{I_{\text{DC}}} = K_f$

\* Rectifier circuit:

converts ac signal into a signal with dc component or pulsating dc.



Types

\* Half wave rectifier

\* full wave rectifier

- ↳ central tapped
- ↳ Bridge circuit

Half wave rectifier:

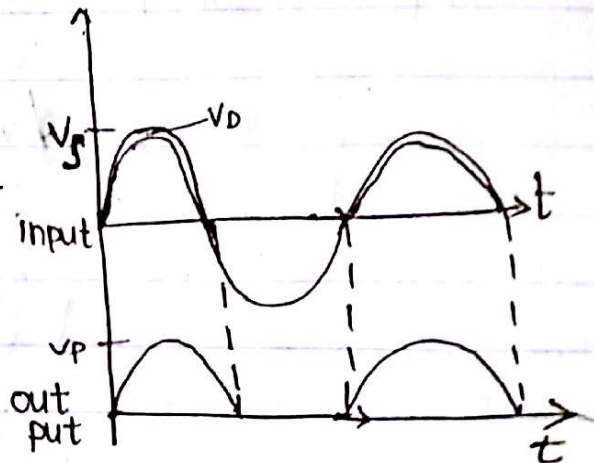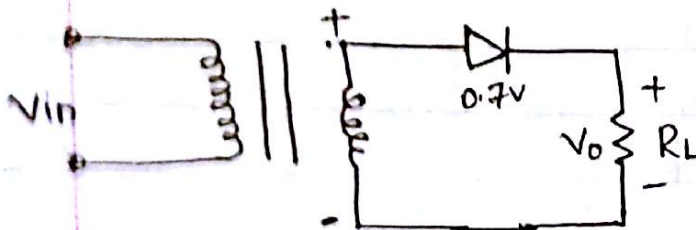

frequency of o/p signal.

$$f_o = f_s$$

output voltage,  $V_o = V_s - V_D$

• for,  $V_s \geq V_D$

= 0 for  $V_s < V_D$

Output peak voltage  $V_p = V_s - V_D$

output rms voltage  $V_{rms} = \frac{V_p}{\sqrt{2}} = 0.5V_p$


output DC "  $V_{DC} = \frac{V_p}{\pi} = 0.318V_p$

form factor  $k_f = \frac{V_{rms}}{V_{DC}} = 1.57$

ripple factor  $r = \sqrt{k_f^2 - 1} \times 100\% = 121\%$

efficiency  $(\eta) = \frac{100\%}{k_f^2} = 40.6\%$


in reverse bias:

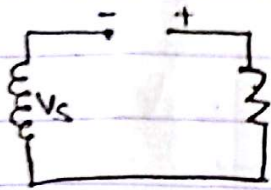

Peak inverse volt =  $V_s$

no volt drop # PIV rating  $> V_s$

(b) central tapped full wave rectifier

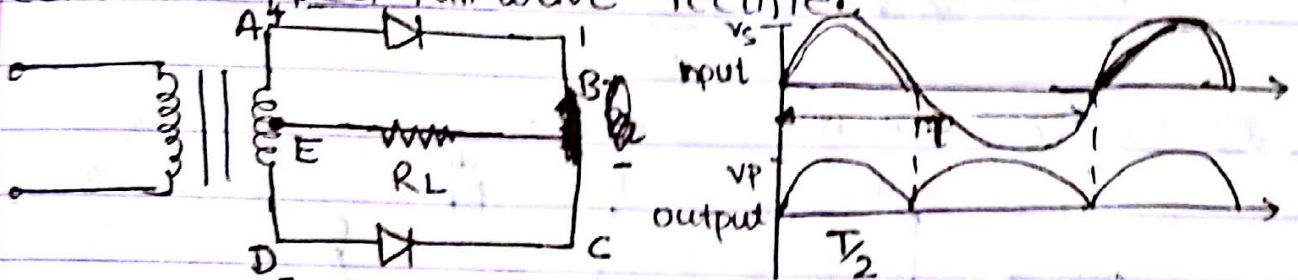

(a) in forward bias, +ve half cycle, end A is +ve so current flows through. ABRLEA (path).

(b) in -ve half cycle, end D is +ve so current flows through path DCBRLED

frequency.  $f_o = 2f_s$

$$V_o = V_s - V_D \text{ for } V_s \geq V_D$$

$$= 0 \text{ for } V_s \leq -V_D$$

Peak volt:  $V_p = V_s - V_D$

$$\text{DC volt } V_D = \frac{2V_p}{\pi} = 0.636V$$

$$\text{Rms. volts } V_{rms} = \frac{V_p}{\sqrt{2}} =$$


$$k_f = 1.11$$

$$\text{ripple factor: } r = \sqrt{k_f^2 - 1} \times 100\%$$

$$= 48.2\%$$


$$\text{efficiency. } \eta = \frac{1}{(k_f)^2} = \frac{100\%}{(1.11)^2} = 81.2\%$$

121 110017

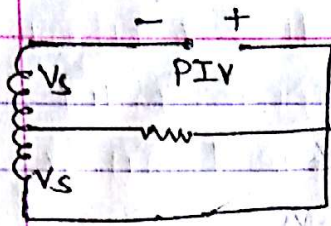

\*  $PIV \geq 2V_s$   
 PIV rating  $\geq 2V_s$

© Bridge circuit.

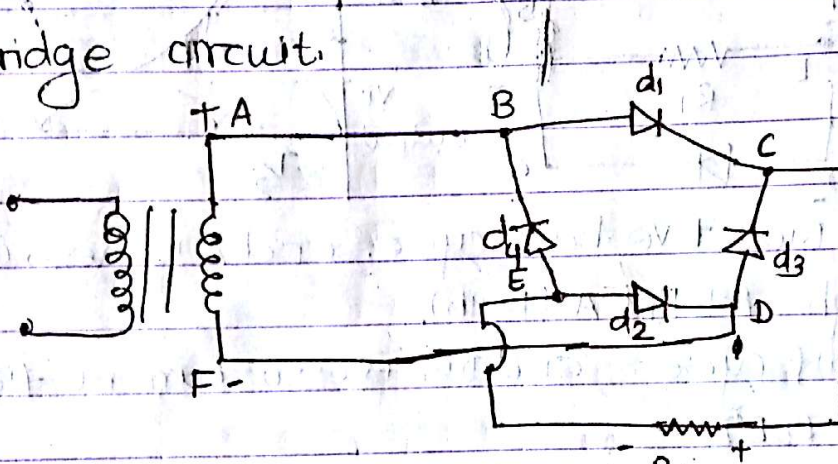

\* for +ve half cycle: A end +ve  
 $d_1$  and  $d_2$  are forward bias.

so current flows through  $A B d_1 C E d_2 D F$

\* for -ve half cycle, F end +ve  
 $d_3$  and  $d_4$  are forward bias.

so current flows along path  $F D d_3 C E d_4 B A$

frequency  $f_o = 2f_s$

$$V_o = V_s - 2V_D \text{ for } V_s \geq V_D$$

$$= -V_s - 2V_D \text{ " } V_s < -V_D$$

op peak volt,  $V_p = V_s - 2V_D$

o/p DC ..  $V_{DC} = \frac{2V_p}{\pi} = 0.636 V_p$

o/p rms ..  $V_{rms} = \frac{V_p}{\sqrt{2}}$



form factor =  $K_f = 1.11$

ripple factor = 48.2%      efficiency = 81.2%

RC

\* Rectifier with filter capacitor:

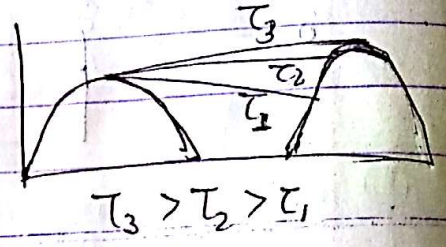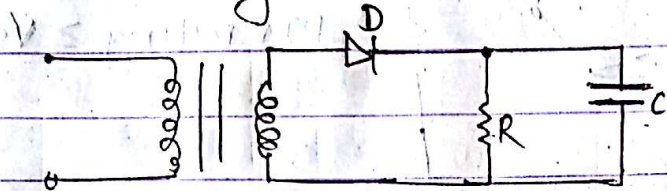Filter capacitor is used to minimize the ac component of rectified signal.



$$T = RC$$


discharge (Time constant) for Triangular wave approximation.

Time constant high discharge capacity low

$$V_{r\text{ rms}} = \frac{V_r (P-P)}{2\sqrt{3}}$$

\* Zener diode voltage regulator circuit:

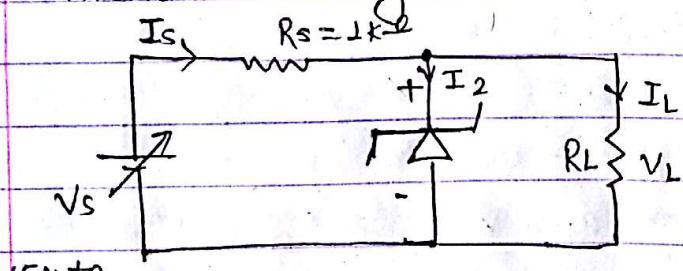Zener diode regulator provides a regulated DC across the load regardless of the voltage fluctuation and current drawn by the load.



15V to 20V

$$I_Z = \frac{V_s - V_Z}{R_s}$$



for  $V_s = 15V$   
 $I_Z = 0 \Rightarrow V_Z = 15V$

$V_Z = 0 \Rightarrow I_Z = \frac{V_s}{R_s} = 15mA$

for  $V_s = 20V$

$V_Z = 0, I_Z = \frac{V_s}{R_s} = 20mA$

$I_Z = 0 \Rightarrow V_Z = 20V$

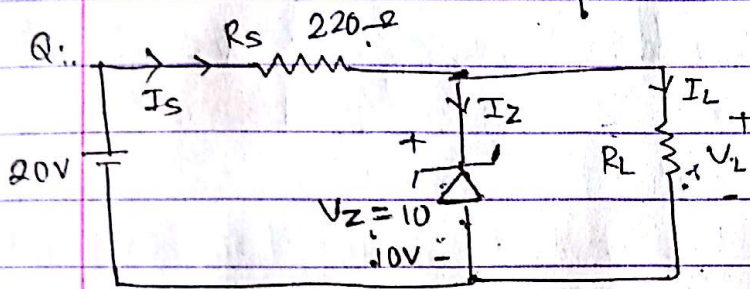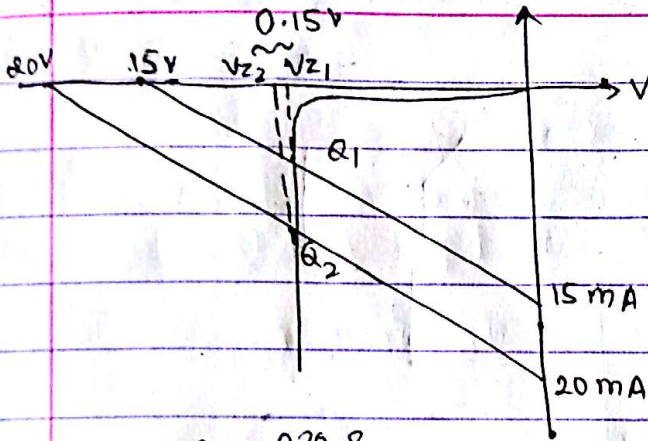

remove zener diode  
(open circuit voltage.)  
calculate V across zener.

$P_z \text{ max} = 400 \text{ mW}$

find.  $V_L, I_L, I_s, I_z$

for  $\Rightarrow R_L = 180 \Omega$

$V_z = \frac{20 \times 180}{180 + 220}$

$= \frac{20 \times 180}{400}$

$V_z = 9 \text{ V} < V_z = 10 \text{ V}$

so it is acting as reverse bias, in reverse bias / Open circuit

$I_z = 0, I_s = I_L = \frac{20}{400} = 0.05 \text{ A}$

$V_L = 9 \text{ V}$

if  $R_L = 470 \Omega$

$V_z = \frac{20 \times 470}{470 + 220} = 13.66 > \text{diode voltage.}$

zener diode is in breakdown voltage

$\therefore V_L = V_z = 10 \text{ V}, I_z = \frac{V_L}{R_L} = \frac{10}{470} = 0.021 \text{ A}, I_s = \frac{V_s - V_L}{R_s}$

$= 0.045 \text{ A} = \frac{20 - 10}{220}$

$$\begin{aligned} I_{z \text{ max}} &= \frac{P}{V} \\ &= \frac{400 \text{ mW}}{10} \\ &= 40 \text{ mW} \end{aligned}$$

## Chapter: 3

### \* Transistor

The device which is able to produce gain in a circuit.

(a) Bipolar Junction Transistor


(b) Field Effect Transistor

(1) MOSFET (Metal oxide semiconductor)

(2) JFET (Junction)

3.1 Bipolar Junction Transistor:

Physical structure of BJT:

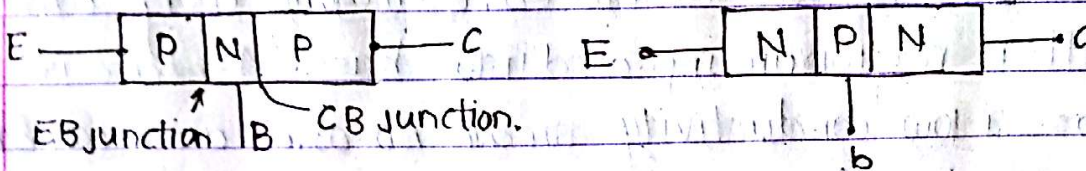


	Region	Doping level	Thickness	function
(a)	E	high	moderate	Supply charge
(b)	C	moderate	Thick	collect "
(c)	B	low	Thin	control the flow of charge

### Mode of Operation

	Mode	EBJ	CBJ	Remarks
RB reverse bias	cutoff	RB	RB	} switching
	saturation	FB	FB	
FB forward bias	Active	FB	FB	amplifier

### 3.1.3. Operation of npn transistors in different mode.

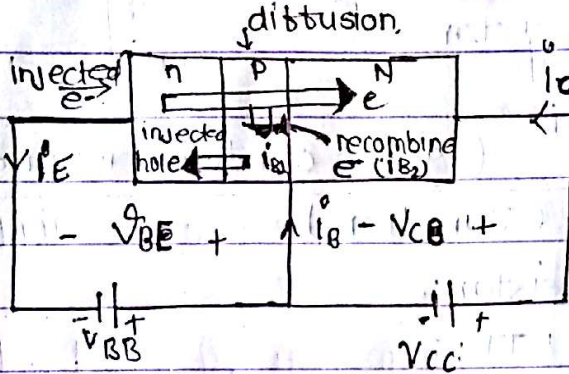(iii) (a) Active mode: (EBJ - FB, CBJ - RB)



$$I_E = I_C + I_B$$

$$I_B < I_C < I_E$$

Operation of NPN Transistor:

Since EBJ is forward biased,  $e^-$  (majority charge carriers) in emitter region are injected into base. As base is thin and has a low conductivity, small no. of  $e^-$  are recombined with hole in p base. The rest of the injected  $e^-$  (>95% diffuse through base region towards the edge of CBJ and sweep into collector (CBJ is reverse biased).

Terminal current of BJT.

(i) Emitter current

$$I_E = I_{En} (e^- \text{ injection from E to B}) + I_{Ep} (\text{hole injection from B to E})$$

$$\approx I_{En}$$

(ii) Collector current:  $I_C = I_{Cn} (e^- \text{ drift}) + I_{CBo} (\text{CBJ reverse saturation current with emitter open})$

$$\approx I_{Cn} = I_S e^{V_{BE}/V_T}$$

(iii) Base current:  $I_B = I_{B1} (\text{hole injection from B to E}) + I_{B2} (\text{recombined in base})$


(b) cut-off mode: (EBJ - RB, CBJ - RB)

$$i_E = i_C = i_B = 0$$

⇒ Transistor act as open switch

\* In active mode transistor acts as a controlled current source

\* saturation mode (EBJ - FB, CBJ - FB)

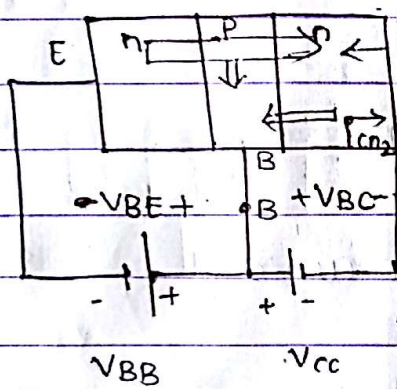

Collector current ( $i_C$ ) =  $i_{C1}$  -  $i_{C2}$

if forward bias of CBJ is increased, the collector current reduces:

Barrier Voltage of EBJ  $\Rightarrow V_{BE} \approx 0.7V$  (0.6-0.8)  
" " " " " " CBJ  $\Rightarrow V_{BC} \approx 0.5V$  (0.4-0.6)

$$V_{CE} = V_{CB} + V_{BE}$$


$$= V_{BE} - V_{BC}$$


$$= 0.2V \text{ (0.3 - 0.4)V}$$

In saturation mode, transistor behaves as a closed switch.

\* closed

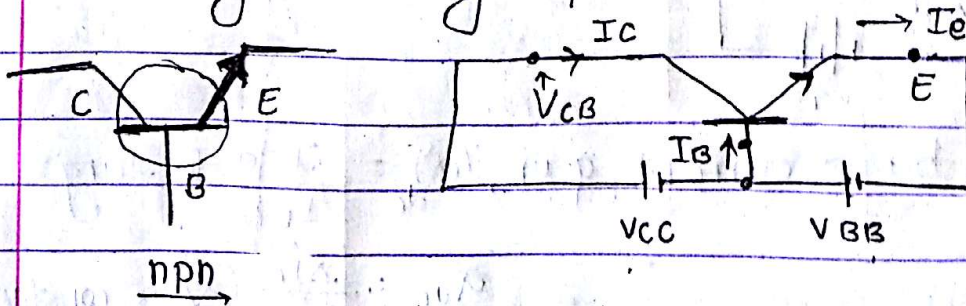\* Circuit symbol voltage polarities and current flow.



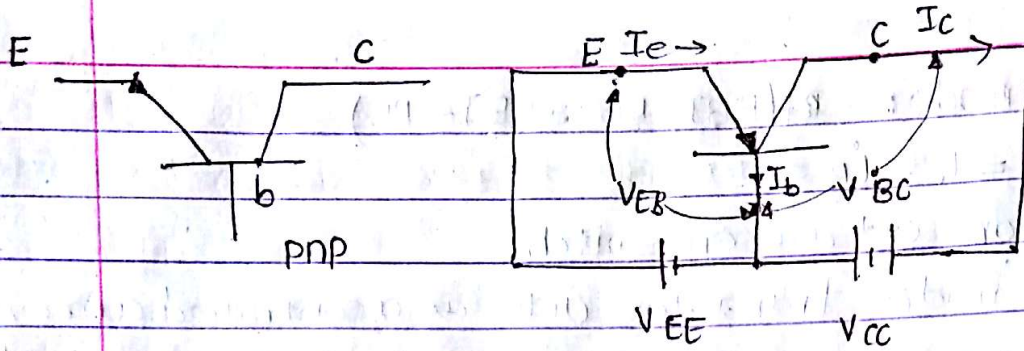

PNP - Transistor.

\* BJT configuration

Common base configuration

Common emitter configuration

Common collector

Two set of DC characteristic curve


(a) Input characteristic curve.

$$i_{in} = f(V_{in}) \text{ for } V_{out} = \text{constant}$$

(\*) output characteristic curve

$$I_{out} = f(V_{out}) \text{ for } i_{in} = \text{constant}$$

\* Common base configuration.

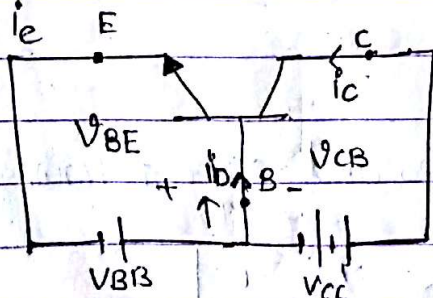

common base current gain,  $\alpha_{dc} = \frac{I_{cQ}}{I_{eQ}}$  for large signal


$$\alpha_{ac} = \frac{\Delta i_c}{\Delta i_e} \text{ (} V_{CB} \text{ constant)}$$



$\alpha$  ranges (0.95 to 0.99)  $\approx 1$

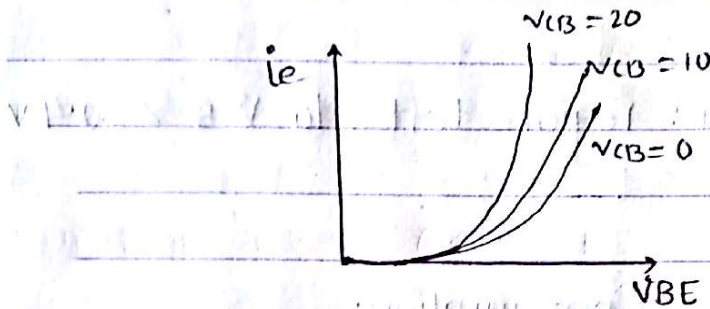
(a) Input characteristic curve:

$i_e = f(V_{BE})$  for  $V_{CB} = \text{constant}$



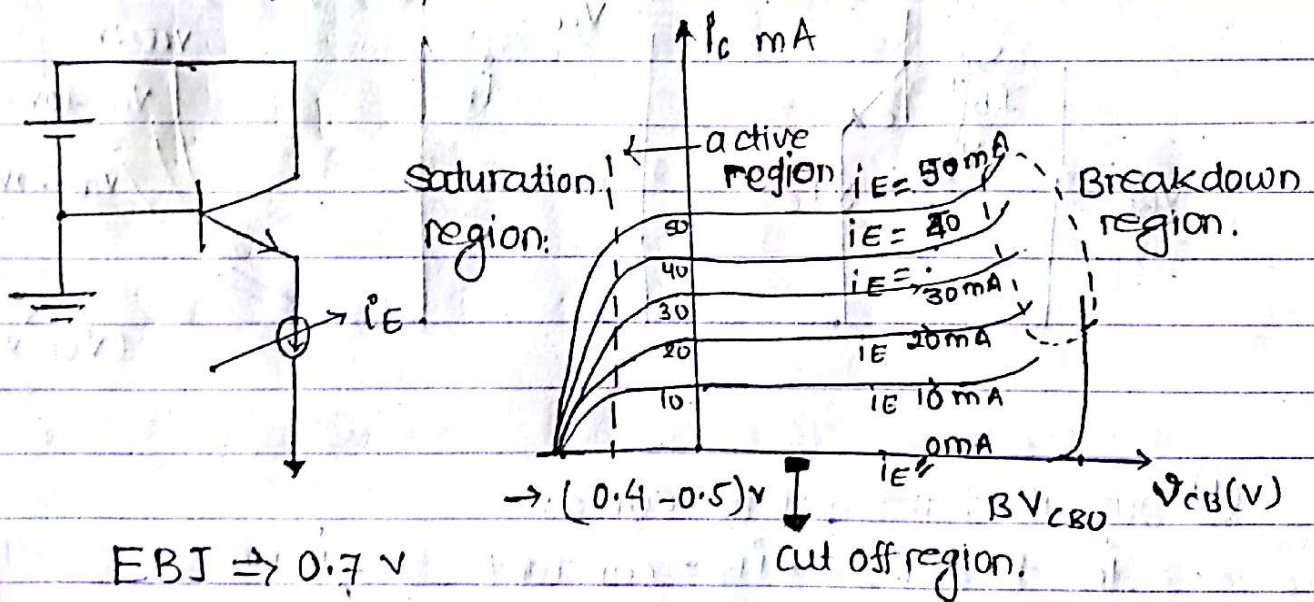(b) Output characteristic curve:

$i_c = f(V_{CB})$  for  $i_E = \text{constant}$



EBJ  $\Rightarrow 0.7 \text{ V}$

CBJ  $\Rightarrow V_{BC} = (0.4 - 0.6) \text{ V}$

$\therefore V_{CB} < -0.4$

(a) Cut off region:  $\Rightarrow$  region below  $i_E = 0$  line,  $i_c = I_{CBO} \approx 0$   
 $I_{CBO}$   $\rightarrow$  Collector to base current with emitter open ( $\mu\text{A}$ )


(b) Active region: Region between  $i_E > 0$  and  $V_{CB} > -0.4 \text{ V}$   
 $i_c \approx i_E$

The curves are approximately horizontal, small slope is due to early effect.  
 Dependence of current with  $V_{CB}$  is early effect.

- © Breakdown region: at high  $v_{cb}$ ,  $i_c$  rises rapidly, and
  - ⊗ CBJ breakdown at voltage  $BV_{CBO}$  for  $I_E = 0$
  - \*  $BV_{CBO} \geq 50V$


(d) Saturation Region: region left to  $v_{cb} < -0.4V$

### 3.2.2 Common Emitter Configuration:

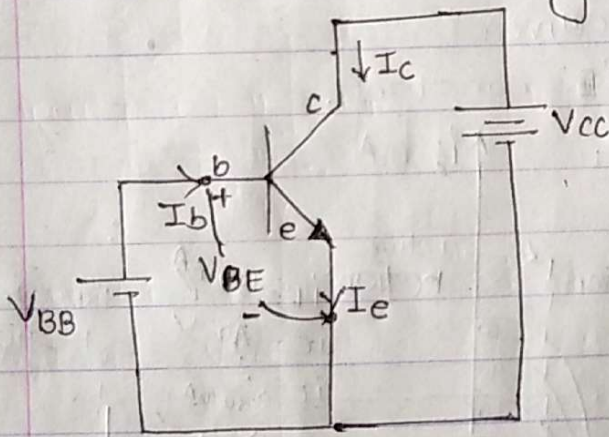



ⓐ Input characteristics curve

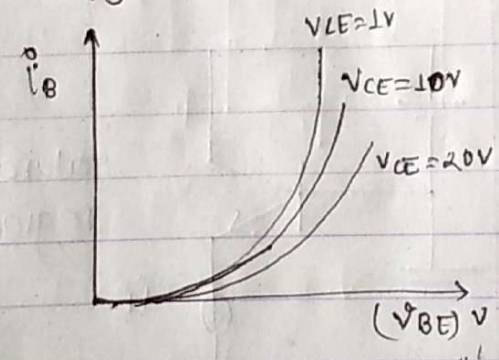$i_B = f(V_{BE})$  at  $V_{CE}$  constant



ⓑ output characteristic curve:

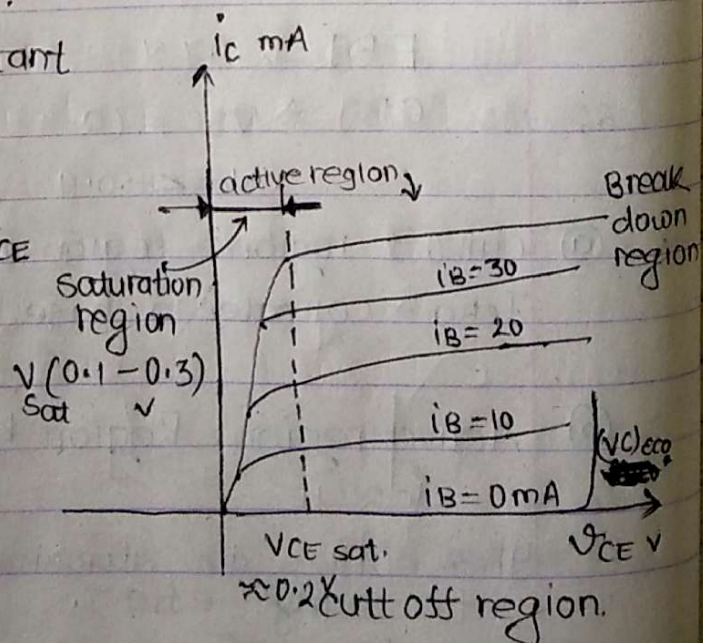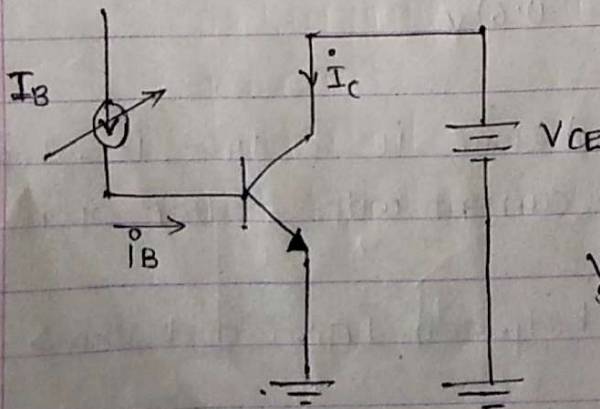$i_c = f(V_{CE})$  as  $i_B = \text{constant}$



$I_{CEO}$  = collector to emitter with open base [leakage current]  
 $= (\beta + 1) I_{CBO} \approx \beta I_{CBO}$

$BV_{CEO} = \frac{BV_{CBO}}{2}$

\* Common emitter current gain,  $(\beta)$

large signal  $\beta_{ac} = \frac{I_C}{I_B} (> 50)$

$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B}$ ,  $V_{CE} = \text{constant}$

### 3.2-3 Common collector configuration.

### 3.2.4 Properties of Transistor configuration:

Properties	CB	CE	CC
voltage gain, $A_v = \frac{V_{out}}{V_{in}}$	highest	high	less than 1 <del>highest</del>
current gain, $A_I = \frac{I_{out}}{I_{in}}$	less than 1	high	highest
power gain = $A_v \cdot A_I$	not high	highest	not high
input resistance, $R_{in} = \frac{V_{in}}{I_{in}}$	Small	high	highest
output resistance, $R_{out} = \frac{V_{out}}{I_{out}}$	highest	high	low.
Polarity of o/p signal	no change	180° out of phase	no change
Application	CB	CE	CC
	used for unity gain current amplifier and high freq amplifier	used for current, voltage and power amplification and used for audio frequency amplifier	used for impedance matching purpose voltage buffer amplifier. It is also known as emitter-follower, because unity voltage gain and no inversion phase property.

### 3.2.5 Relation between $\alpha$ and $\beta$ .

We have,

$$i_E = i_B + i_C$$

$$\text{where, } \alpha = \frac{I_C}{I_E}$$

$$\text{or, } \frac{i_E}{I_C} = \frac{i_B}{i_C} + \frac{i_C}{i_C}$$

$$\beta = \frac{I_C}{I_B}$$


$$\text{or, } \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\therefore \alpha = \frac{\beta}{\beta + 1}, \quad \beta = \frac{\alpha}{1 - \alpha}$$

### 3.3 DC - Biasing:

The purpose of biasing is to set the operating point that is independent of  $\beta$ , change and temperature variation.

Fixed bias (base bias)

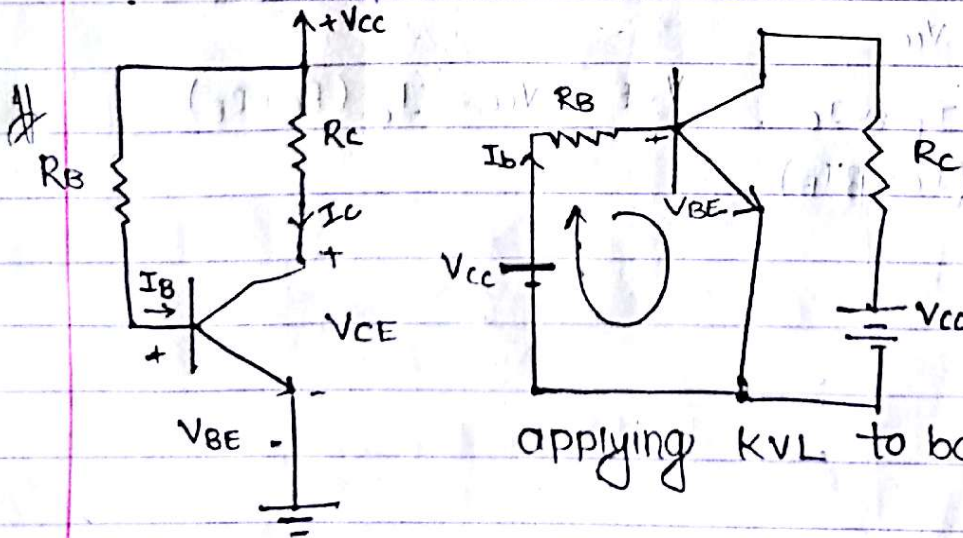

applying KVL to base emitter loop.

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


Applying KVL at collector to emitter loop

$$V_{CC} = I_C R_C + V_{CE}$$

$$\therefore V_{CE} = V_{CC} - I_C R_C, I_C = \beta I_B$$

Terminal voltage:  $V_E = 0, V_B = V_{BE}, V_C = V_{CE}$

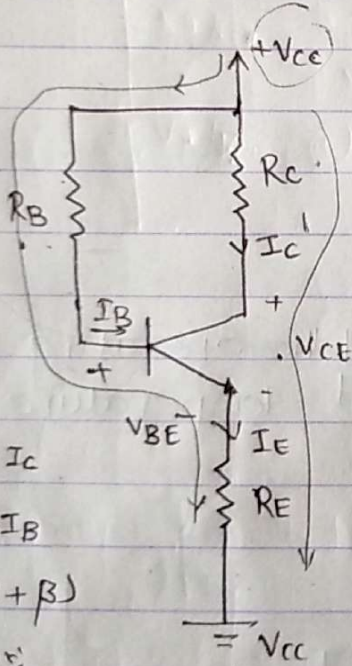(b) Emitter feedback bias (current feedback)



Applying KVL to base emitter loop

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$= I_B R_B + V_{BE} + (\beta + 1) I_B R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Applying KVL to collector emitter loop

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$I_C = I_B + I_E$$

$$= I_B + \beta I_B$$

$$= I_B (1 + \beta)$$

$$I_E \approx I_C$$

$$(I_C = \beta I_B)$$


# not complete

$$V_C = V_{CC} - I_C R_C$$

$$O_1 = V_{CE} + V_E$$

① collector Feedback bias (Voltage feedback)

at input loop

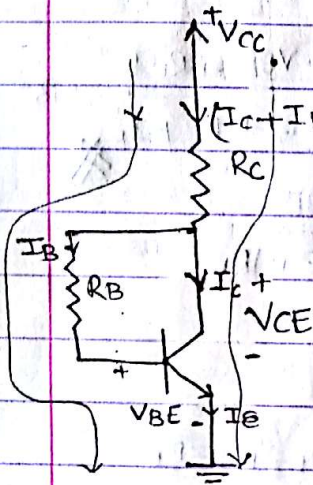

$$V_{CC} = (I_C + I_B)R_C + I_B R_B + V_{BE}$$

$$= (\beta I_B + I_B)R_C + I_B R_B + V_{BE}$$

$$= (\beta + 1)R_C I_B + I_B R_B + V_{BE}$$

$$\therefore \frac{V_{CC} - V_{BE}}{R_C(\beta + 1) + R_B} = I_B$$

$$\beta = \frac{I_C}{I_B}$$

collector/emitter loop:

$$V_{CC} = R_C I_C + I_B R_C + V_{CE}$$


$$V_{CC} = \beta I_B R_C + I_B R_C + V_{CE}$$

$$V_{CE} = V_{CC} - (\beta + 1)I_B R_C$$

② voltage divider bias:

- universal biasing method.


input part - (Thevenize circuit)

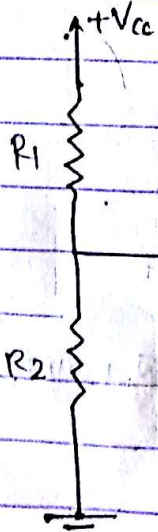


$$V_{TH} = \frac{R_2 \times V_{CC}}{(R_1 + R_2)}$$

$$R_{TH} = \frac{R_1 \times R_2}{(R_1 + R_2)}$$

$V_{BB} \rightarrow$  Base & ground

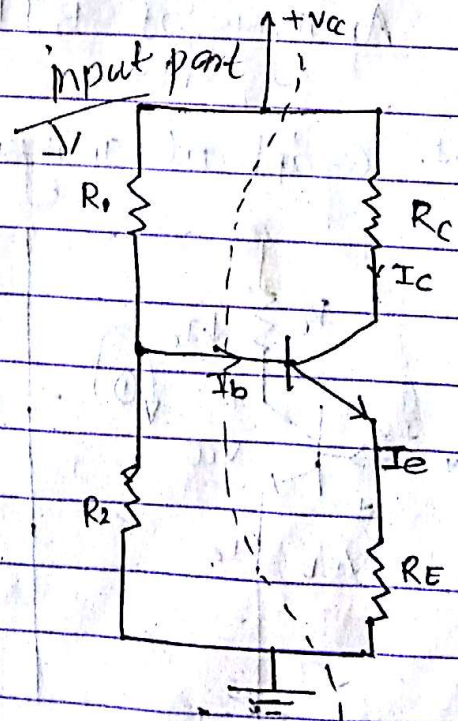

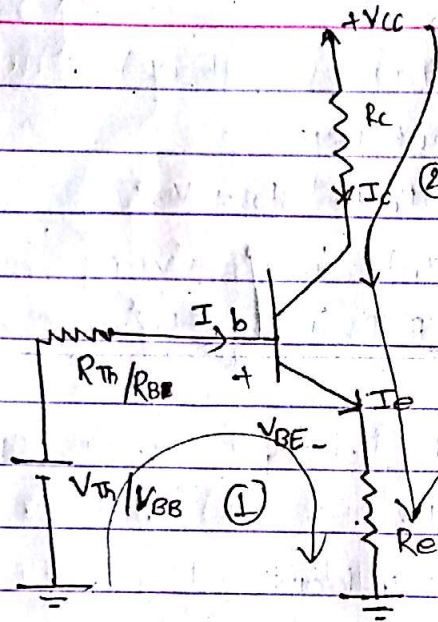

in input loop (1)

$$V_{BB} = R_B I_B + V_{BE} + R_E I_E$$

$$V_{BB} - V_{BE} = I_B R_B + R_E \beta I_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

$$V_{CC} = R_C I_C + V_{CE} + I_E R_E$$


$$V_{CE} = V_{CC} - (R_C I_C + I_E R_E)$$

$$V_{CE} = V_{CC} - (R_C I_C + I_E R_E)$$


$$I_C \approx I_E \quad V_{CE} = V_{CC} - (R_C + R_E) I_C$$

### Analysis of BJT circuit

#### 3.4.1. Graphical analysis:

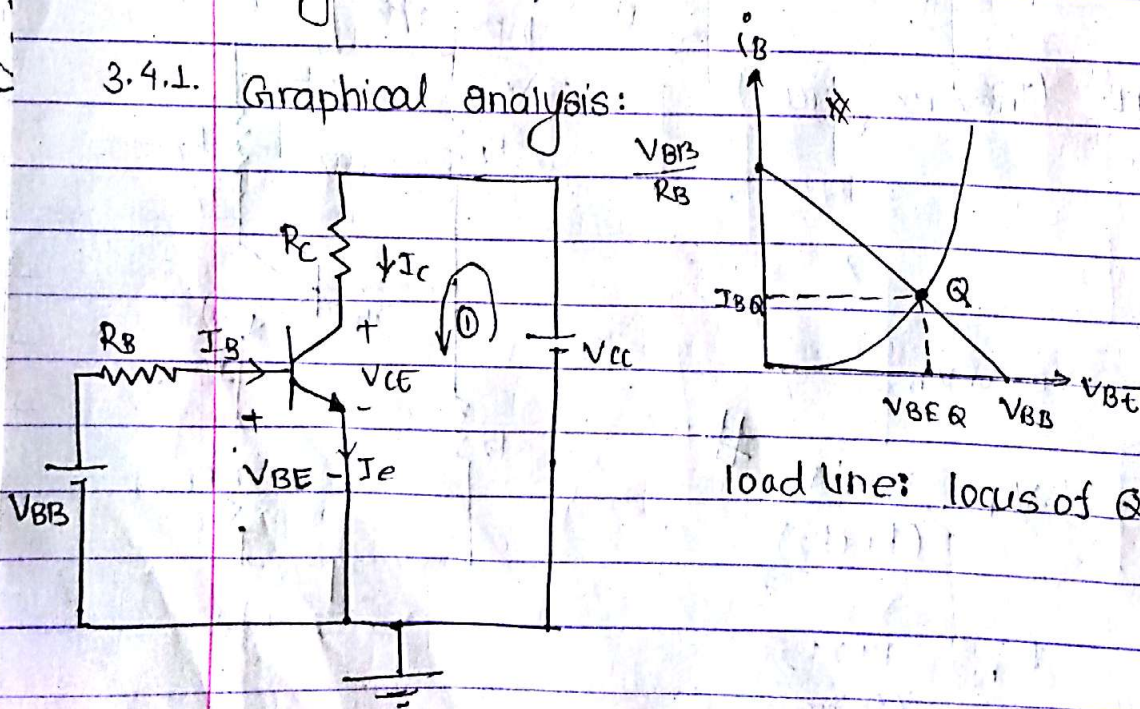


load line: locus of Q point

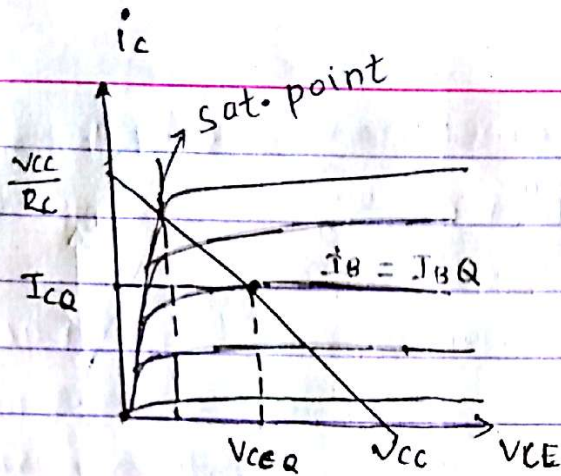


$V_{CC} = I_C R_C + V_{CE}$  from loop ①

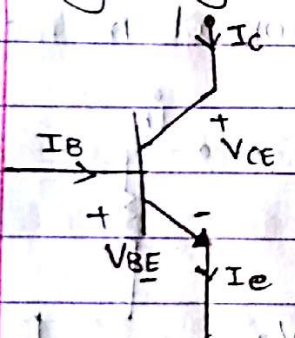3.4.2 Modeling the BJT:  
 (a) large signal model:




(b) active model:

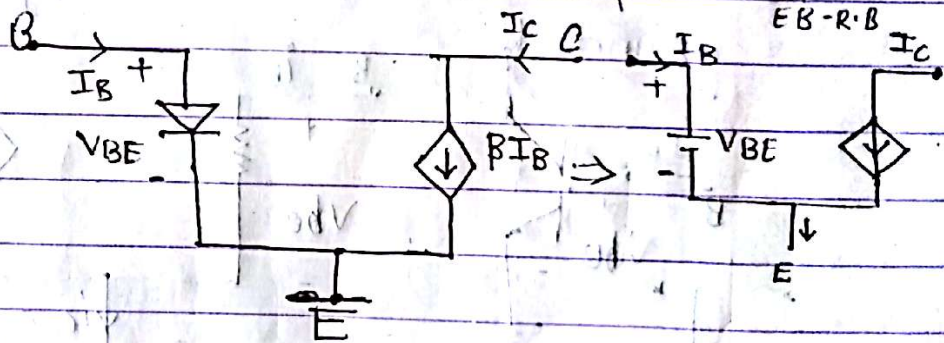

transistor active mode -  
 controlled current source  
 saturation: closed sw  
 cut off - open sw  
 $E-B-R \cdot B$


(b)

Saturation mode

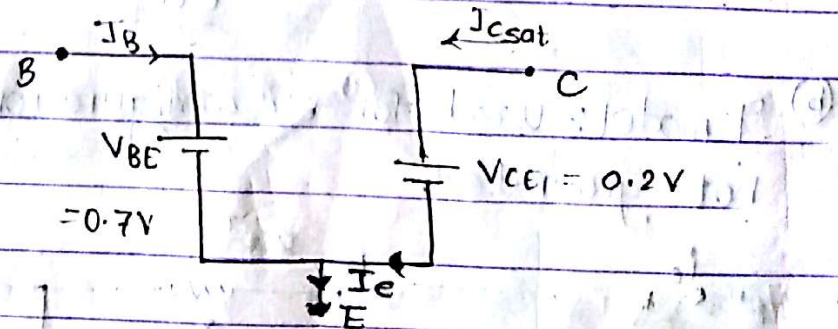

15

\* Cut off :

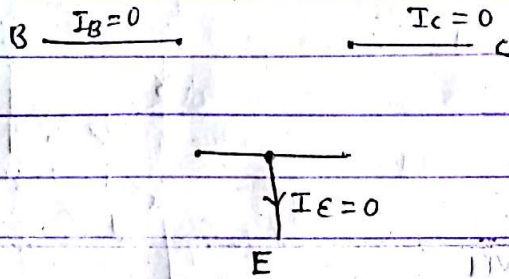


(B) Small signal Model (ac model)


$r_e$  model: (resistance at emitter model)

\* small signal model of diode: is  $r_d = \frac{V_T}{I_D}$

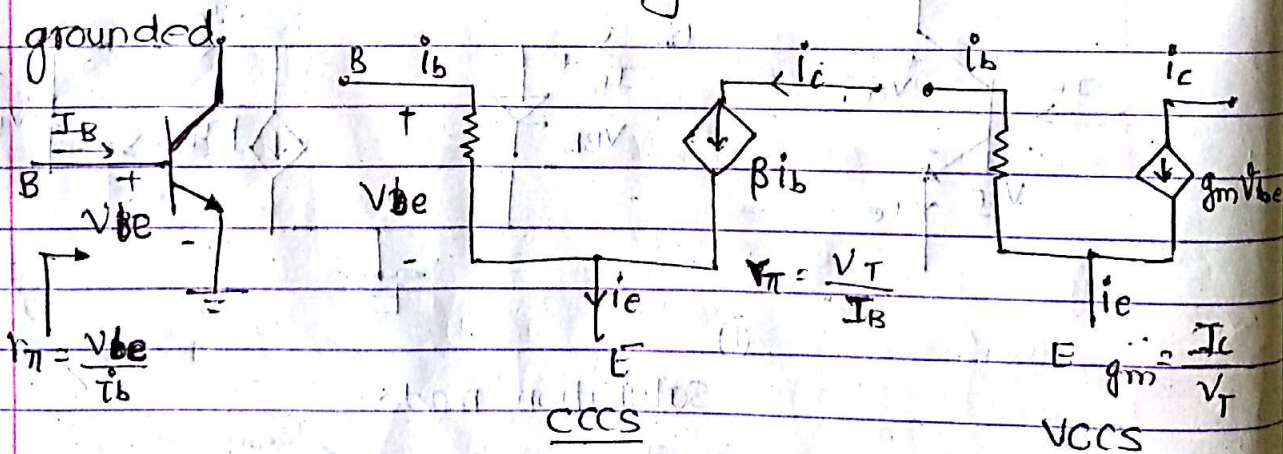(a)  $\pi$  model: used for CE configuration or when emitter is grounded.



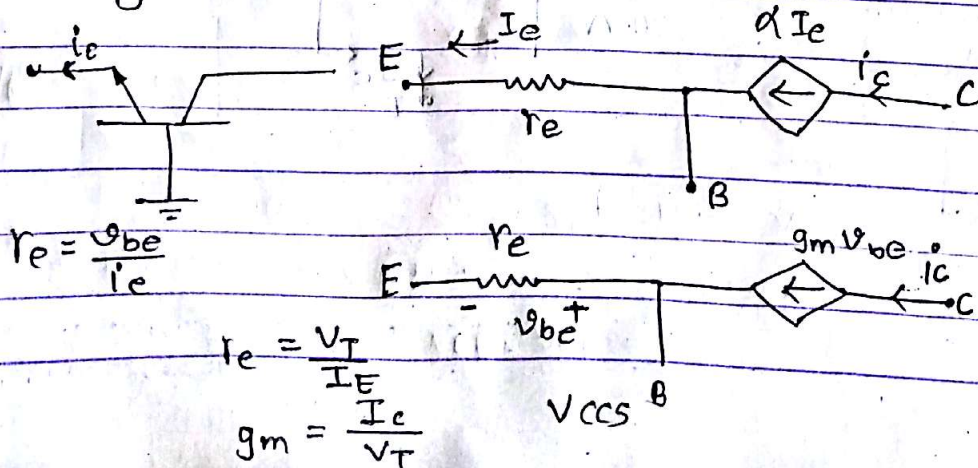(b) T model: used for CB configuration or when emitter is not grounded.



Relationship between  $r_e$  and  $r_{\pi}$


$$r_{\pi} = \frac{V_{be}}{i_b} = \frac{(\beta+1) V_{be}}{i_e} = (1+\beta) r_e$$

$$\therefore r_{\pi} = (\beta+1) r_e$$

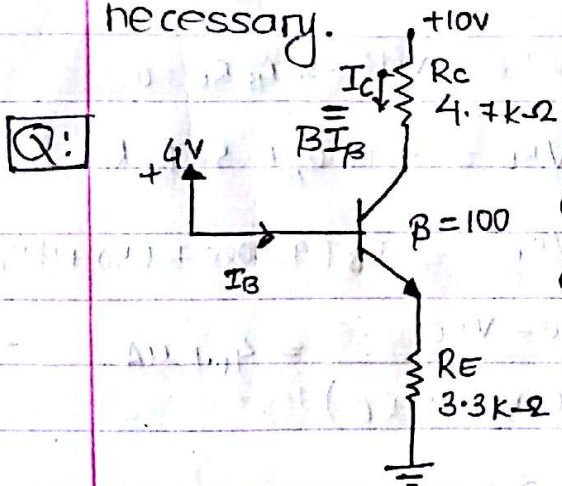3.4.3 DC analysis of BJT circuits:

Procedure:

- \* always assume the model as active.
- \* use corresponding mode and analysis.
- \* verify the sol<sup>n</sup> if  $V_{CE} > 0.3 \text{ V}$  or  $V_{CB} > -0.4 \text{ V}$  (assumption correct)
- \* Repeat the above steps with another assumption if necessary.



①  $I_C \approx I_E = 1 \text{ mA}$

①  $V_E = 4 - 0.7 = 3.3 \text{ V}$

②  $I_E = \frac{3.3 \text{ V}}{3.3 \times 1000} = 1 \text{ mA}$

$I_C = \beta I_B, I_E = 10.4 \text{ A}$

$V_C = 10 - I_C \times 4.7 = 5.3 \text{ V}$

Find all terminal currents.  $V_{CE} = V_C - V_E = 2 \text{ V} > 0.3 \text{ V}$  (assumption correct)

⑥ if  $V_{BB} = 6 \text{ V}$

$V_E = 6 - 0.7 = 5.3 \text{ V}$

$I_E = \frac{5.3 \text{ V}}{3.3 \times 1000} = 1.6 \text{ mA}$

$I_C \neq \beta I_B = 100 \cdot I_B$

$V_C = 10 - I_C \cdot 4.7 \times 1000$   
 $= 10 - 1.6 \times 10^{-3} \times 4.7 \times 10^3$   
 $= 0.6 \text{ V}$

Given  $V_{CE} = 0.2 \text{ V}, V_C = 2.48$


$V_{CC} = 10 \text{ V}$

$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{10 - 2.48}{4.7 \times 1000} = 2 \text{ mA}$

$I_B = 0.64 \text{ mA}$

$I_C = 0.96 \text{ mA}$

Q.

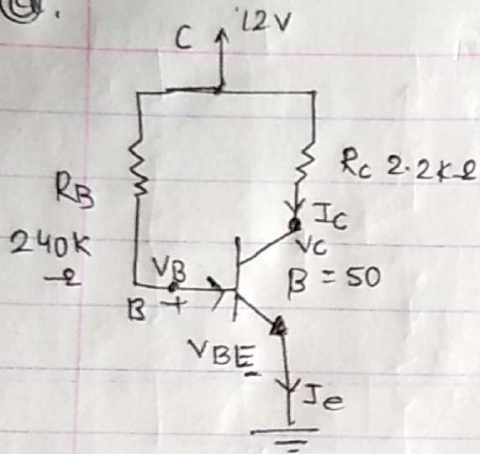

$$12 - 240 \times 1000 I_B - V_{BE} = 0 \quad \beta = \frac{I_C}{I_B}$$

$$\frac{12 - V_{BE}}{240 \times 1000} = I_B \quad \boxed{I_C = 50 I_B}$$

$$12 - 2.2 \times 1000 I_C = 0$$

$$I_B = 47 \mu A$$

$$I_C = 2.35 mA$$


$$I_E \approx 2.35 mA$$

$$V_B = 0.7 V$$

$$V_C = 6.83 = V_{CE} V$$

$$V_{BC} =$$

$$I_C = I_E + I_B$$

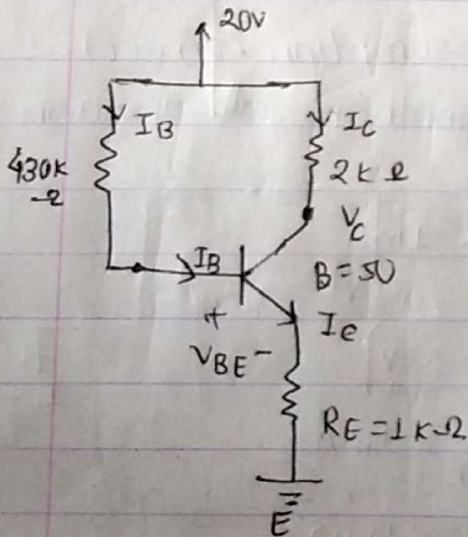

$$20 - 430 \times 1000 I_B - V_{BE} - I_E R_E = 0$$

$$20 - 430000 I_B - V_{BE} - 50 I_B R_E = 0$$

$$\Rightarrow 20 - V_{BE} = 430000 I_B + 50 I_B R_E$$

$$\Rightarrow \frac{20 - V_{BE}}{430000 + (50 + 1) R_E} = I_B$$

$$\textcircled{1} I_B = \frac{20 - V_{BE}}{(430000 + 51 R_E)} = 40.1 \mu A$$

$$\textcircled{ii} I_C = \beta I_B = 50 \times 40.1 \mu A = 2.01 mA$$

$$\frac{V_{CC} - V_C}{R_C} = I_C$$

$$\therefore V_{CC} - I_C R_C = V_C$$


$$\textcircled{iii} \therefore V_C = 15.98 V$$

$$= 15.98 V > 0.3 V \quad \textcircled{iv} I_E \approx I_C = 2.01 mA$$

$$V_B = 2.71 V$$

$$V_{BE} = V_{CE} =$$

$$V_{BC} =$$

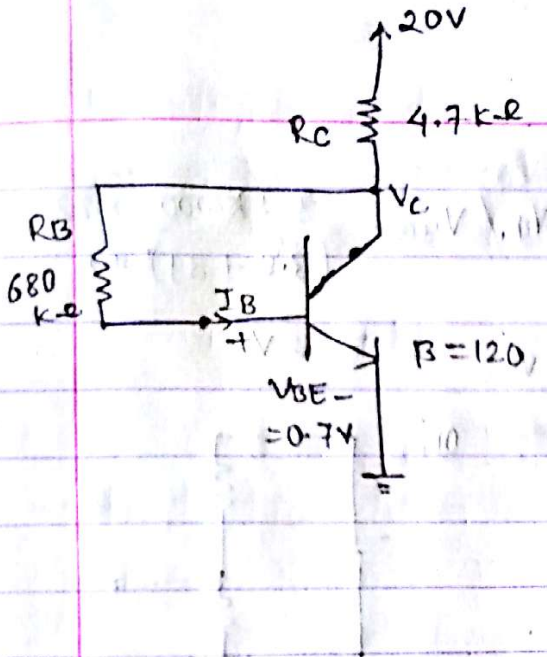

$$I_B = \frac{V_{CC} - V_{BE}}{R_C(B+1) + R_B} = \frac{20 - 0.7}{4.7 \times 1000(120+1) + 680 \times 1000}$$

$$= \frac{19.3}{1.248700} = 1.54 \times 10^{-5} \text{ A}$$


$$I_C = \beta I_B = 120 \times 1.54 \times 10^{-5} \text{ A} = 1.85 \text{ mA}$$

$$I_E = I_C + I_B = (1.85 \times 10^{-3} + 1.54 \times 10^{-5}) \text{ A} = 1.87 \times 10^{-3} \text{ A}$$

$$V_C = V_{CE} = +V_{CC} - I_C R_C$$



$$V_{CC} - V_C = I_C R_C \Rightarrow V_C = 20 - 1.85 \times 10^{-3} \times 4.7 \times 10^3 = 20 - 8.695 = 11.305 \text{ V}$$

$$V_{BE} = V_B = 0.7 \text{ V}$$

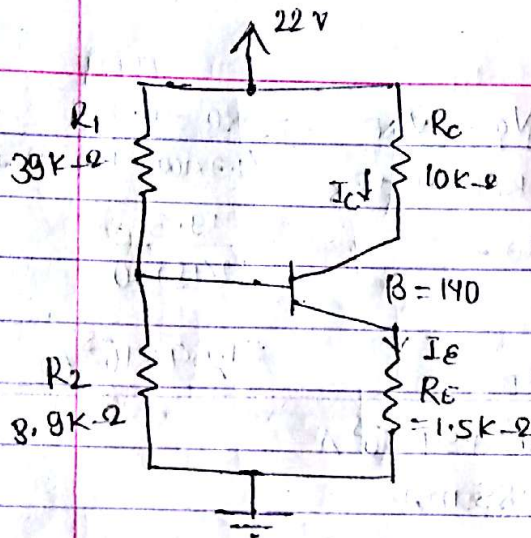

$$V_{th} / V_{BB} = \frac{3.9 \times 1000 \times 22}{(3.9 + 39) \times 1000}$$

$$V_{BB} = 2V$$

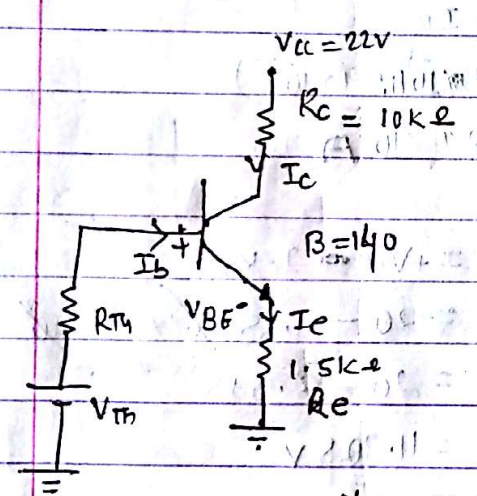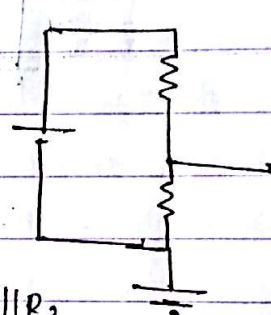

$$R_{th} / R_B = R_1 || R_2$$

$$= \frac{(39 \times 3.9) \times 10^3 \times 10^3}{(39 + 3.9) \times 10^3}$$

$$= 3.5 k\Omega$$

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{2 - 0.7}{10 \times 1000 + (141) \times 1.5 \times 1000}$$

$$= \frac{1.3}{221500}$$

$$= 5.8 \mu A$$

$$I_C = \beta I_B$$

$$= 140 \times 5.8 \mu A$$


$$= 8.21 \times 10^{-4} A$$

$$V_E = I_C R_E$$


$$V_C = 22 - I_C R_C = 22 - 0.85 \times 10^{-3} \times 10 \times 10^3$$

$$= 13.5 V$$

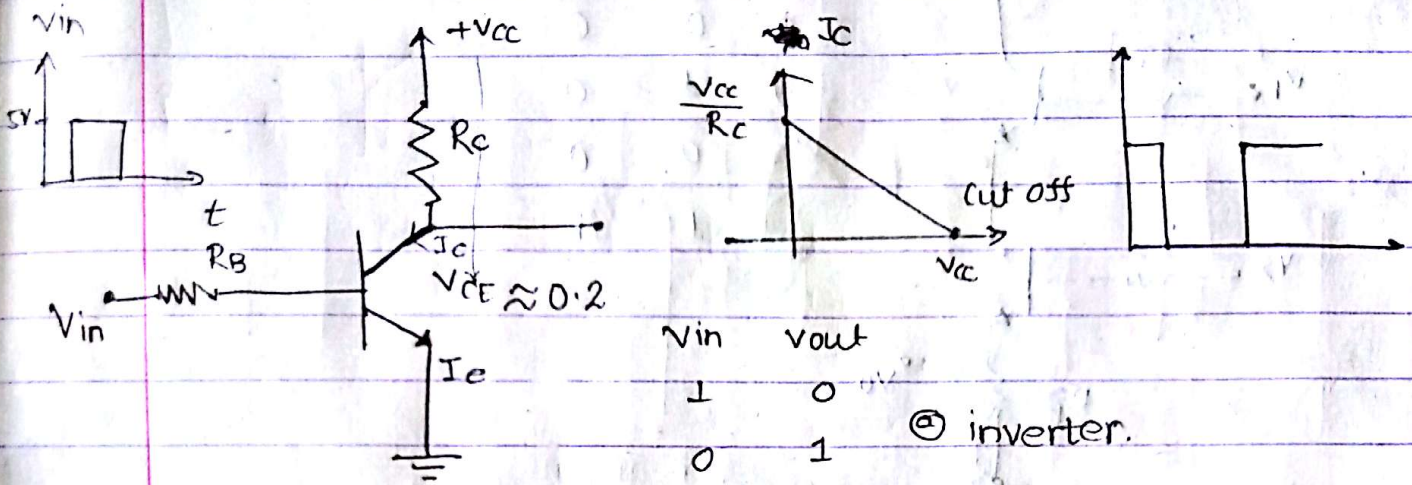
### 3.5 BJT switch and logic circuit: cut off and saturation mode:




### OR-Gate:

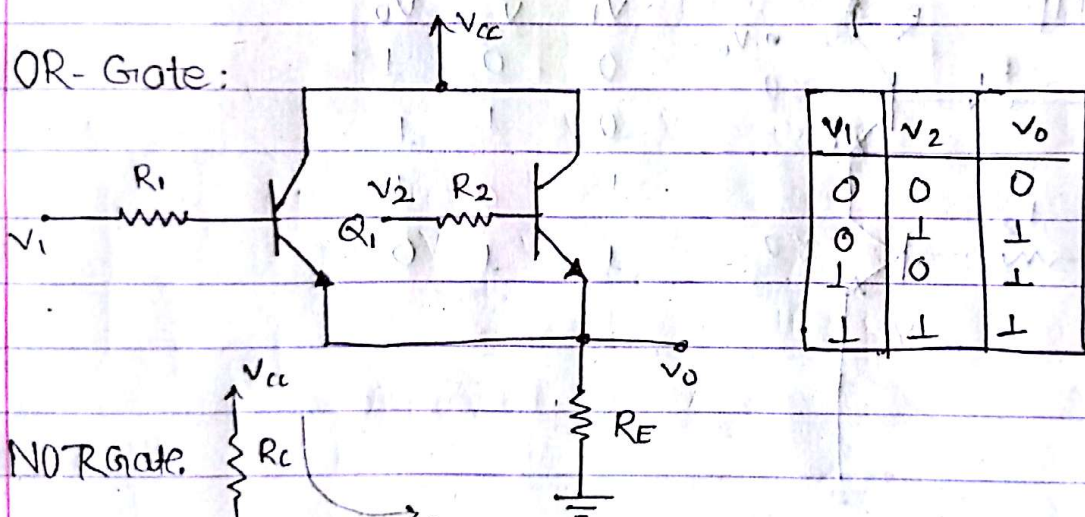


### NOR Gate:

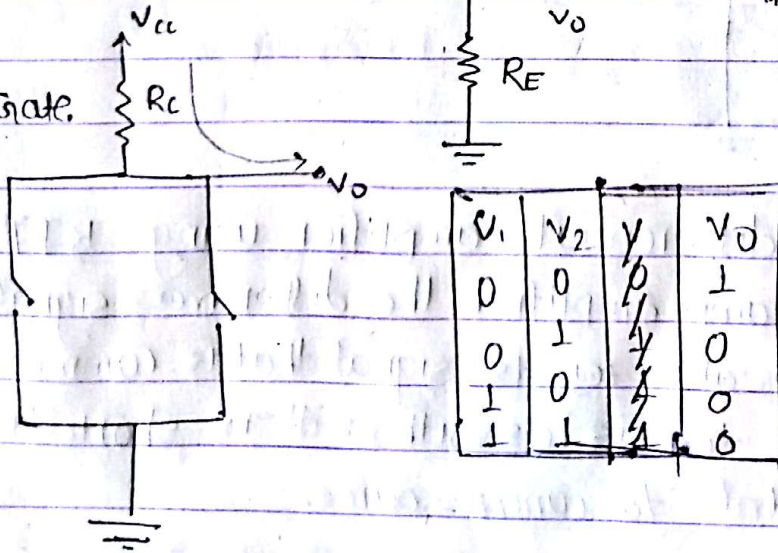

AND Gate :

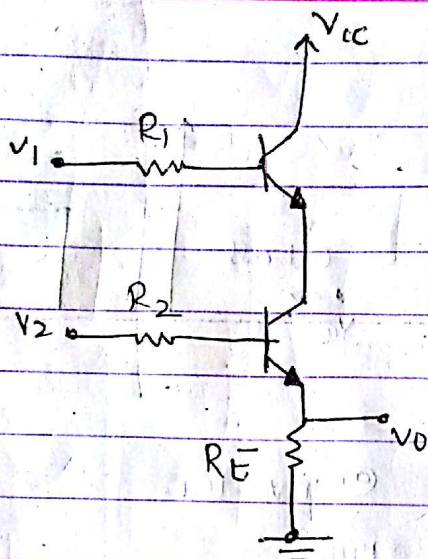


$V_1$	$V_2$	$V_0$
0	0	0
0	1	0
1	0	0
1	1	1

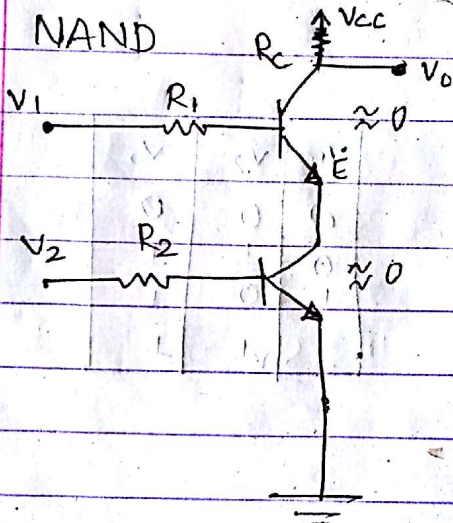

$V_1$	$V_2$	$V_0$
0	0	1
0	1	1
1	0	1
1	1	0

Concept of differential amplifier using BJT

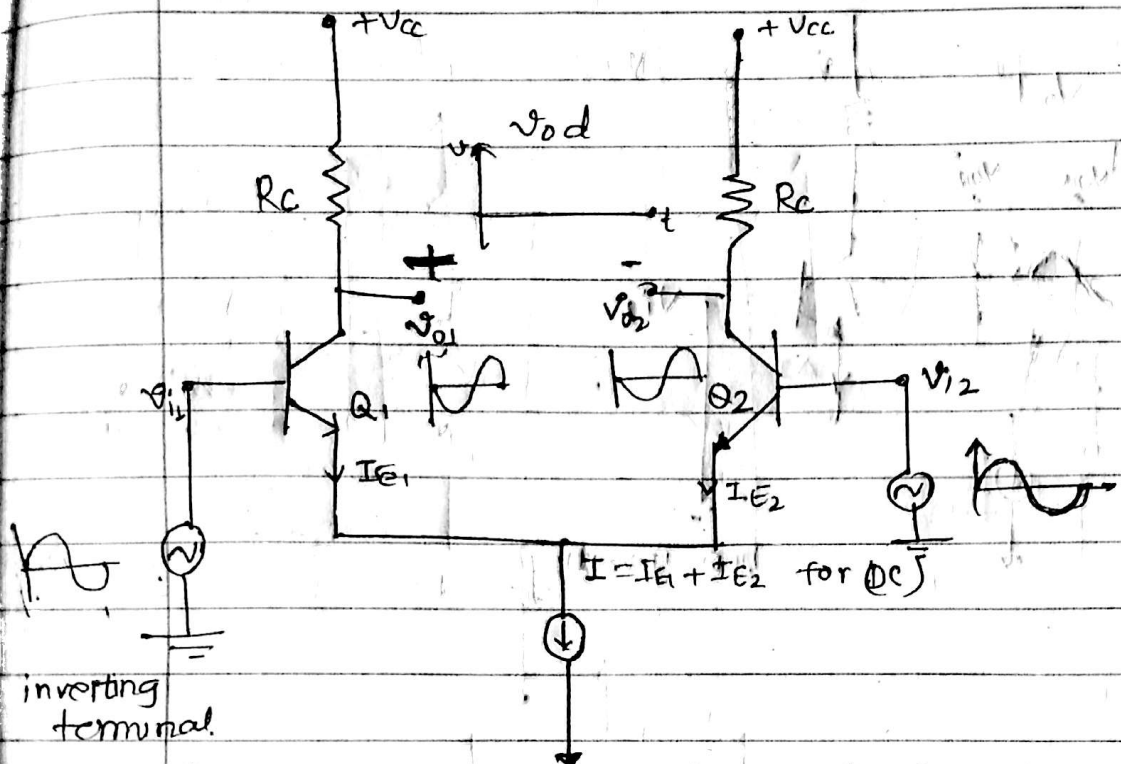- Differential amp. amplifier the difference signal bet<sup>n</sup> two inputs and ideally rejects signal that is common on both.
- two matched transistors with emitters shorted together and connected to current source.




(a) if  $V_{i1} = V_{i2}$  common mode, output is zero.


$$V_{od} = A (V_{i2} - V_{i1})$$


$$\therefore V_{od} = V_{o1} - V_{o2}$$

(b) if  $V_{i1} > V_{i2}$

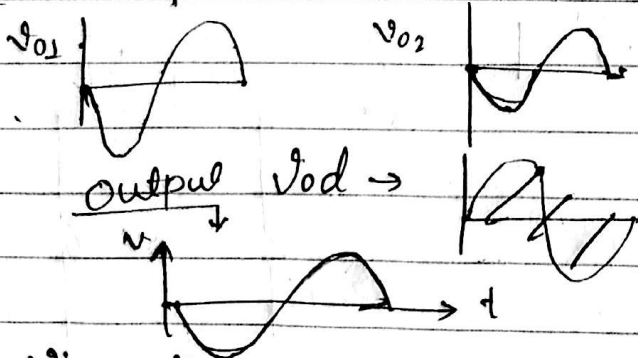

(c) if  $V_{i2} > V_{i1}$

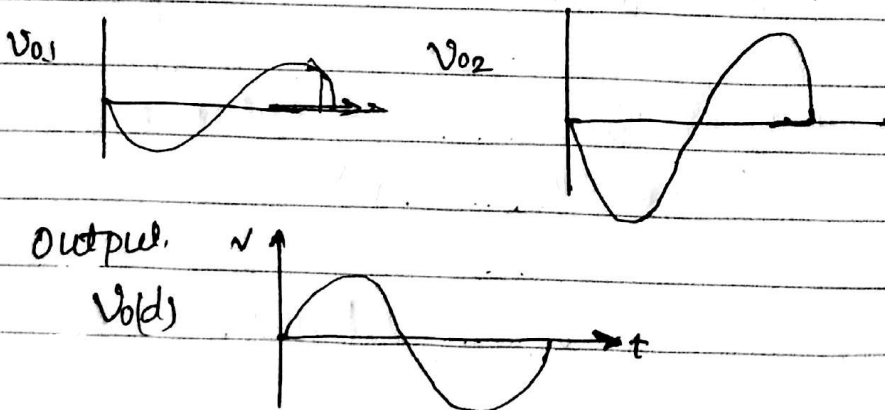

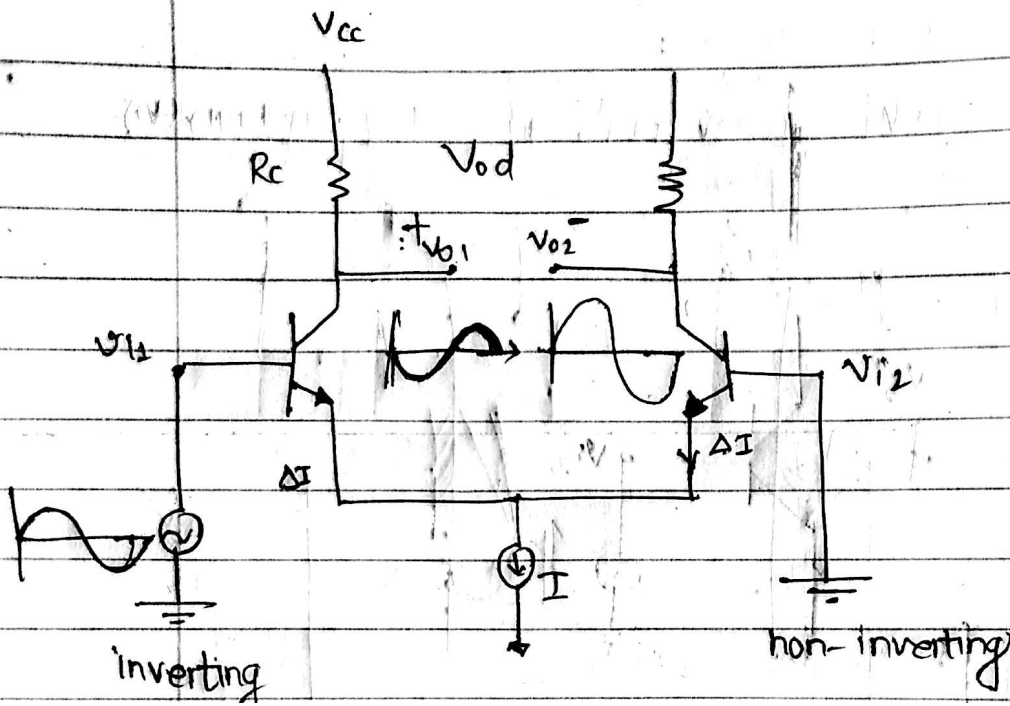

Metal oxide semiconductor

Field effect transistor


MOSFET

FET is


voltage controlled device

Unipolar device

high i/p impedance and low.

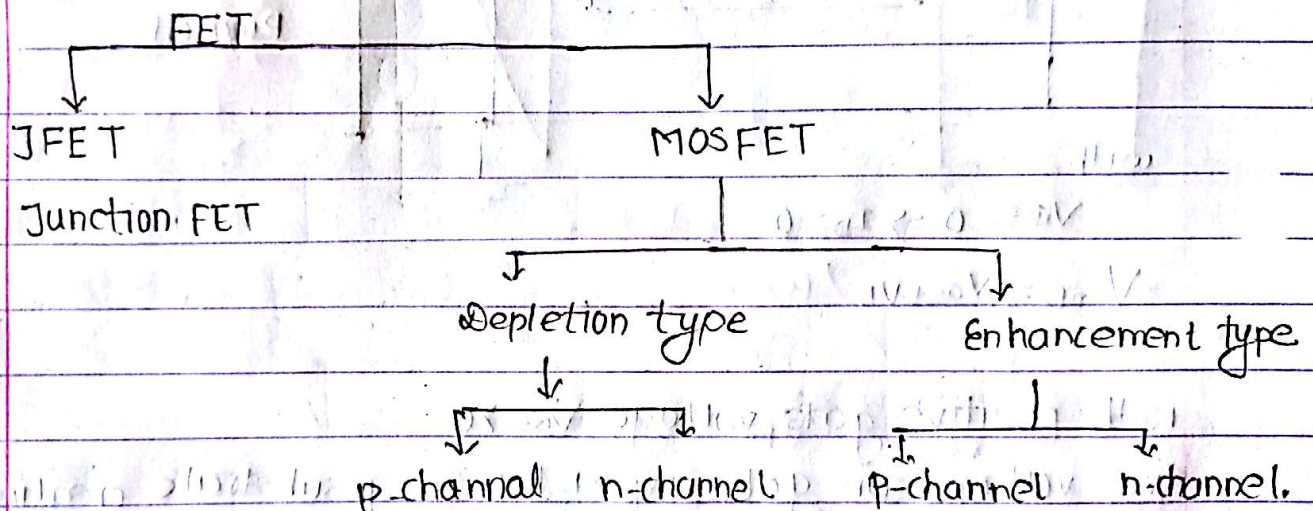

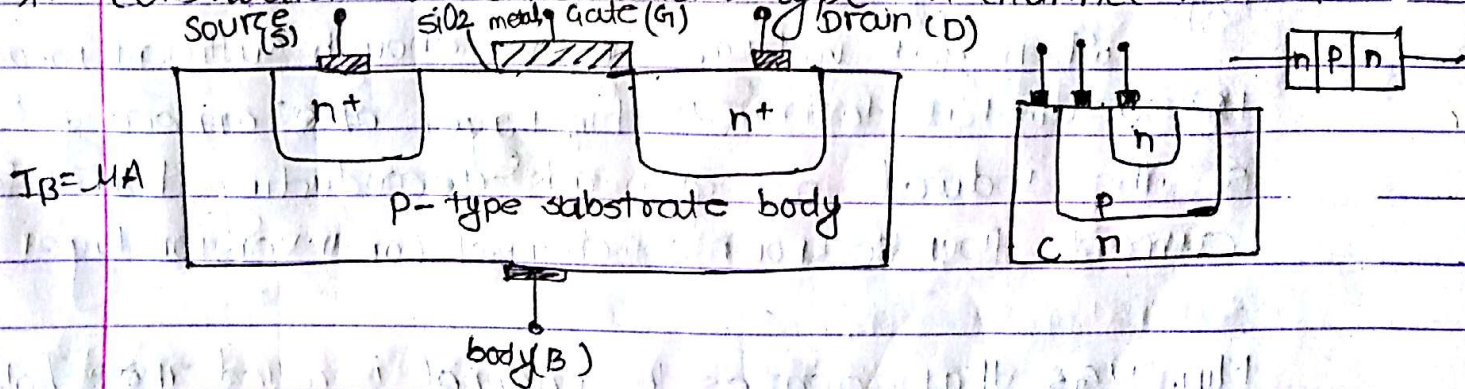
\* Construction of enhancement type n-channel MOSFET



Insulated gate, FET

$I_G = 0$

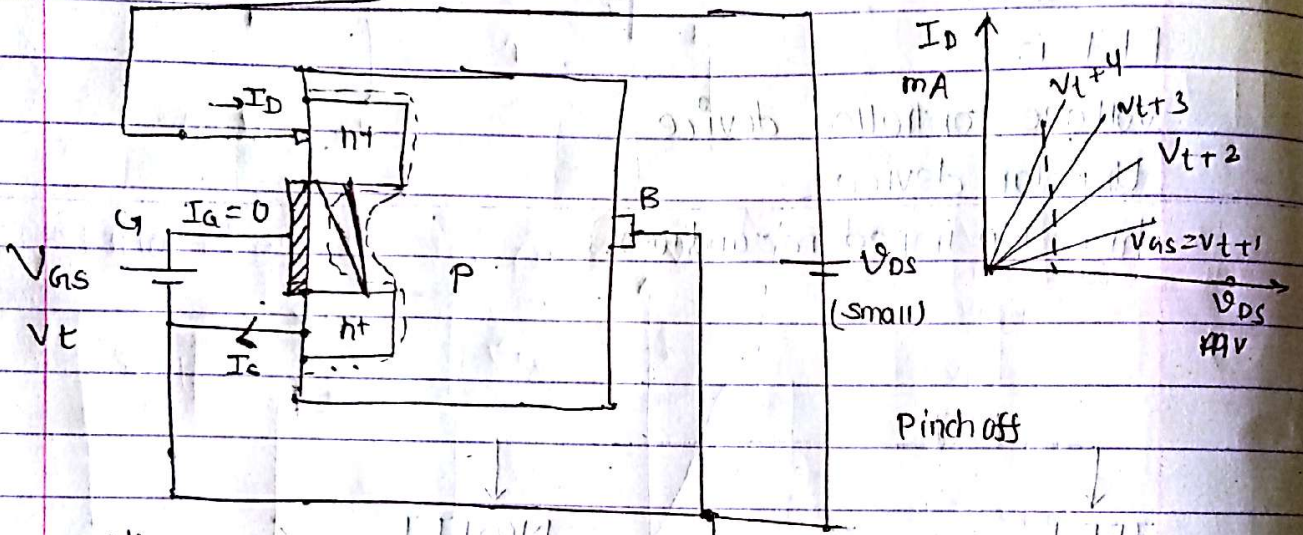② applying a small drain voltage  $V_{DS}$



with,

$$V_{GS} = 0 \Rightarrow I_D = 0$$

$$V_{GD} = V_{GS} + V_D$$

with positive gate voltage  $V_{GS} > 0$

positive voltage on gate repel hole in p substrate creating carrier depletion region  $e^-$  from D and S and accumulate into region under gate.

when gate voltage is +ve enough sufficient no. of  $e^-$  accumulate to form a thin layer of  $e^-$  connecting D and S. The induced n region acts as a conducting channel for current flow so known as channel (or inversion layer)

Min.  $V_{GS}$  that creates the channel is called threshold voltage  $V_t$  (typically 1 to 3v)

When small  $V_{DS}$  is applied the channel is uniform

and current flows drain to source.

if  $V_{GS}$  is further increased conductivity of ch  $\uparrow$  -  
 $i_D \uparrow$  for higher value of  $V_{GS}$ ,

(b) Operation as  $V_{DS}$  is increased while  $V_{GS} = \text{constant}$ .

if  $V_{GS} = \text{constant}$ ,  $V_{DS} \uparrow$

$V_{GD} = (V_{GS} - V_{DS}) \downarrow$  so less


$e^-$  are attracted at drain and channel is no longer uniform but is tapered. The  $i_D$  doesn't rise linearly.

at certain value of  $V_{DS}$ , at which  $V_{GD} = V_{GS} - V_{DS} = V_t$

The depth at drain decreases to zero and ch is said to be pinched off.

Increasing  $V_{DS}$  beyond this value has no effect on channel shape and  $i_D$  saturates

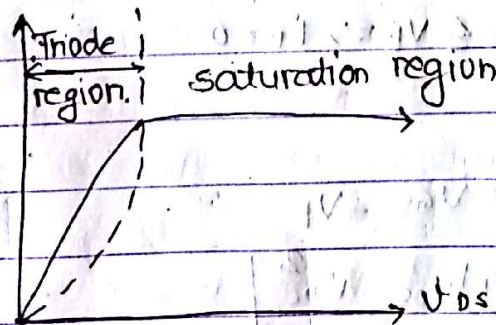voltage at which saturation occurs is  $V_{DS \text{ sat}} = V_{GS} - V_t$




Expression for  $i_D$




$$i_D = K [ 2(V_{GS} - V_t)V_{DS} - V_{DS}^2 ]$$

where,  $K = \text{constant}$  depends on construction of device

Symbol:

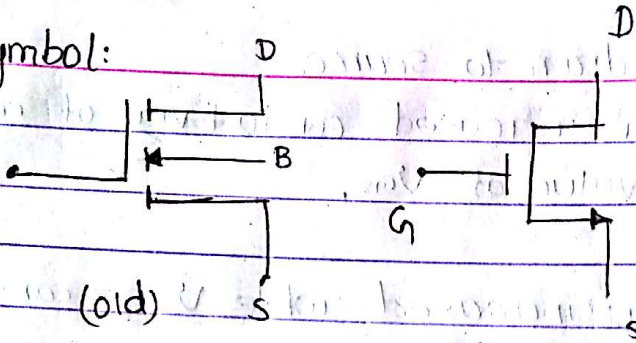

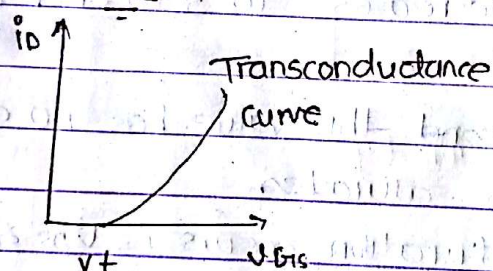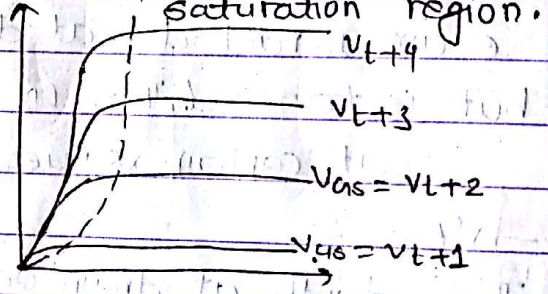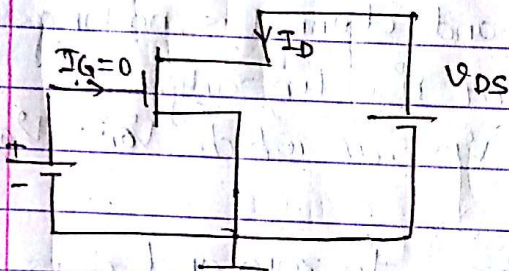Static characteristic curves:  $v_{DS} \leq v_{GS} - v_t$  and  $v_{DS} \geq v_{GS} - v_t$  saturation region.



cut off region,  $v_{GS} \leq v_t \Rightarrow i_D = 0$

Triode region:

$v_{GS} > v_t$  and  $v_{DS} \leq v_{GS} - v_t$

$$\Rightarrow i_D = k [ 2(v_{GS} - v_t)v_{DS} - v_{DS}^2 ]$$


if  $v_{DS}$  is sufficiently small

$$i_D \approx 2k (v_{GS} - v_t) v_{DS}$$



Saturation region.

$$v_{DS} > v_t \text{ and } v_{DS} \geq v_{GS} - v_t \Rightarrow i_D = k (v_{GS} - v_t)^2$$


### MOSFET as logic circuit:

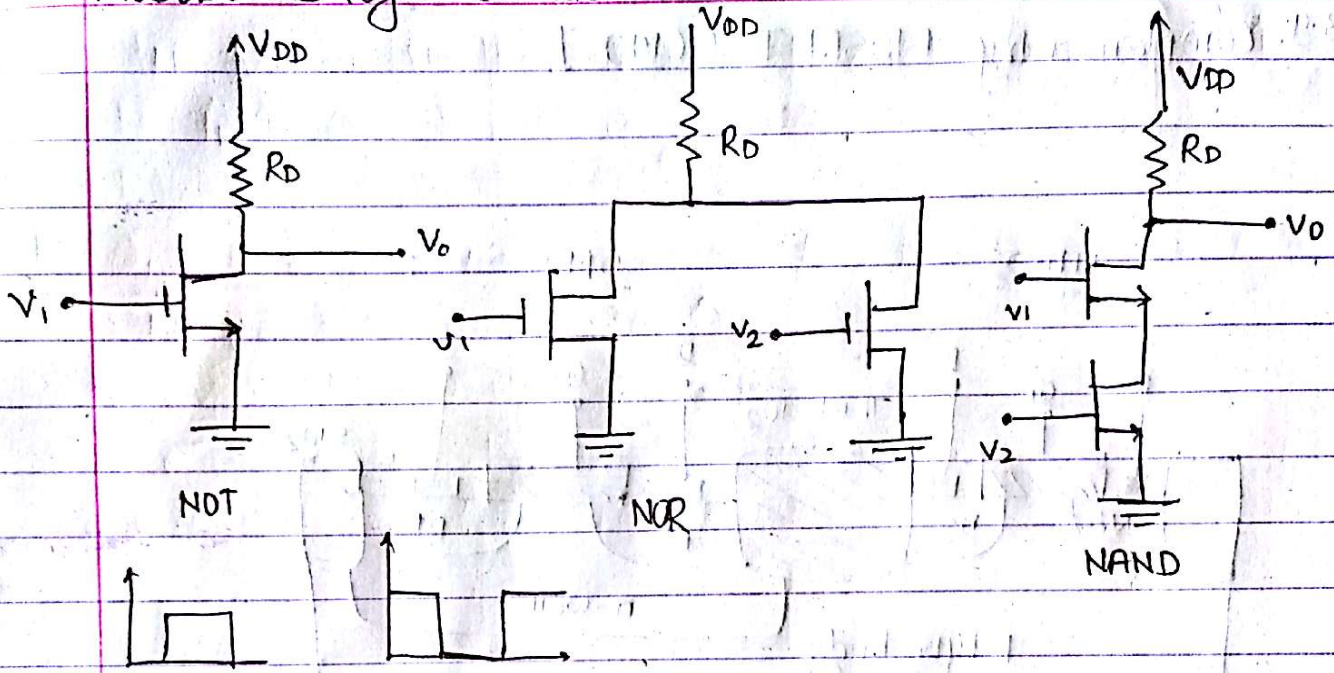

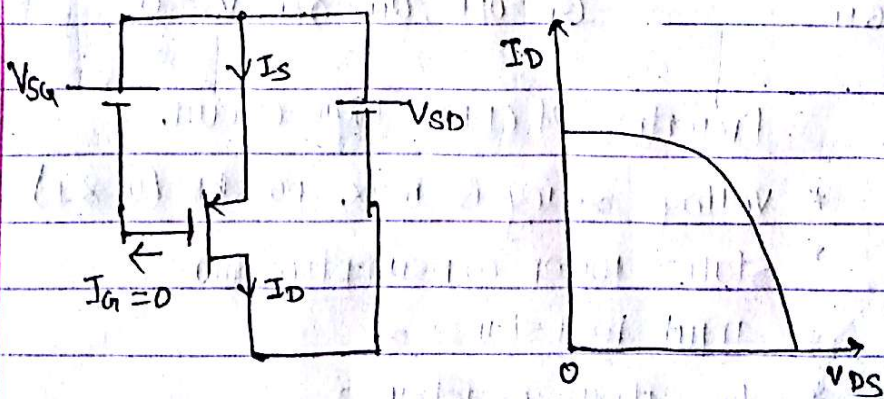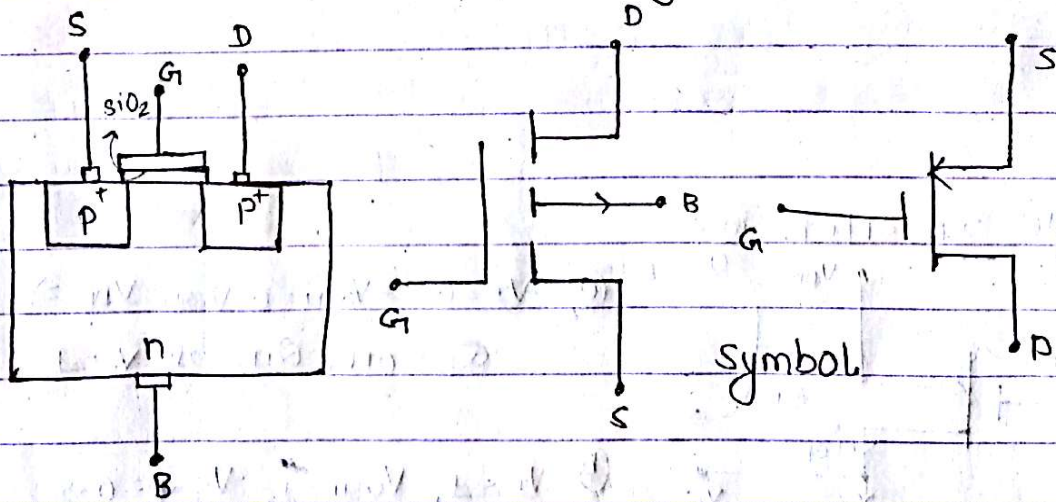
### (3.8) The P-channel enhancement type MOSFET



### 3.9: Complementary MOSFET (CMOS)

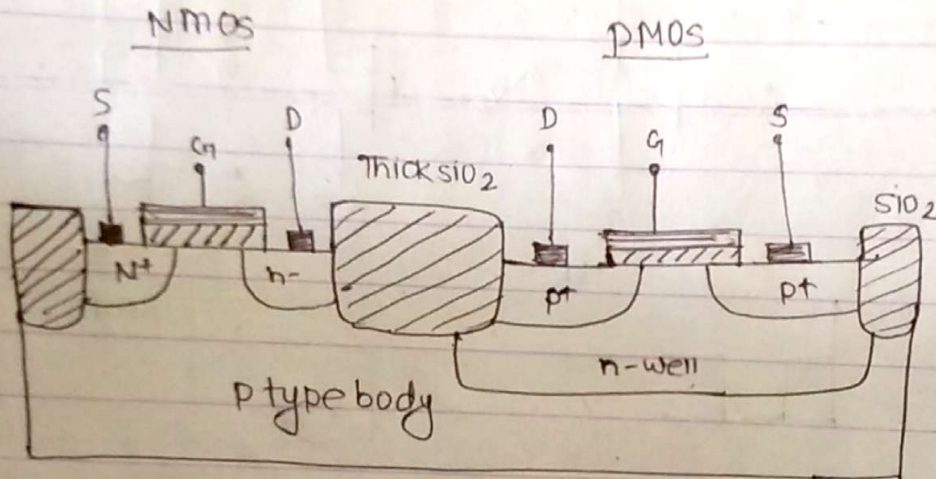

#### Logic Inverter

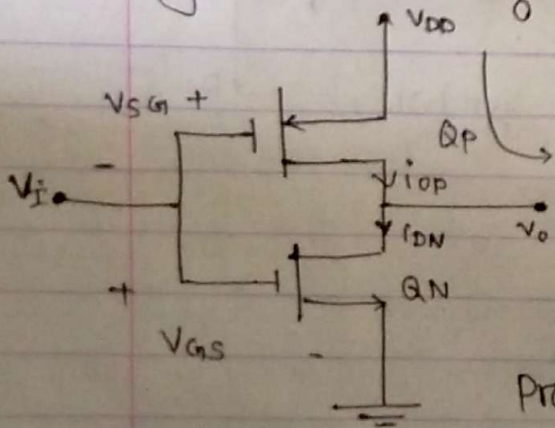

(a)  $V_i = 0 \Rightarrow V_{GSN} = 0, V_{GSP} = V_{DD} \Rightarrow$   
 $Q_P = ON, Q_N = OFF, V_o = 1$


(b)  $V_i = 1, V_{GSN} = 1, V_{GSP} = 0 \Rightarrow$   
 $Q_P = OFF, Q_N = ON, V_o = 0$

#### Properties of CMOS logic circuit.


$V_i$	$V_o$
0	1
1	0

- \* Voltage swing is max. possible (0, & 1)
- \* static power consumption low
- \* input resistance  $\infty$
- \* low output resistance

3.9.1 CMOS logic inverter:

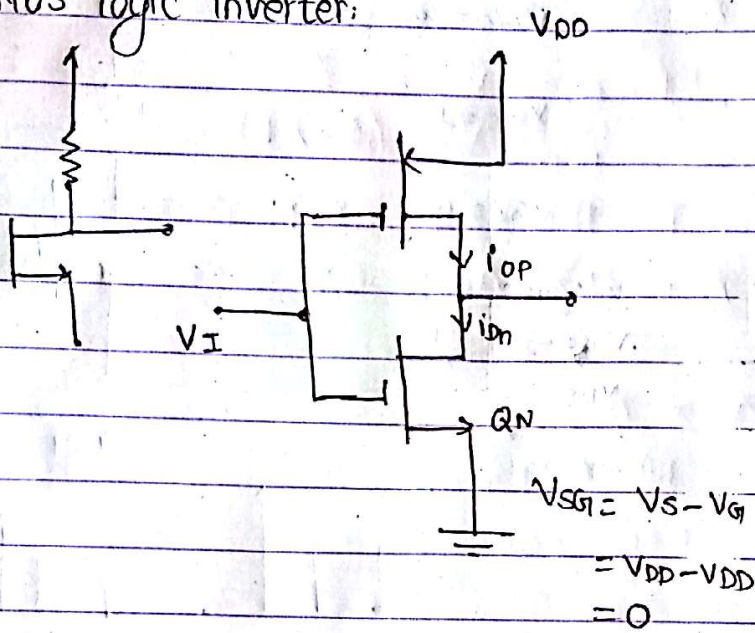

3.10 Depletion type n channel MOSFET.

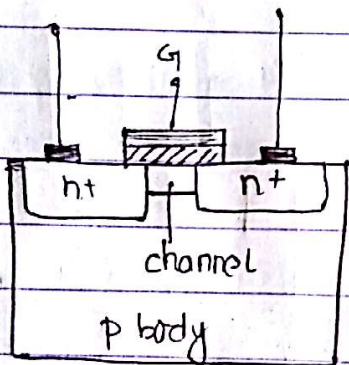



it has physically implanted channel both source and drain.

Working Principle:

- Ⓐ  $V_{GS} = 0 \Rightarrow I_D$  finite
- Ⓑ  $V_{GS} > 0 \Rightarrow I_D \uparrow$
- Ⓒ  $V_{GS} < 0 \Rightarrow I_D \downarrow$

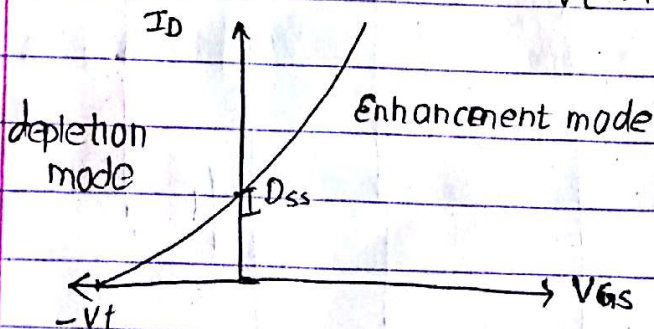at,  $V_{GS} = -V_t \Rightarrow$  channel is depleted of charge carriers  $I_D = 0$   
 $V_t \rightarrow$  threshold voltage (negative)



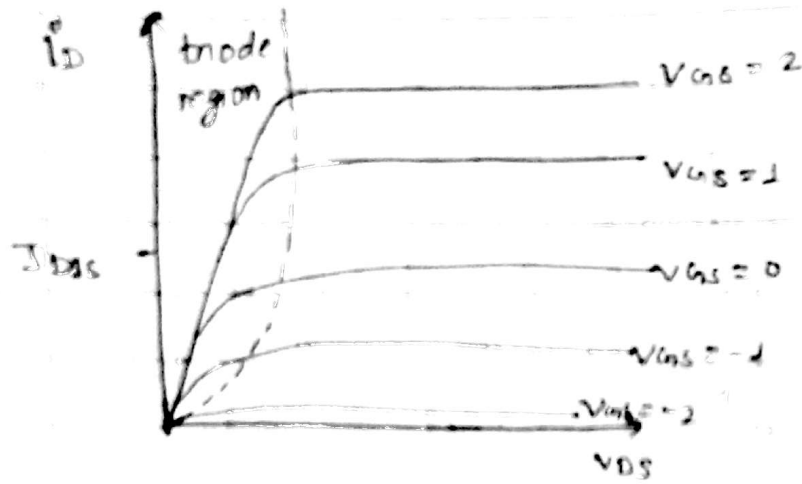


## chapter 4:

### The operational amplifier and Oscillator.
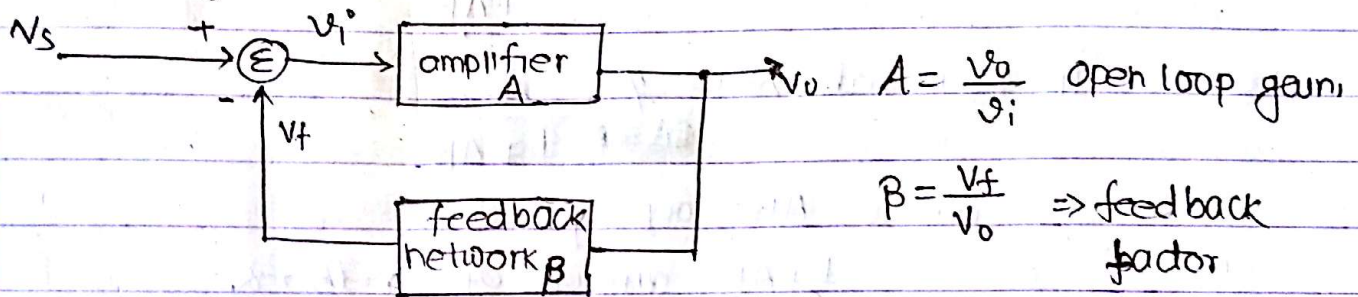
#### 4.1: Basic feedback theory

The process of applying a fraction of output signal back to the input signal is known as feedback.



$$\text{total input, } V_i = V_s + V_f$$

$$\text{closed loop gain, } = \frac{V_o}{V_s}$$

\* Negative (degenerative) feedback  $\Rightarrow$  feedback signal is out of phase with input signal, i.e.,  $V_f = -\beta V_o$  input to amplifier is reduced,

$$V_i = V_s - \beta V_o$$

\* Positive (regenerative) feedback: feedback signal is in phase with input signal, i.e.,  $V_f = \beta V_o$ , input to amplifier is increased,

$$V_i = V_s + \beta V_o$$

Consider a positive feedback system:  $V_f = \beta V_o$

$$\therefore V_o = A V_i$$

$$= A (V_s + V_f)$$

$$V_o = A V_s + A \beta V_o$$

$$V_o(1 - AB) = V_s A$$

Gain of feedback amp.  $A = \frac{V_o}{V_s} = \frac{A}{(1 - AB)}$   
closed loop

Similarly, for -ve feedback amplifier:

$$A_{\text{closed}} = \frac{A}{1 + AB}$$

In General,  $A_{cl} = \frac{A}{1 \mp AB}$

where,  $AB = \text{loop gain}$  and

$1 \mp AB = \text{amount of feedback}$


Generally  $A \rightarrow \infty$

$$A_{cl} = \frac{1}{\frac{1}{A} \mp B} \approx \frac{1}{\mp B}$$

- \* Negative feedback results in
- \* decreased voltage gain.
  - \* improved freq<sup>n</sup> response
  - \* reduced noise
  - \* more linear operation.


Positive feedback .  $\therefore$  increases the gain and stability of amplifier  
is determined by magnitude of loop gain

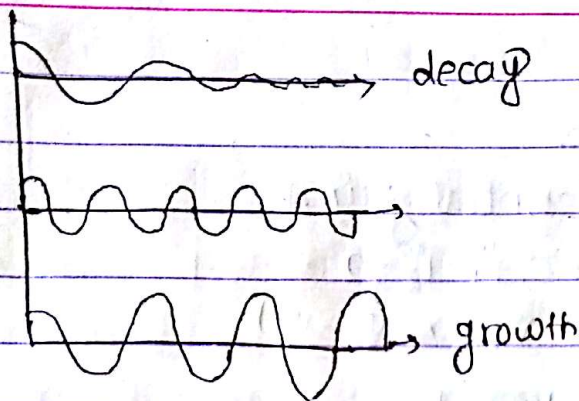- if,  $AB < 1$ , oscillation decays
  - if,  $AB = 1$ , oscillation
  - if,  $AB > 1$ , oscillation growth
- } unstable


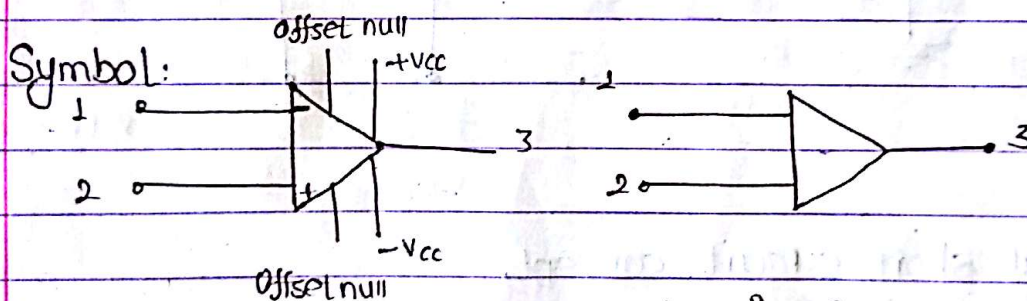
#### 4.2: Operation amp: (Op amp)

- \* a very high gain differential amp with high I/P impedance and low O/P impedance
- \* Performs addition, subtraction, integration, differentiation etc so named op-amp.
- \* available in IC (IC 741)
- \* It has two I/P and one output.



#### Application

+ve, non inverting terminal  
-ve, inverting "

3 - output  
1, 2, input

- Ⓐ analog computation (add, sub, etc) and instrumentation
- Ⓑ voltage buffer
- Ⓒ oscillator circuits and active filter circuits.


### 4.2.1: Ideal Op-amp

characteristic of Op-amp:

- ① Infinite Open loop differential gain  $A$
- ② infinite input impedance,  $i_1 = i_2 = 0$
- ③ Zero output impedance,  $v_o = A(v_2 - v_1)$
- ④ infinite common mode rejection,

$$CMRR = \frac{A_d}{A_{cm}} = \infty$$

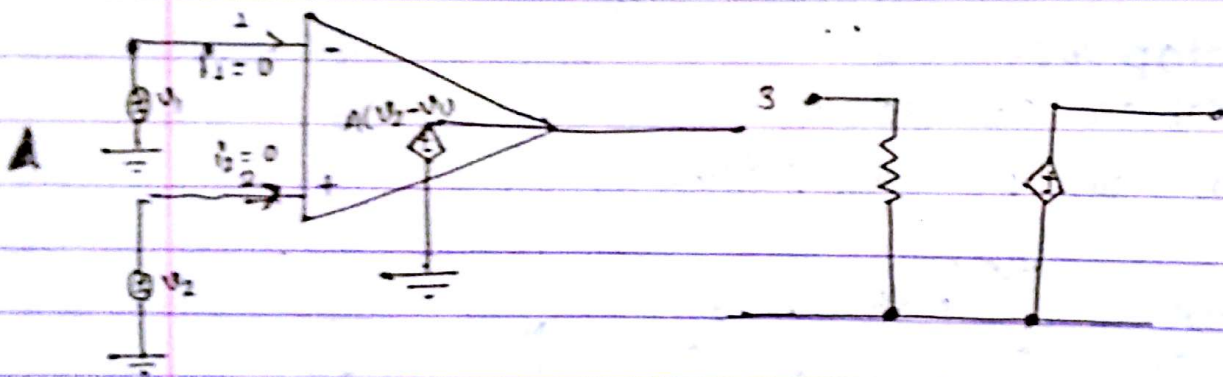- ⑤ infinite bandwidth.  $\rightarrow$  common mode gain
- $A_d$  - diff. gain.



\* Virtual short circuit concept.

$$v_o = A(v_2 - v_1)$$

$$\therefore v_2 - v_1 = v_o / A$$

$$A \rightarrow \infty$$


$$v_2 - v_1 = \frac{v_o}{\infty} \approx 0$$

$$\Rightarrow v_2 = v_1 \text{ Virtual short circuit}$$

It means whatever voltage is at 2 will automatically appear at 1.

731.1  
26

① Inverting amplifier

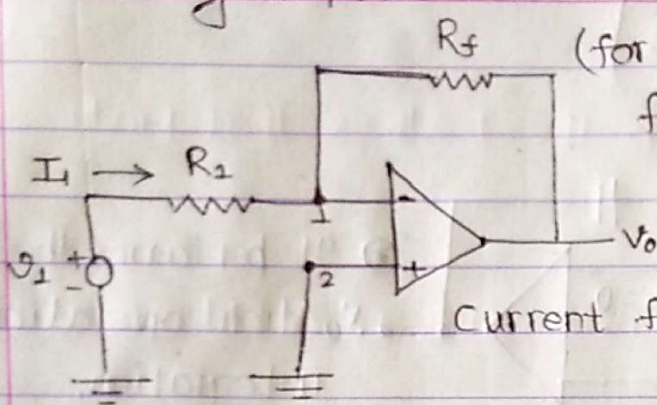

(for ideal op-amp) - Resistance  $\infty$  so current

flows through  $R_f$

from virtual ground concept


$$V_1 = V_2 = 0$$

Current flowing through  $R_1 \Rightarrow I_1 = \frac{V_I - V_0}{R_1}$

$$= \frac{V_I}{R_1}$$

So,  $I_f = I_1$  (ideal op-amp)  $R \rightarrow \infty$

$$= \frac{V_I}{R_1}$$

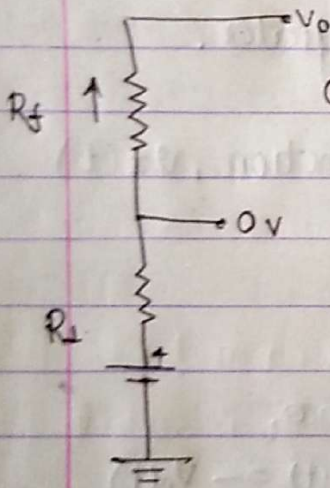


Output voltage,  $V_0 = V_1 - I_f R_f$

$$= 0 - \frac{V_I \cdot R_f}{R_1}$$

$$= - \frac{R_f}{R_1} \cdot V_I$$

$\therefore A_{closed} = \frac{V_0}{V_I} = - \frac{R_f}{R_1}$

② Non-inverting amplifier:

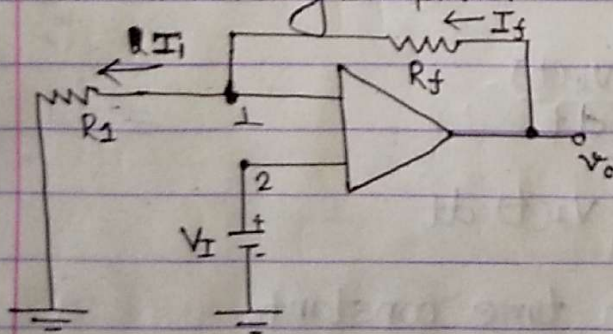

from virtual short circuit concept

$$V_1 = V_2 = V_I$$

Current flowing through  $R_1$

$$I_1 = \frac{V_I}{R_1}$$

for ideal op amp  $\rightarrow R_{in} = \infty$

$$I_1 = I_f$$

Output voltage,  $V_0 = V_1 + I_f R_f$


$$= V_I + \frac{V_I \cdot R_f}{R_1}$$

$$= \left(1 + \frac{R_f}{R_1}\right) V_I$$

$$\therefore \frac{V_0}{V_I} = \left(1 + \frac{R_f}{R_1}\right)$$

$$\therefore A_{open} = \frac{V_o}{V_i} = \left( 1 + \frac{R_f}{R_i} \right)$$

### 4.2.4. Inverting Integrator:

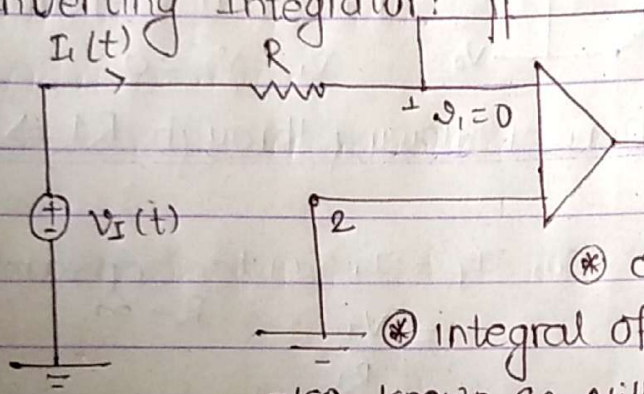

\* It performs the mathematical operation of integration.

\* o/p is proportional to time

\* integral of i/p.

also known as millers integrator.

Let the input be the time varying function,  $V_i(t)$

$$I_i(t) = \frac{V_i(t)}{R}$$

current flowing through C,

$$I_f(t) = C \frac{d(V_c)(t)}{dt} = -C \frac{dV_o(t)}{dt} \quad \text{since, } V_c(t) = -V_o(t)$$


But,

$$\frac{V_i(t)}{R} = -C \frac{dV_o(t)}{dt}$$

$$\therefore V_o(t) = -\frac{1}{RC} \int V_i(t) dt$$

$RC \rightarrow$  integration time constant.

4.2.5. Inverting differentiator:

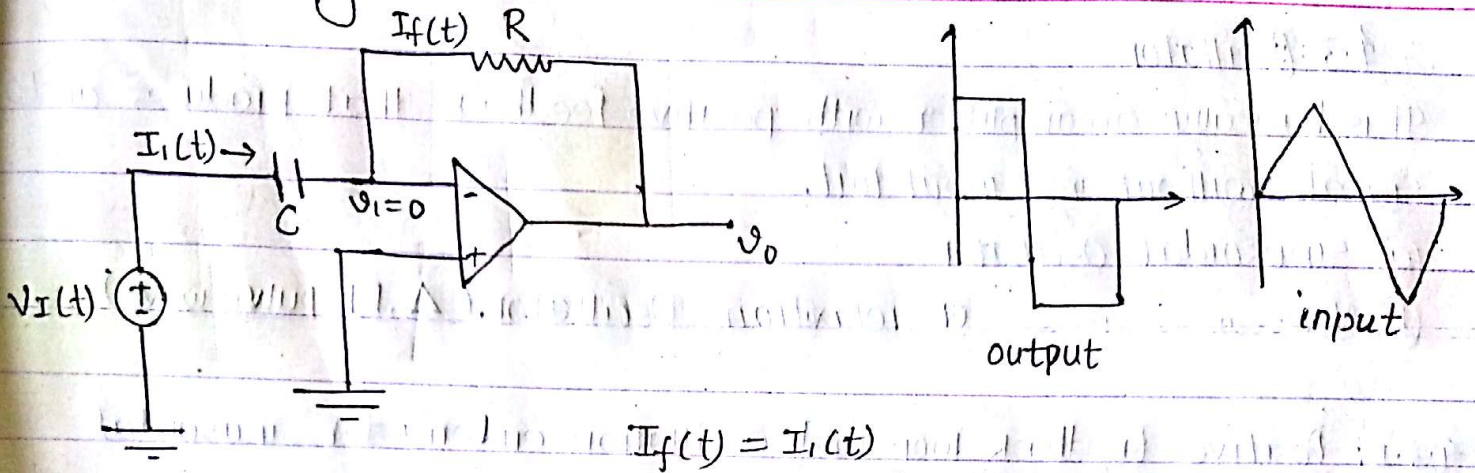

$I_f(t) = I_i(t)$

let, the input be the time varying function,  $V_I(t)$ ,


$$I_i(t) = \frac{C d(V_I(t))}{dt} \quad \because (V_i=0)$$

$$\therefore V_o = -I_f(t)R \quad (\text{for inverting configuration})$$

$$= -C \frac{d(V_I(t))}{dt} \cdot R$$

$$= -RC \frac{dV_I(t)}{dt}$$

4.2.6 Summing amplifier:

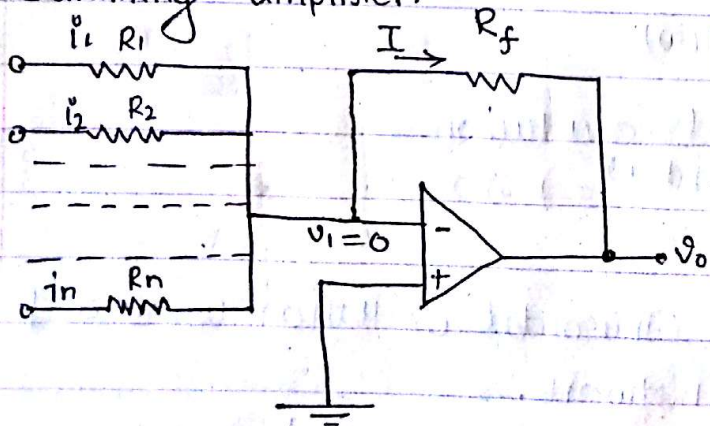

$$I_1 = \frac{V_1}{R_1}, \quad I_2 = \frac{V_2}{R_2}, \quad \dots, \quad I_n = \frac{V_n}{R_n}$$

$$\therefore I = I_1 + I_2 + I_3 + \dots + I_n$$

$$V_o = -I R_f$$

$$= -\left( \frac{V_1}{R_1} R_f + \frac{V_2}{R_2} R_f + \frac{V_3}{R_3} R_f + \dots + \frac{V_n}{R_n} R_f \right)$$

If  $R_1 = R_2 = \dots = R_n = R$

$$V_o = -\left( \frac{V_1 R_f}{R} + \frac{V_2 R_f}{R} + \frac{V_3 R_f}{R} + \dots \right)$$

$$V_o = -\frac{R_f}{R} \left[ V_1 + V_2 + \dots + V_n \right]$$


### 1.3: Oscillator

It is basically an amplifier with positive feedback that produces an output signal without any input to it.

(a) Sinusoidal Oscillator

(b) Non- " " or relaxation Oscillator. ( $\Delta$ ,  $\square$  pulse wave)

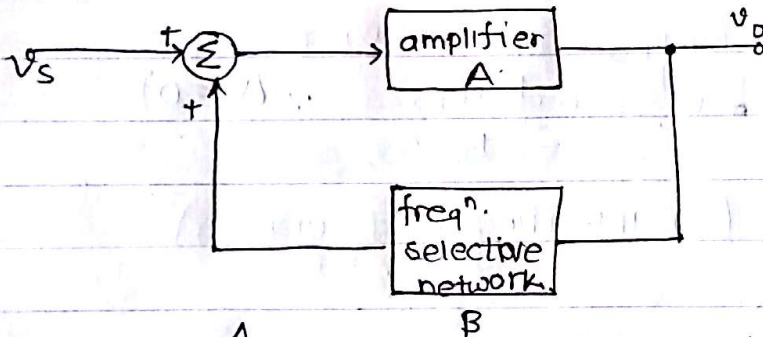4.3.1: Positive feedback loop and oscillation criteria for sinusoidal Oscillation.



$$A_{closed} = \frac{A}{1 - AB}$$

if  $v_o \Rightarrow AB = 1, A_{cl} = \infty$

Generally both amplifier and feedback factor is function of freq<sup>n</sup> so loop gain is complex.


$$L(j\omega) = A(j\omega) B(j\omega) = |A(j\omega) B(j\omega)| e^{j\phi(\omega)}$$

condition for sinusoidal oscillation,

$$L(j\omega) = |A(j\omega) B(j\omega)| e^{j\phi(\omega)} = 1 \angle 0^\circ$$

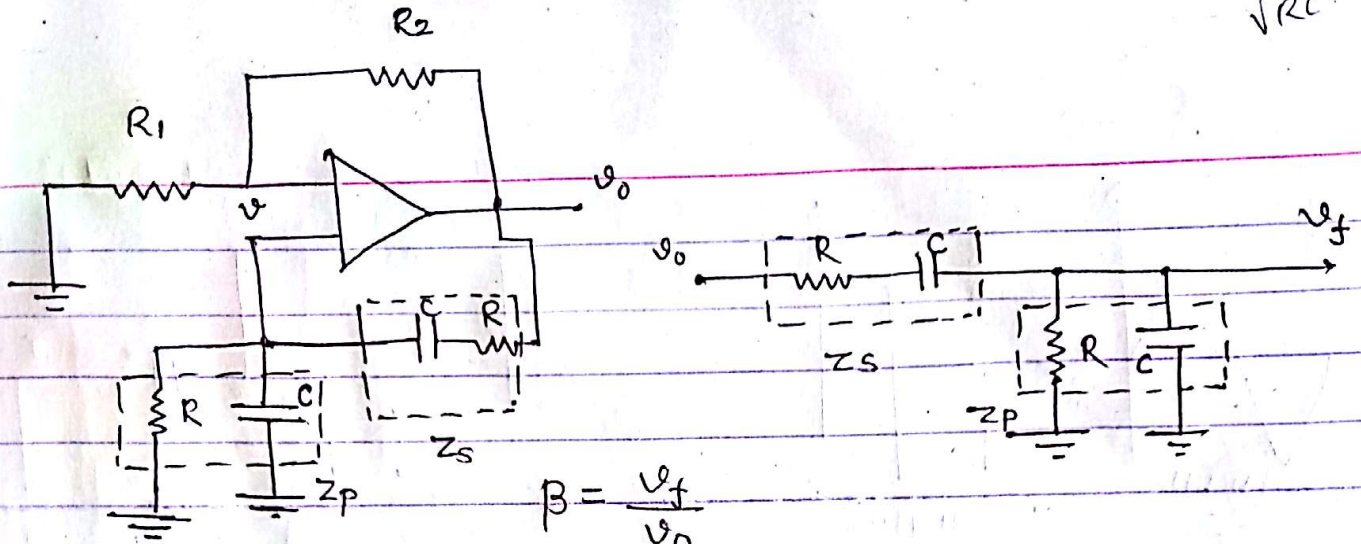1.3.2. Wien bridge Oscillator for Sinusoidal oscillation uses a feedback network called lead lag network.

amplifier is non inverting conf<sup>n</sup>.  $A = \left( 1 + \frac{R_f}{R_1} \right)$  be ph.



$$\beta = \frac{V_f}{V_o}$$

$$V_f = \frac{Z_p}{Z_p + Z_s} V_o$$

$$\therefore \beta = \frac{V_f}{V_o} = \frac{Z_p}{Z_p + Z_s} = \frac{R \parallel (-jX_c)}{[R \parallel (-jX_c)] + (R - jX_c)}$$

$$= \frac{V_f}{V_o} = \frac{1}{3 + j\left(\frac{R}{X_c} - \frac{X_c}{R}\right)}$$

$$= \frac{1}{\sqrt{9 + \left(\frac{R}{X_c} - \frac{X_c}{R}\right)^2}} \angle \tan^{-1}\left(\frac{\frac{R}{X_c} - \frac{X_c}{R}}{3}\right)$$


The phase of lead-lag network will be zero when imaginary term vanishes,

$$\frac{X_c}{R} - \frac{R}{X_c} = 0$$

$$\text{or, } R^2 = X_c^2$$

$$\therefore R = X_c$$
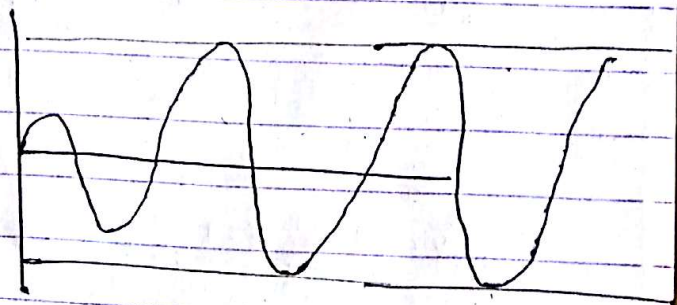
$$R = X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$



for oscillation,  $|\beta| = \frac{1}{3}$ ,  $|AB| = 1$

$$\text{or, } |AB| = 1$$

$$\left(\frac{1+R_f}{R_1}\right) \frac{1}{3} = 1 \Rightarrow \boxed{\frac{R_f}{R_1} = 2}$$



# Civinnovate

Discover, Learn, and Innovate in Civil Engineering